

Digital Design

A Datapath and Control Approach

Chris Coulston

January 8, 2025

This document was prepared with L^AT_EX.

Digital Design - A Datapath and Control Approach © 2024 by Christopher Coulston is licensed under CC BY-NC-SA 4.0 For more information about the Create Commons license see: <https://creativecommons.org/licenses/by-nc-sa/4.0/>



Contents

Contents	iv
1.0 Exercises	2
2.2 Exercises	4
3.0 Exercises	15
4.0 Exercises	24
5.0 Exercises	36
6.0 Exercises	40
7.0 Exercises	49
8.0 Exercises	68

Homework Solutions

1.0 Exercises

1. (1 pt. each) Syllabus:

- What is the late penalty for homework?
There is a 33% deduction per day.
- True or False: Calculators can be used during exams.
You cannot use calculators at my exams.
- True or False: University ID is required during exams.
I check ID at the exams. After I learn your names its not such a big deal, but bring it to be safe.
- What is my thesis regarding grades?
- Bob L. Student has the following grades. Determine his final overall course percentage and grade.

Component	Percentage
Homework	60%
Exam 1	90%
Exam 2	80%
Final	70%

Component	Percentage	Weight
Homework	60%	$60 \cdot 0.35 = 21$
Exam 1	90%	$90 \cdot 0.20 = 18$
Exam 2	80%	$80 \cdot 0.20 = 16$
Final	70%	$70 \cdot 0.25 = 17.5$
Total	72.5%	C

- How should you prepare for the 43rd lecture?
Look over homework problem 8.10, page 165

2. (1 pt. each) Convert the following numbers to decimal. Show work, or receive 1/2 credit.

- 100_2 $100_2 = 2^2 = 4_{10}$
- 1000_2 $1000_2 = 2^3 = 8_{10}$
- 10000_2 $10000_2 = 2^4 = 16_{10}$
- 100000_2 $100000_2 = 2^5 = 32_{10}$
- 111111_2 $111111_2 = 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0 = 63_{10}$
- 1000100101000101_2 $1000100101000101_2 = 2^{15} + 2^{11} + 2^8 + 2^6 + 2^5 + 2^0 = 35141_{10}$
- $3EA_{16}$ $3EA_{16} = 001111101010 = 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^3 + 2^1 = 1002_{10}$

3. (1 pt. each) Convert the following number to binary. Show work, or receive 1/2 credit.

- 44_{16} $44_{16} = 01000100_2$
- 44_{10} $44_{10} = 32 + 8 = 2^5 + 2^3 = 101100_2$
- 1023_{10} $1023_{10} = 512 + 256 + 128 + 64 + 32 + 16 + 8 + 4 + 2 + 1 = 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0 = 111111111_2$

4. **(1 pt. each)** Convert the following number to hex. Show work, or receive 1/2 credit.
- a) 101011101_2 $101011101_2 = 15D_{16}$
- b) 77_{10} $77_{10} = 64 + 8 + 4 + 1 = 2^6 + 2^3 + 2^2 + 2^0 = 1001101_2 = 4D_{16}$
5. **(2 pts. each)** Toughies:
- a) Convert 123_5 to base-12 $123_5 = 1 * 5^2 + 2 * 5^1 + 3 * 5^0 = 25 + 10 + 3 = 38_{10} = 3 * 12^1 + 2 * 12^0 = 32_{12}$
- b) Convert 789_{12} to base-5 $789_{12} = 7 * 12^2 + 8 * 12^1 + 9 * 12^0 = 1008 + 96 + 9 = 1113_{10} = 1 * 5^4 + 3 * 5^3 + 4 * 5^2 + 2 * 5^1 + 3 * 5^0 = 13423_5$
- c) What is the largest base-10 quantity that can be represented using 5 digits in base 12?
- $$BBBBB_{12} = 11 * 12^4 + 11 * 12^3 + 11 * 12^2 + 11 * 12^1 + 11 * 12^0 = 248831_{10}$$
6. **(1 pt. each)** Perform the following additions, assume a word size of four bits. Determine if overflow occurs.
- a) $0110_2 + 0101_2$ $0110 + 0101 = 1011$
- b) $0010_2 + 0110_2$ $0010 + 0110 = 1000$
- c) $0111_2 + 0011_2$ $0111 + 0011 = 1010$
- d) $0010_2 + 0101_2$ $0010 + 0101 = 0111$
- e) $0010_2 + 1010_2$ $0010 + 1010 = 1100$
- f) $0101_2 + 1011_2$ $0101 + 1011 = 10000$ *overflow*
- g) $0011_2 + 1001_2$ $0011 + 1001 = 1100$

2.2 Exercises

1. (2 pts. each) Given: $F(A, B, C, D) = (AB' + (C + (AD)')(BD))'$

- a) Determine the truth table for $F(A, B, C, D)$

Solution

$$\text{Let } T_3 = C + (AD)'$$


$$T_4 = BD$$

$$T_1 = AB' \quad T_5 = T_3 * T_4$$

A	B	C	D	AB'	(AD)'	C+(AD)'	BD	T3*T4	T1+T5	F
0	0	0	0	0	1	1	0	0	0	1
0	0	0	1	0	1	1	0	0	0	1
0	0	1	0	0	1	1	0	0	0	1
0	0	1	1	0	1	1	0	0	0	1
0	1	0	0	0	1	1	0	0	0	1
0	1	0	1	0	1	1	1	1	1	0
0	1	1	0	0	1	1	0	0	0	1
0	1	1	1	0	1	1	1	1	1	0
1	0	0	0	1	1	1	0	0	1	0
1	0	0	1	1	0	0	0	0	1	0
1	0	1	0	1	1	1	0	0	1	0
1	0	1	1	1	0	1	0	0	1	0
1	1	0	0	0	1	1	0	0	0	1
1	1	0	1	0	0	0	1	0	0	1
1	1	1	0	0	1	1	0	0	0	1
1	1	1	1	0	0	0	1	1	1	0

- b) Draw a schematic of the logic circuit which realizes F as shown, i.e. do not use Boolean Algebra on F .

Solution

 

2. (2 pts. each) For the circuit in Figure 2.1

- a) Write a Boolean expression for the function.

Solution $F(A, B, C, D) = (AB + C)D' + ABD'$

- b) Draw the truth table for the function.

Solution

A	B	C	D	$AB+C$	$(AB+C)D'$	ABD'	F
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	1	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	0	0	1
1	0	1	1	1	1	0	0
1	1	0	0	1	0	1	1
1	1	0	1	1	1	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	0	0	0

 


Figure 2.1: The circuit for Problems 2 and 3.

3. (2 pts. each) For the functions F, G, H, I defined by the truth table shown below:

a) Determine the canonical SOP and POS realization for F, G, H, I .

Solution

$$F(A,B,C) = (A+B+C)(A+B'+C')(A'+B+C')(A'+B'+C) = A'B'C + A'BC' + AB'C' + ABC$$

$$G(A,B,C) = (A'+B+C)(A'+B'+C') = A'B'C' + A'B'C + A'BC' + A'BC + AB'C + ABC'$$

$$H(A,B,C) = (A+B'+C)(A+B'+C')(A'+B+C)(A'+B+C')(A'+B'+C) = A'B'C' + A'B'C + ABC'$$

$$I(A,B,C) = (A+B+C)(A+B'+C)(A'+B+C)(A'+B'+C) = A'B'C + A'BC + AB'C + ABC$$

b) Draw the circuit diagram for the canonical SOP and POS realization.

Solution

Treat each output independently of the other. For example when working with function I , cover up the columns F, G and H .

A	B	C	F	G	H	I
0	0	0	0	1	1	0
0	0	1	1	1	1	1
0	1	0	1	1	0	0
0	1	1	0	1	0	1
1	0	0	1	0	0	0
1	0	1	0	1	0	1
1	1	0	0	1	1	0
1	1	1	1	0	0	1

4. **(2 pts. each)** Prove the validity of the following statements using the laws of Boolean Algebra. For each step of the proof, identify which law was used.

a) $X'Y' + XY + X'Y = X' + Y$

Solution

$$\begin{aligned}
 X'Y' + XY + X'Y &= && 3D \\
 X'Y' + X'Y + XY + X'Y &= && 8 \\
 X'(Y' + Y) + Y(X + X') &= && 5 \\
 X' + Y &= && QED
 \end{aligned}$$

b) $(X + Y')X'Y' = X'Y'$

Solution

$$\begin{aligned}
 (X + Y')X'Y' &= && 8 \\
 XX'Y' + X'Y'Y' &= && 5D \\
 0 + X'Y' &= && 1 \\
 X'Y' &= && QED
 \end{aligned}$$

c) $(X + Y)(X' + Z) = XZ + X'Y$

Solution

$$\begin{aligned}
 (X + Y)(X' + Z) &= && 8 \\
 (X + Y)X' + (X + Y)Z &= && 8 \\
 XX' + YX' + XZ + YZ &= && 1D, 5 \\
 YX' + XZ + YZ(X + X') &= && 8 \\
 YX' + XZ + XYZ + X'YZ &= && 6 \\
 X'Y + X'YZ + XZ + XYZ &= && 1D, 8 \\
 X'Y(1 + Z) + XZ(1 + Y) &= && 2, 1D \\
 X'Y + XZ &= && QED
 \end{aligned}$$

d) $X'Y' + (X + Y)Z = X'Y' + Z$

Solution

$$\begin{aligned}
 X'Y' + (X + Y)Z &= && 8 \\
 X'Y' + XZ + YZ &= && 1D, 5 \\
 X'Y'*(Z + Z') + XZ + YZ(X + X') &= && 8 \\
 X'Y'Z' + X'Y'Z + XZ + XYZ + X'YZ &= && 3 \\
 X'Y'Z' + X'Y'Z + X'Y'Z + XZ + XYZ + X'YZ &= && 8 \\
 X'Y'(Z + Z') + XZ(1 + Y) + X'Z(Y' + Y) &= && 5, 1D \\
 X'Y' + XZ + X'Z &= && 8 \\
 X'Y' + Z(X + X') &= && 5, 1D \\
 X'Y' + Z &= && QED
 \end{aligned}$$

e) $A'C + BC + AB = A'C + AB$

Solution

$$\begin{aligned}
 A'C + BC + AB &= & 1D, 5 \\
 A'C + (A+A')BC + AB(C+C') &= & 8 \\
 A'C + ABC + A'BC + ABC + ABC' &= & 3 \\
 A'C + A'BC + ABC + ABC' &= & 8 \\
 A'C(1+B) + AB(C+C') &= & 5, 1D \\
 A'C + AB &= & QED
 \end{aligned}$$

f) $A(B + C) = AB + AB'C$

Solution

$$\begin{aligned}
 AB + AB'C &= & 1D, 5 \\
 AB(C+C') + AB'C &= & 8 \\
 ABC + ABC' + AB'C &= & 3 \\
 ABC + ABC + ABC' + AB'C &= & 6 \\
 ABC + ABC' + ABC + AB'C &= & 8 \\
 AB(C+C'+C) + AB'C &= & 8 \\
 AB + AB'C &= & QED
 \end{aligned}$$

g) $(A + B + C)(A + B + C')(A' + B + C')(A' + B' + C') = (A + B)(A' + C')$

Solution

$$\begin{aligned}
 (A+B+C)(A+B+C')(A'B+C')(A'+B'+C') &= & 4 \\
 ((A+B+C)(A+B+C')(A'B+C')(A'+B'+C'))' &= & 9D \\
 (A'B'C + A'B'C' + AB'C + ABC)' &= & 8 \\
 (A'B'(C+C') + AC(B'+B))' &= & 5, 1D \\
 (A'B' + AC)' &= & 9 \\
 (A+B)(A'+C') &= & QED
 \end{aligned}$$

5. (4 pts.) Design a circuit called MUX2. MUX2 has three bits of input S, y_0, y_1 and one bit of output F . If $S = 0$, then $F = y_0$; else if $S = 1$, then $F = y_1$.

- a) Write down the truth table for the MUX2 function.

Solution

S	y_0	y_1	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- b) Determine the canonical SOP realization for MUX2; do not simplify.

Solution $F = S'y_0y_1' + S'y_0y_1 + Sy_0'y_1 + Sy_0y_1$

6. (6 pts.) Design a circuit called MUX4. MUX4 has six bits of input $S_1S_0, y_0, y_1, y_2, y_3$ and one bit of output F .

If $S_1S_0 = 00$ then $F = y_0$

else if $S_1S_0 = 01$ then $F = y_1$

else if $S_1S_0 = 10$ then $F = y_2$

else if $S_1S_0 = 11$ then $F = y_3$

Without writing down the truth table determine a SOP expression to realize F by listing all possible inputs which will cause F to equal 1. Then try to simplify your expression using Boolean Algebra.

Solution

The output F only equals one in the following cases.

$$S1=0 \ S0=0 \text{ and } y0=1$$

$$S1=0 \ S0=1 \text{ and } y1=1$$

$$S1=1 \ S0=0 \text{ and } y2=1$$

$$S1=1 \ S0=1 \text{ and } y3=1$$

With this information we can form four product terms, one for each input, that equal 1 only for that input. ORing together these product terms will give us the solution to the problem.

$$F = S_1'S_0'y_0 + S_1'S_0y_1 + S_1S_0'y_2 + S_1S_0y_3$$

7. (4 pts.) Design a logic circuit called MAJ which has three inputs A,B,C and one output Z. The output equals 1 when a majority of the inputs are equal to 1, otherwise the output is 0.

- a) Write the truth table for the MAJ function.

Solution

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- b) Determine the canonical SOP realization for the MAJ function, do not simplify.

$$\text{Solution } F = A'BC + AB'C + ABC' + ABC$$

8. (4 pts.) Let X and Y each be 2-bit signals whose elements are x_1x_0 and y_1y_0 respectively. Determine the $\sum m$ and $\prod M$ expression for a circuit whose 1-bit output z is defined by the following statement.

if (X == Y) then z = 1 else z = 0

Solution

a_1	a_0	b_1	b_0	A	B	z
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	2	0
0	0	1	1	0	3	0
0	1	0	0	1	0	0
0	1	0	1	1	1	1
0	1	1	0	1	2	0
0	1	1	1	1	3	0
1	0	0	0	2	0	0
1	0	0	1	2	1	0
1	0	1	0	2	2	1
1	0	1	1	2	3	0
1	1	0	0	3	0	1
1	1	0	1	3	1	0
1	1	1	0	3	2	0
1	1	1	1	3	3	1

Yielding

$$z = \sum m(0, 5, 10, 15) = \prod M(1, 2, 3, 4, 6, 7, 8, 9, 11, 12, 13, 14)$$

9. (4 pts.) Let X and Y each be 2-bit signals whose elements are x_1x_0 and y_1y_0 , respectively. Determine the $\sum m$ and $\prod M$ expressions for a circuit whose 1-bit output z is defined by the following statement.

if ($X + Y > 3$) then $z = 0$ else $z = 1$

Solution

a_1	a_0	b_1	b_0	A	B	z
0	0	0	0	0	0	1
0	0	0	1	0	1	1
0	0	1	0	0	2	1
0	0	1	1	0	3	1
0	1	0	0	1	0	1
0	1	0	1	1	1	1
0	1	1	0	1	2	1
0	1	1	1	1	3	0
1	0	0	0	2	0	1
1	0	0	1	2	1	1
1	0	1	0	2	2	0
1	0	1	1	2	3	0
1	1	0	0	3	0	1
1	1	0	1	3	1	0
1	1	1	0	3	2	0
1	1	1	1	3	3	0

Leading to the answer $z = \sum m(0, 1, 2, 3, 4, 5, 6, 8, 12) = \prod M(7, 9, 10, 11, 13, 14, 15)$

10. **(3 pts.)** Determine the canonical SOP and POS expression for $F(A, B, C) = \prod M(0, 1, 4, 5)$
Hint, compose the truth table for F .

Solution

$$F(A, B, C) = A'B'C' + A'BC + ABC' + ABC$$

$$F(A, B, C) = (A+B+C)(A+B+C')(A'+B+C)(A'+B+C')$$

11. **(3 pts.)** Determine the canonical SOP and POS expression for $F(A, B, C, D) = \sum m(0, 4, 12, 15)$ Hint, write out the truth table for F .

Solution

$$F(A, B, C, D) = A'B'C'D' + A'BC'D' + ABC'D' + ABCD$$

$$F(A, B, C, D) = (A+B+C+D')(A+B+C'+D)(A+B+C'+D')(A+B'+C+D')(A+B'+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C'+D)(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C'+D)(A'+B'+C'+D)$$

12. **(4 pts.)** For the function $F(A, B, C) = BC + AB'C'$, draw a timing diagram for an input sequence that follows the same order as the rows of the truth table. Assume a propagation delay for NOT, AND and OR gate are all 10ns.

Solution *skipped for now*

13. **(4 pts.)** Complete the timing diagram in Figure 2.2 for the functions $F(A, B, C) = AB' + BC + ABC'$ and $G(A, B, C) = (A + B')C + (BC')'$

Solution

14. **(16 pts.)** Design a circuit to control the water pump of a washing machine. The pump will not pump water if

The lid is closed and the cycle is not fill

The cycle is fill and the detergent level is empty

The detergent is not empty and the lid is open

The variables for this problem are:

L = lid is closed

C = cycle is fill

D = detergent is empty

P = pump will pump water

Create a truth table which describes when the pump will not pump water. Call this output P'. Determine the canonical SOP expression for P'. Use this canonical SOP expression to generate a circuit diagram for P. This can be done by inserting an inverter onto the output of the circuit.

Take the P' column from truth table and invert all the entries to generate a new output column called P (because the negation of P' is P). Determine the canonical SOP realization for P using this new column.

15. **Lab** Design a hexadecimal-to-seven-segment display (hex2SevenSegment) digital circuit. The hex2SevenSegment circuit converts a 4-bit input that represents a hexadecimal digit to a 7-bit output that displays the hexadecimal digit on a 7-segment display as shown in

Figure 2.3. A 7-segment display is an figure-8 shaped arrangement of 7 LEDs that can be individually illuminated.









Each of the 7 LEDs is associated with the output from the hex2SevenSegment circuit as shown in Figure 2.4A. Active high LEDs illuminate when their input is logic 1 and turn-off when their input of logic 0. If the LEDs of a 7-segment display are active then a binary input of 1100110 would display the pattern shown in Figure 2.4B

Since there are many different ways to illuminate the 7 segments to form the characters 0 ... F, we will standardize our pattern to those shown in Figure 2.5.

The truth table for the hex2SevenSegment circuit is started below. Complete the truth table by filling the outputs for the seg column. Note that the number inside the square brackets is the bit index in the 7-bit output. The relationship between the bit index and the segments is shown in Figure 2.3.

x	seg[6]	seg[5]	seg[4]	seg[3]	seg[2]	seg[1]	seg[0]
0000							
0001							
0010							
0011							
0100	1	1	0	0	1	1	0
0101							
0110							
0111							
1000							
1001							
1010							
1011							
1100							
1101							
1110							
1111							

Now determine the SOP_{\min} expression for each of the 7 outputs.

        

 


Figure 2.2: The timing diagram for two functions, $F(A, B, C)$ and $G(A, B, C)$.

 
 


Figure 2.3: The connection between the 4-bit input and the 7-segment display.

 


Figure 2.4: A) The individual segments of a 7-segment display and their bit position in the 7-bit output from the `he2SevenSegment` circuit. b) The illumination patten for the digit “4”

 


Figure 2.5: The illuminated patterns for all 16 inputs.

3.0 Exercises

1. (6 pts.) Design a circuit called DECODE. DECODE has two bits of input S, D and two bit of output $y_1 y_0$. If $S = 0$ then $y_0 = D$ and $y_1 = 0$ else if $S = 1$ then $y_0 = 0$ and $y_1 = D$.

a) Write down the truth table for the DECODE function.

Solution	S	D	y_1	y_0
	0	0	0	0
	0	1	0	1
	1	0	0	0
	1	1	1	0

b) Determine the SOP_{\min} realization for DECODE.

Solution $y_0 = S'D$
 $y_1 = SD$

2. (6 pts.) Design a circuit called FULLADD. FULLADD has three bits of input a, b, c and two bits of output $s_1 s_0$. The output represents the sum of the three bits.

a) Write down the truth table for the FULLADD function.

Solution	a	b	c	s_1	s_0
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	0
	0	1	1	1	1
	1	0	0	0	0
	1	0	1	1	1
	1	1	0	1	0
	1	1	1	1	1

b) Determine the SOP_{\min} realization for FULLADD.

Solution $s_1 = ab + ac + bc$
 $s_0 = a'b'c + a'bc' + ab'c' + abc$


3. (4 pts.) Determine SOP_{\min} expression for the following circuit and draw the circuit using the fewest number of gates possible.

Solution From the circuit we have: $F(A, B, C, D) = A'B'C'D' + A'C'D + AC'D + A'B'C$

$AB \backslash CD$	00	01	11	10
00	1	1	1	1
01		1		
11		1		
10		1		

From this it follows that $F(A, B, C, D) = A'B' + C'D$

 4. (8 pts.) Design a digital system with four bits of inputs $I_3 I_2 I_1 I_0$ and two bits of outputs $O_1 O_0$. At least one of the inputs is always equal to 1. The output encodes the index of the most significant 1 in the input. For example, if $I_3 I_2 I_1 I_0 = 0101$, then the index of the most significant 1 is 2, hence $O_1 O_0 = 10$. Submit:



- ### Solution

I_3	I_2	I_1	I_0	O_1	O_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

- ### Solution

$I3I2 \setminus I1I0$	00	01	11	10
00	x			
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$O_1 = I_3 + I_2$$

$$O_1 = I_3 + I_2$$

$I3I2\backslash I1I0$	00	01	11	10
00	x		1	1
01				
11	1	1	1	1
10	1	1	1	1

$$O_0 = I_3 + I_2' I_1$$

$$O_0 = I_3 + I_2' I_1$$

- Truth tables.

	a_3	a_2	a_1	a_0	f_3	f_2	f_1	f_0
	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
	0	0	1	0	0	0	1	1
	0	0	1	1	0	0	1	0
	0	1	0	0	0	1	1	0
	0	1	0	1	0	1	1	1
	0	1	1	0	0	1	0	1
Solution	0	1	1	1	0	1	0	0
	1	0	0	0	1	1	0	0
	1	0	0	1	1	1	0	1
	1	0	1	0	1	1	1	1
	1	0	1	1	1	1	1	0
	1	1	0	0	1	0	1	0
	1	1	0	1	1	0	1	1
	1	1	1	0	1	0	0	1
	1	1	1	1	1	0	0	0

- Four k-maps for the converter.

	$a_3a_2 \backslash a_1a_0$	00	01	11	10		$a_3a_2 \backslash a_1a_0$	00	01	11	10
	00						00				
Solution	01						01	1	1	1	1
	11	1	1	1	1		11				
	10	1	1	1	1		10	1	1	1	1
	$f_3 = a_3$						$f_2 = a_3a'_2 + a'_3a_2$				
	$a_3a_2 \backslash a_1a_0$	00	01	11	10		$a_3a_2 \backslash a_1a_0$	00	01	11	10
	00			1	1		00		1		1
Solution	01	1	1				01		1		1
	11	1	1				11		1		1
	10			1	1		10		1		1
	$f_1 = a_2a'_1 + a'_2a_1$						$f_0 = a'_1a_0 + a_1a'_0$				

- SOP_{min} expression for the outputs, no product sharing please (use the -Dso command line option).
- Espresso file for the converter
- Espresso output in PLA format
- Compare the number of gates required in your solution versus the number of gates required by Espresso.

7. (4 pts. each) Determine SOP_{min} expression for:

a) $F(A, B, C) = \sum m(0, 1, 3, 4, 5)$

	$A \backslash BC$	00	01	11	10
Solution	0	1	1	1	
	1	1	1		

$$F(A, B, C) = B' + A'C$$

b) $F(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$

$AB \backslash CD$	00	01	11	10
00		1		
01		1	1	1
11	1	1	1	
10			1	

Solution

$$F(A,B,C) = ABC' + A'C'D + ACD + A'BC$$

c) $F(A,B,C,D) = \sum m(0, 2, 5, 6, 8, 11, 12, 13, 14, 15)$

$AB \backslash CD$	00	01	11	10
00	1			1
01		1		1
11	1	1	1	1
10	1		1	

Solution

$$F(A,B,C,D) = AB + BC'D + ACD + B'C'D' + A'CD'$$

d) $F(A,B,C,D,E) = \sum m(0, 8, 9, 10, 13, 15, 22, 26, 29, 30, 31)$

$BC \backslash DE$	00	01	11	10
00	1			
01				
11		1	1	
10	1	1		1

$A=0$

$BC \backslash DE$	00	01	11	10
00				
01				1
11		1	1	1
10				1

$A=1$

$$F(A,B,C,D,E) = BCE + A'C'D'E' + BC'DE + ACDE' + A'BD'E \text{ or}$$

$$F(A,B,C,D,E) = BCE + A'C'D'E' + BC'DE + ACDE' + A'BC'D'$$

e) $F(A,B,C,D,E) = \sum m(0, 2, 4, 5, 7, 10, 13, 15, 18, 21, 24, 26, 28, 29)$

$BC \backslash DE$	00	01	11	10
00	1			1
01	1	1	1	
11		1	1	
10				1

$A=0$

$BC \backslash DE$	00	01	11	10
00				1
01		1		
11	1	1		
10	1			1

$A=1$

$$F(A,B,C,D,E) = A'B'D'E' + CD'E + C'DE' + ABD'E' + A'CE$$

8. (4 pts. each) Determine SOP_{min} expression for:

a) $F(A,B,C,D) = \sum m(4, 7, 9, 12, 13, 15) + \sum d(0, 1, 2, 3, 10, 14)$

$AB \backslash CD$	00	01	11	10
00	x	x	x	
01	1		1	
11	1	1	1	x
10		1		x

Solution

$$F(A,B,C,D) = BC'D' + AC'D + BCD$$

b) $F(A,B,C,D) = \sum m(0, 1, 5, 7, 10, 14, 15) + \sum d(2, 8)$

$AB \backslash CD$	00	01	11	10
00	1	1		x
01		1	1	
11			1	1
10	x			1

Solution

$$F(A,B,C,D) = B'D' + A'C'D + BCD + ABC$$

c) $F(A, B, C, D) = \sum m(0, 1, 3, 4, 15) + \sum d(10, 12)$

Solution

$AB \backslash CD$	00	01	11	10
00	1	1	1	
01	1			
11	x		1	
10				x

$$F(A, B, C, D) = ABCD + A'C'D' + A'B'D$$

d) $F(A, B, C, D, E) = \sum m(2, 3, 5, 7, 11, 13, 17, 19, 29, 31) + \sum d(1, 4, 9, 16, 25)$

Solution

$BC \backslash DE$	00	01	11	10
00		x	1	1
01	x	1	1	
11		1		
10		x	1	

$A=0$

$BC \backslash DE$	00	01	11	10
00	x	1	1	
01				
11		1	1	
10		x		

$A=1$

$$F(A, B, C, D, E) = A'D'E + A'C'E + A'B'C'D + B'C'E + ABCE + A'B'E$$

e) $F(A, B, C, D, E) = \sum m(2, 3, 6, 10, 12, 13, 14, 18, 25, 26, 28, 29) + \sum d(11, 27)$

Solution

$BC \backslash DE$	00	01	11	10
00			1	1
01				1
11	1	1		1
10			x	1

$A=0$

$BC \backslash DE$	00	01	11	10
00				1
01				
11	1	1		
10		1	x	1

$A=1$

$$F(A, B, C, D, E) = A'C'D + C'DE' + A'DE' + BCD' + ABC'E$$

9. (8 pts. each) Determine SOP_{min} and POS_{min} expressions for:

a) $F(A, B, C, D) = \sum m(0, 1, 2, 5, 8, 10, 13, 15)$

Solution

$AB \backslash CD$	00	01	11	10
00	1	1		1
01		1		
11		1	1	
10	1			1

F

$AB \backslash CD$	00	01	11	10
00			1	
01	1		1	1
11	1			1
10		1	1	

F'

$$SOP_{min} F(A, B, C, D) = B'D' + A'C'D + ABD$$

$$POS_{min} F(A, B, C, D) = (B' + D)(A + C' + D')(A' + B + D')$$

b) $F(A, B, C, D) = \prod M(0, 4, 6, 10, 11, 12)$

Solution

$AB \backslash CD$	00	01	11	10
00		1	1	1
01		1	1	
11		1	1	1
10	1	1		

F

$AB \backslash CD$	00	01	11	10
00	1			
01	1			1
11	1			
10			1	1

F'

$$SOP_{min} F(A, B, C, D) = AB'C' + A'B'C + ABC + C'D + A'D \text{ or}$$

$$\begin{aligned}
SOP_{min} F(A,B,C,D) &= AB'C' + A'B'C + ABC + C'D + BD \text{ or} \\
SOP_{min} F(A,B,C,D) &= AB'C' + A'B'C + ABC + A'D + BD \\
POS_{min} F(A,B,C,D) &= (A+C+D)(B'+C+D)(A+B'+D)(A'+B+C')
\end{aligned}$$

c) $F(A,B,C,D) = \sum m(0,5,7,10,11,14) + \sum d(3,12,15)$

Solution

$AB \backslash CD$	00	01	11	10
00	1		x	
01		1	1	
11	x		x	1
10			1	1

F

$AB \backslash CD$	00	01	11	10
00		1	x	1
01	1			1
11	x	1	x	
10	1	1		

F'

$$\begin{aligned}
SOP_{min} F(A,B,C,D) &= A'B'C'D' + A'BD + AC \\
POS_{min} F(A,B,C,D) &= (A'+C)(A+C'+D)(A+B+D')(B'+C+D) \text{ or} \\
POS_{min} F(A,B,C,D) &= (A'+C)(A+C'+D)(B+C+D')(B'+C+D) \text{ or} \\
POS_{min} F(A,B,C,D) &= (A'+C)(A+C'+D)(A+B+D')(A+B'+D) \text{ or} \\
POS_{min} F(A,B,C,D) &= (A'+C)(A+C'+D)(B+C+D')(A+B'+D)
\end{aligned}$$

d) $F(A,B,C,D) = \prod M(2,6,7,9,15) * \prod d(4,12,13)$

Solution

$AB \backslash CD$	00	01	11	10
00	1	1	1	
01	x	1		
11	x	x		1
10	1		1	1

F

$AB \backslash CD$	00	01	11	10
00				1
01	x		1	1
11	x	x	1	
10		1		

F'

$$\begin{aligned}
SOP_{min} F(A,B,C,D) &= A'C' + AD' + A'CD \\
POS_{min} F(A,B,C,D) &= (A+C'+D)(B'+C'+D')(A'+C+D')
\end{aligned}$$

e) $F(W,X,Y,Z) = WX'Z' + X'YZ + W'Y'Z + XYZ + WXY'$

Solution

$WX \backslash YZ$	00	01	11	10
00		1	1	
01		1	1	
11	1	1	1	
10	1		1	1

F

$WX \backslash YZ$	00	01	11	10
00	1			1
01	1			1
11				1
10		1		

F'

$$\begin{aligned}
SOP_{min} F(W,X,Y,Z) &= W'Z + XZ + WY'Z' + WX'Y \\
POS_{min} F(W,X,Y,Z) &= (W+Z)(X'+Y'+Z)(W'+X+Y+Z')
\end{aligned}$$

f) $F(W,X,Y,Z) = (W + X' + Y')(W' + Z')(W + Y')$

Solution

We have that $F'(W,X,Y,Z) = W'XY + WZ + W'Y'$

$WX \backslash YZ$	00	01	11	10
00			1	1
01			1	1
11		1	1	
10		1	1	

F'

$WX \backslash YZ$	00	01	11	10
00	1	1		
01	1	1		
11	1			1
10	1			1

F

$$\begin{aligned}
SOP_{min} F(W,X,Y,Z) &= W'Y' + WZ' \\
POS_{min} F(W,X,Y,Z) &= (W'+Z')(W+Y')
\end{aligned}$$

Hint, the negation of a “Don’t care” is a “Don’t care”.

10. **(3 pts.)** While grading homework for a digital design class the following question/answer pair is encountered. What is the problem with the answer given?

Question: Generate the POS_{\min} expression for $F(A, B, C) = \sum m(2, 3, 4, 5)$

Answer: $F(A, B, C) = (A + B')(A' + B)$

11. **(6 pts.)** Determine the SOP_{\min} realization of the following function.

A	B	C	D	F(A,B,C,D)
x	1	1	x	0
0	x	0	1	0
x	x	0	0	x
x	0	1	x	1
1	x	0	1	1

$AB \setminus BC$	00	01	11	10
00	x	0	1	1
01	x	0	0	0
11	x	1	0	0
10	x	1	1	1

$$F(A, B, C) = AC' + B'C$$

12. **(6 pts.)** What is the worst function SOP_{\min} of 3 variable that can be created? That is, define a function whose minimal SOP form has the largest possible number of product terms. What is the largest number of product terms that a 4-variable SOP_{\min} expression can have? How about N variables?

Solution The worst function of three variable is shown in the Kmap below:

$A \setminus BC$	00	01	11	10
0	1		1	
1		1		1

This function requires four product terms. Any additional minterm added to this Kmap would create a grouping with neighboring minterms, perhaps not decreasing the the number of product terms, but certainly making the product terms simpler. Its important to note that this configuration looks like a checkerboard. The worst function of four variables looks like:

$AB \setminus BC$	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

This function requires 8 product terms, each containing every variable. Boy that's one bad realization. In a general, the worst realization of an N variable function requires 2^{N-1} product terms. This is because the checkerboard configuration can be applied to any Kmap, with half of the cells containing 1's. Since a function with N variables has 2^N cells, then $1/2$ of these cells works out to 2^{N-1} .

13. **(16 pts.)** Sometimes a logic circuit needs to output a logic 0 in order to produce some behavior. For example, an LED can be attached to a digital circuit output so that it

lights up when the circuit outputs a 0. This response is called an active low output; the output device is *active* then the digital output is *low*.

Build a digital circuit that takes as input two 2-bit numbers, A and B. The circuit has three outputs which drive three LEDs labeled G, L, and E. The G LED should be illuminated when $A > B$. The L LED should be illuminated when $A < B$. The E LED should be illuminated when $A = B$. The LEDs are illuminated when the circuit outputs a 0, otherwise they are turned off.

Determine SOP_{min} expression for the G, L and E outputs. Determine POS_{min} expression for the G, L and E outputs.

4.0 Exercises

1. (2 pts. each) Short answer:

- a) How many 3:8 decoders would it take to build a 9:512 decoder?

Solutions A total of 73 decoders are required. There are $512/8 = 64$ on the output layer, $64/8 = 8$ in the middle layer and 1 on the input.

- b) How many AND gates are there in a $2^N:1$ mux?

Solutions Each input requires 1 AND gate, hence 2^N AND gates.

- c) How many AND gates are there in a $2^N : 1$ mux which is constructed out of 2:1 muxes?

Solutions A 2^N Mux requires the following number of 2:1 muxes:

$$\begin{aligned} 2^N/2 + 2^N/4 + \dots + 2^N/2^N &= \\ 2^N(1/2 + 1/4 + \dots + 1/2^N) &= \\ 2^N(1 - 1/2^{(N+1)}) &= \\ 2^N - 1 \end{aligned}$$

Since each 2:1 mux contains 2 AND gates, the total number of AND gates is $2^N(N+1) - 2$.

- d) How many AND gates are there in a $2^N:1$ mux which is constructed out of $2^L:1$ muxes, assume that 2^N is an integer multiple of 2^L ?

Solutions A 2^N Mux requires the following number of $2^L : 1$ muxes:

$$\begin{aligned} 2^N/2^L + 2^N/2^{(2L)} + \dots 2^N/2^{(kL)} \\ 2^N(1/2^L + 1/2^{(2L)} + \dots 1/2^{(kL)}) \end{aligned}$$

Where $k = N/L$. Each $2^L : 1$ mux requires 2^L AND gates for its construction, so the number of AND gates is the product of the number of $2^L : 1$ muxes and the number of AND gates in a single $2^L : 1$ mux, or:

$$\begin{aligned} 2^N * 2^L(1/2^L + 1/2^{(2L)} + \dots 1/2^{(kL)}) \\ 2^N(1 + 1/2 + \dots 1/2^k) \\ 2^N(2 - 1/2^{(k+1)}) \\ 2^N(2 - 1/2^{(N/L+1)}) \\ 2^{(N+1)} - 2^{(N - N/L - 1)} \end{aligned}$$

2. (6 pts.) Determine the SOP_{min} expression for each of the three outputs of a bit-slice of the comparator.

Solutions The following five variable Kmap describes E_{out}

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	x	x	x	x
01	0	0	0	0
11	x	x	x	x
10	0	0	0	0

$E_{in} = 0$

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	1	0	1	0
01	x	x	x	x
11	x	x	x	x
10	x	x	x	x

$E_{in} = 1$

$$E_{out} = L'_{in}G'_{in}x'y' + L'_{in}G'_{in}xy$$

The following five variable Kmap describes G_{out}

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	x	x	x	x
01	1	1	1	1
11	x	x	x	x
10	0	0	0	0

$E_{in} = 0$

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	0	0	0	1
01	x	x	x	x
11	x	x	x	x
10	x	x	x	x

$E_{in} = 1$

$$G_{out} = G_{in} + L'_{in}xy'$$

The following five variable Kmap describes L_{out}

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	x	x	x	x
01	0	0	0	0
11	x	x	x	x
10	1	1	1	1

$E_{in} = 0$

$L_{in}G_{in} \backslash xy$	00	01	11	10
00	0	1	0	0
01	x	x	x	x
11	x	x	x	x
10	x	x	x	x

$E_{in} = 1$

$$L_{out} = L_{in} + G'_{in}x'y$$

3. (2 pts.) Show how to connect together four 4-bit comparators to construct a 16-bit comparator.

Solutions *Figure forthcoming*

4. (2 pts.) Determine the circuitry for the overflow detection circuit for a 2's-complement adder subtractor. See page ??.

Solutions

$c_{in} \backslash c_{out}$	0	1
0		1
1		1

$$\text{Thus } ovf = c'_{in}c_{out} + c_{in}c'_{out} = c_{in} \oplus c_{out}$$

5. (10 pts.) Build a BCD to 7-Segment Display converter using Espresso.

Building Block: BCD to 7-segment

Nomenclature:	BCD to 7-segment converter
Data Input:	4-bit vector $D = d_3d_2d_1d_0$
Data Output:	7-bit vector $Y = y_6 \dots y_1y_0$
Control:	none
Status:	none
Behavior:	The output drives a 7-segment display pattern representing the BCD digit.

A binary coded digit (BCD) is a 4-bit binary number that is constrained to assume the values of 0-9. That is, 1010 ... 1111 are illegal BCD digits.

A 7-segment display is a box with seven inputs and seven output LED bars. Each input is wired to an LED bar that is illuminated when a 1 is applied to its input. Each of the seven LED segments is numbered according to the pattern shown on the left-hand side of Figure 4.6.

 


Figure 4.6: The numbering of the segments in a 7-segment display. The patterns of the BCD digits.

The pattern of LEDs to illuminate for each BCD digit is shown on the right-hand side of Figure 4.6. A BCD to 7-segment converter has four inputs, $d_3d_2d_1d_0$ and seven outputs $S_7 \dots S_1$. Complete the design using Espresso. Make sure to include “Don’t cares” in the truth table specification.

- a) Use Espresso to determine the SOP_{\min} expression for the outputs $S_7 \dots S_1$. Underline product terms that are shared. Submit the Espresso source file.

Solutions *The following is the source file for the BCD to 7-segment converter.*

The following is the output from espresso on the BCD to 7-segment converter.

- b) Use Espresso to determine the POS_{\min} expression for the outputs $S_7 \dots S_1$. Underline sum terms that are shared. Submit the Espresso source file **Solutions** *The following output was generated by using the same file as the solution in the previous part; but using the epos option in espresso.*

Remember that these are the negation of the output variables, hence we have to use DeMorgan’s to put them into POS_{\min} form. Symbolically we have: $s_7 = (b_3 + b_2 + b_1 + b_0')(b_2' +$

$$s_6 = (b_2 + b_1' + b_0);$$

$$s_5 = (b_2' + b_1 + b_0')(b_3 + b_2 + b_1 + b_0')(b_2 + b_1 + b_0')(b_2' + b_1 + b_0)(b_3' + b_0')(b_2' + b_1' + b_0');$$

$$s_4 = (b_3 + b_2 + b_1)(b_2' + b_1' + b_0');$$

$$s_3 = (b_2' + b_1' + b_0)(b_2' + b_1 + b_0');$$

$$s_2 = (b_2 + b_1' + b_0)(b_3 + b_2 + b_1 + b_0')(b_2 + b_1' + b_0');$$

$$s_1 = (b_3 + b_2 + b_1 + b_0')(b_2' + b_1 + b_0);$$

6. **(10 pts.)** Build a box which has one 4-bit input called A and one 4-bit output called T. The output T is the 2’s-complement value of the input A. Use the bit slice paradigm to solve this problem. That is, create a building block for one bit of the problem then string four of them together to solve the problem. For the problem at hand this can be done as follows:

- Start at the LSB of A.
- If this is the first, least significant, 1, flip all bits to the left.
- If this is not the first 1, leave the bit alone.
- Move one bit to the left.
- Goto Step b.

A bit-slice should communicate whether there has been a 1 to the right, to the more significant bit. Submit:

A	c_{in}	T	c_{out}	comment
0	0	0	0	There is no 1 to the right
0	1	1	1	There is a 1 to the right, flip A
1	0	1	1	There is no 1 to the right, but we've created one
1	1	0	1	There is a 1 to the right, flip A

- How the above "algorithm" behaves when presented with the inputs $A=1100$
- The truth table for one bit slice
- SOP_{min} expression and circuit diagram for a bit slice.
- The organization of four bit slices to solve the problem

Solutions The key to the begin solution is to figure out the structure of the begin solution and then give meaning to the signals involved. The problem will be sliced into four bit-slices; each handled but its own complement box. Thus, there will be four complement box in the begin solution. Each box will have 2 inputs, one being a bit of A and the other being a "carry in" from the less significant less, immediately to the right. Each box will have two bits of output, a bit of T and a "carry out". The carry bits (both into and out of a box will convey information regarding the rightmost 1 in the number A .

If the carry in is equal 1 then there is a one to the right. If the carry in is equal 0 then there is not a one to the right. The truth table for a box is then


From this it follows that:

$$T = A'c_{in} + Ac'_{in} = A \oplus c_{in}$$

$$c_{out} = A + c_{in}$$


7. (4 pts.) Build a 7:128 decoder using a minimum number of 4:16, 2:4 and 1:2 decoders. Describe the wiring of the select lines. **Solutions**
8. (4 pts. each) Design a circuit with two 8-bit inputs X, Y , an 8-bit output Z and a 1-bit input sel . Construct a circuit that yields the correct value of Z using only the basic building blocks presented in this chapter; do NOT show the internal organization of these building blocks. If a mux is used, denote which input is the y_0 and which is y_1 . If a comparator is used denote which input is X and which is Y . Do not use any AND or OR gates; it will tempting in the later problems.

 - a) if ($sel==0$) then $Z = X$ else $Z = Y$




Solutions

 - b) if ($sel==0$) then $Z = X+Y$ else $Z = Y$




Solutions

 c) if ($\text{sel}==0$) then $Z = X+Y$ else $Z = X-Y$




Solutions

d) if ($X==0$) then $Z = X$ else $Z = Y$

 


Solutions

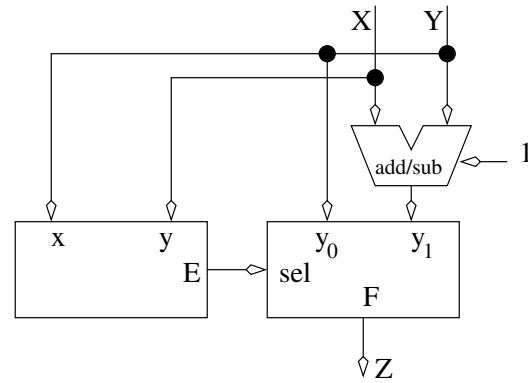e) if ($X==Y$) then $Z = X-Y$ else $Z = Y$




Solutions

 
f) if ($X==Y$) then $Z = X+Y$ else $Z = X-Y$



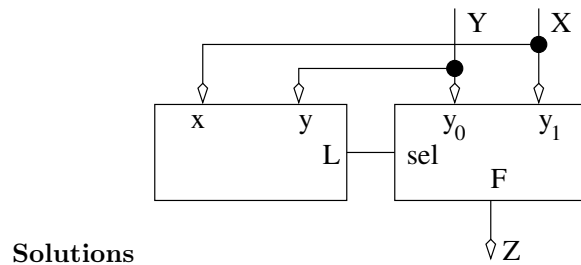
g) if $(X < Y)$ then $Z = X$ else $Z = Y$



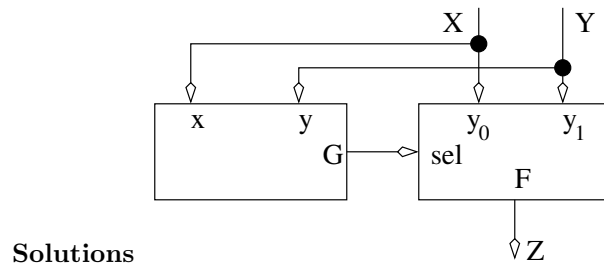
h) if $(X \leq Y)$ then $Z = X$ else $Z = Y$



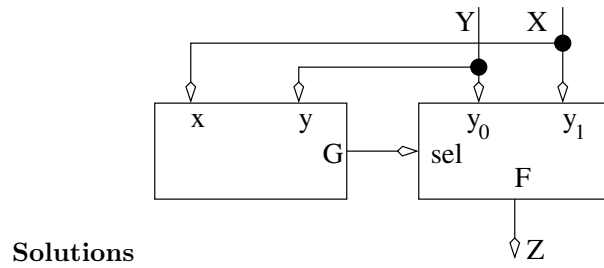i) if $(X > Y)$ then $Z = X$ else $Z = Y$



 j) if $(X > Y)$ then $Z = X+X$ else $Z = Y+Y$



Solutions

9. (10 pts.) Build a 4-bit priority encoder.

Building Block: Priority Encoder

Nomenclature:	N-bit priority encoder
Data Input:	N-bit vectored $D = d_{N-1} \dots d_1 d_0$
Data Output:	$\log_2(N)$ -bit vector $Y = y_{\log_2(N)} \dots y_1 y_0$
Control:	none
Status:	none
Behavior:	$F = i$ where i is the highest indexed input which equals 1. When all inputs equal 0, the output is a “don’t care”.

The idea is for the outputs to represent (in binary code) the highest input index which equals 1. For example, a 4-bit priority encoder with input $D = 1010$ has inputs $d_3 = 1$ and $d_0 = 1$. Of these two inputs, the index of d_3 is greater than the index of d_0 so the output, F is equal to 3, or in binary 11. If the input were $D = 0111$ then $F = 10$.

- a) Write down the truth table for a 4-bit priority encoder. Hint, the truth table could be structured so that it contains only five rows by using “don’t cares” on the inputs.

d_3	d_2	d_1	d_0	f_1	F_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	x	0	1
0	1	x	x	1	0
1	x	x	x	1	1

Solutions

- b) An SOP_{min} realization of the circuit. **Solutions** $f_1 = d_3 + d_2$
 $f_0 = d_3 + d'_2 d_1$


10. (10 pts.) Build a 4-bit saturation adder. A saturation adder performs normal 4-bit addition when the resulting sum is less than 15. If the sum is greater than 15, the saturation adder outputs 15. The following table summarizes.

Building Block: Saturation Adder

Nomenclature:	4-bit saturation adder
Data Input:	2, 4-bit vectors A, B
Data Output:	4-bit vector sum
Control:	none
Status:	none
Behavior:	<pre> if (A+B > 15) sum = 15 else sum = A+B </pre>

Submit a schematic showing the basic building blocks, their data status, and control interconnections. Show any truth tables used to build glue logic.

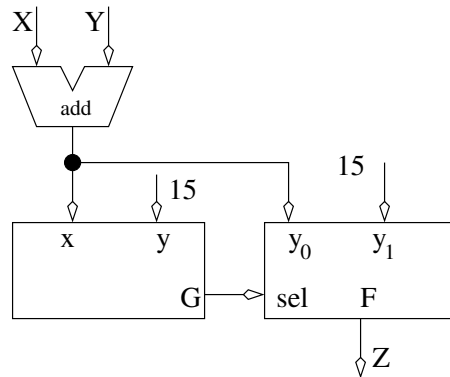Solutions All we need to do is to determine when the sum is greater than 15 and output 15 when it is. The comparator/mux combo mentioned several times in the chapter should do the trick.



11. (10 pts.) Build a mod-6 adder. The mod-6 adder takes as input two 3-bit (mod 6) numbers and adds them together modulus 6.


Modular arithmetic only operates with a limited portion of the integers. The range of numbers is $\{0, 1, 2, \dots, m-1\}$ where m is called the *modulus*; note there are m different integers because counting started at 0. For example, when working in mod-6 arithmetic use the integers $\{0, 1, 2, 3, 4, 5\}$. To solve any addition problem in modular arithmetic, it is only necessary to perform regular addition with the special rule that the addition process rolls over from the largest number, $m-1$ to 0 when the result is larger than $m-1$. For example, in mod-6 arithmetic $(5+1) \bmod 6 = 0$. The statement “ mod 6” is always included in the addition problem to indicate to the reader that mod-6 arithmetic is being performed. Here are a few more examples to help

$$\begin{aligned}
 2 + 3 & \bmod 6 = 5 \\
 3 + 3 & \bmod 6 = 0 \\
 4 + 3 & \bmod 6 = 1 \\
 5 + 5 & \bmod 6 = 4
 \end{aligned}$$

Nomenclature:	3-bit mod 6 adder
Data Input:	two, 3-bit (mod-6) vectors A , B
Data Output:	3-bit (mod-6) vector sum
Control:	none
Status:	none
Behavior:	$\text{sum} = A+B \bmod 6$

Submit a schematic showing the basic building blocks, their data status, and control interconnections. Show any truth tables used to build glue logic. Be careful that the word size of the result is handled correctly.

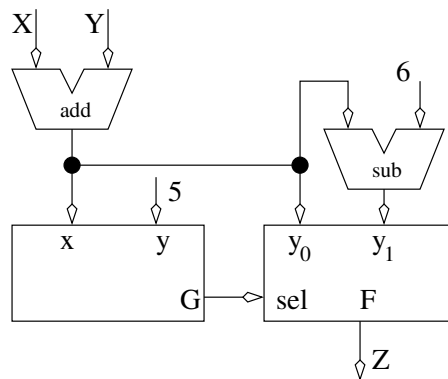Solutions Since the inputs are mod 6 numbers then the inputs can be in the range $[0-5]$. Adding two such values will yield a value in the range $[0-10]$. Hence a simple adjustment of the sum when its larger than 5 is required.



12. (1pt. each) Convert the following to 2's-complement assuming a word size of eight bits.

a) -35

Solutions $35 = 32 + 2 + 1 = 100011 = 00100011$, thus $-35 = 11011101$

b) -128

Solutions This is a special case, see page 10 for more information. $-128 = 10000000$

c) 67

Solutions $67 = 64 + 2 + 1 = 1000011 = 01000011$

d) 128

Solutions There are not enough bits to represent this positive number; hence the 8-bit representation does not exist.

13. (1 pt. each) Perform the following operations for the given 2's-complement numbers. Assume a word size of eight bits in all cases. Indicate where overflow occurs. If there is no overflow, convert the result to decimal.

a) $01011101 + 00110111$

Solutions $01011101 + 00110111 = 10010100$ overflow

Key	scancode	Key	scancode	Key	scancode	Key	scancode
0	45 ₁₆	1	16 ₁₆	2	1E ₁₆	3	26 ₁₆
4	25 ₁₆	5	2E ₁₆	6	36 ₁₆	7	3D ₁₆
8	3E ₁₆	9	46 ₁₆	A	1C ₁₆	B	32 ₁₆
C	21 ₁₆	D	23 ₁₆	E	24 ₁₆	F	2B ₁₆
P	4D ₁₆	L	4B ₁₆	M	3A ₁₆	I	43 ₁₆

Table 4.1: Some keyboard scancodes.

b) $11101011 + 11110001$

Solutions $11101011 + 11110001 = 11011100$

c) $01011101 + 10101011$

Solutions $01011101 + 10101011 = 00001000$

d) $10111011 - 11110001$

Solutions $10111011 - 11110001 =$
 $10111011 + 00001111 = 11001010$

e) $01011101 - 00110111$

Solutions $01011101 - 00110111 =$
 $01011101 + 11001001 = 00100110$

f) $01011101 - 10101111$

Solutions $01011101 - 10101111 =$
 $01011101 + 01010001 = 10101110$, *overflow*

14. **(10 pts.)** Build a flip box. A flip box is defined by the following input, output, and behavior definition.

Nomenclature:	8-bit flip box.
Data Input:	8-bit $D = d_7 \dots d_0$
Data Output:	8-bit $F = f_7 \dots f_0$
Control:	3-bit $S = s_2 s_1 s_0$
Status:	none
Behavior:	The output is the same as the input except for one bit which is inverted. The index of the inverted bit is given by S .

The flip box takes the 8-bit data input, flips a single bit identified by S , then sends the new 8-bit value to the output. For example, if $D = 11110000$ and $S = 010$ then $F = 11110100$. If $D = 11110000$ and $S = 101$ then $F = 11010000$. The solution should rely heavily on the basic building blocks.

Solutions Arrange 8, 2:1 muxes with d_i and d'_i going into the data inputs. Run the select into a 3:8 decoder and route the data outputs to the individual selects of the 2:1 muxes.


15. **(10 pts.)** Build a box which recognizes some keyboard scancode. When a key is pressed on a keyboard, the keyboard transmits (among other things) an 8-bit scancode of the pressed key. Each key has its own scancode listed in Table 4.1. The relationship between the keys and their scancode is not based on ASCII.

Nomenclature:	scancode classifier
Data Input:	8-bit $D = d_7 \dots d_0$
Data Output:	IsP, IsL, IsM, IsI, IsS
Control:	none
Status:	none
Behavior:	IsP = 1 when D is the scan code for the letter "P". IsL = 1 when D is the scan code for the letter "L". IsM = 1 when D is the scan code for the letter "M". IsI = 1 when D is the scan code for the letter "I". IsS = 1 when D is the scan code for the letter "S".

16. **(10 pts.)** Build a box which converts an 8-bit scancode for a hexadecimal digit into a 4-bit hexadecimal values.

Nomenclature:	scancode classifier
Data Input:	8-bit $D = d_7 \dots d_0$
Data Output:	4-bit $H = h_3h_2h_1h_0$
Control:	none
Status:	none
Behavior:	Converts the scancode D , representing a the key of a hexadecimal character, into its 4-bit value H .

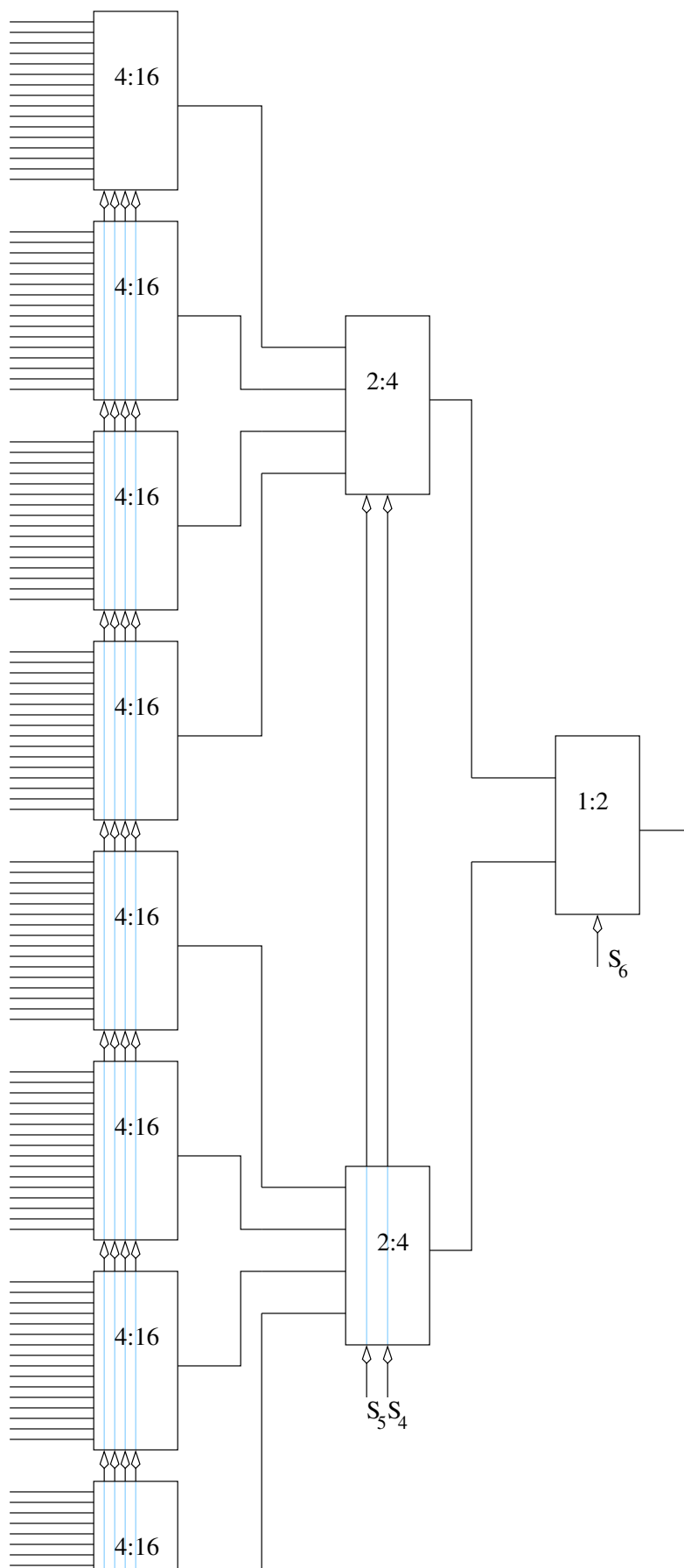For example, if $D = 25_{16}$, the scancode for the "4" key, then the converter should output $H = 0100_2$. Assume that the inputs are always legal hexadecimal scancodes.



5.0 Exercises

1. (8 pts.) Determine the state table for the circuit in Figure 5.8.

 


Figure 5.8

Solution The analysis of the cross-coupled NANDs show in Figure ?? is almost exactly the same as that for the cross coupled NORs. Start with the truth table for an NAND gate:

a	b	$(ab)'$
0	0	1
0	1	1
1	0	1
1	1	0

Observe that the output is 1 whenever either input is 0. Now onto the state table for the cross coupled NANDs:

A	B	F^+	G^+
0	0	1	1
0	1	1	0
1	0	0	1
1	1	F	G

For the cross coupled NANDs the output holds when the input $A, B = 1, 1$ occurs. In fact if you compare this table to that of the cross coupled NORs, you will notice that $A, B = S', R'$ and $F, G = Q, Q'$.

2. (8 pts.) Determine the state table for the circuit in Figure 5.9. Which basic memory element does it act like? Hint, one of the inputs is acting like a clock. Additional hint, in order to simplify the analysis, replace a portion of the circuit with a component from this chapter.

 


Figure 5.9

Solution The main idea in this problem is to simplify the cross coupled NOR gates into an SR latch. Then use the state table for the SR latch. This substitution will simplify the analysis of this circuit. Since the lower NOR gate is denoted A, call the lower input of the SR latch R and the upper input S (see Figure 5.6).

This yields the following truth table:

A	B	S	R	comment	Q^+
0	0	0	0	Hold	Q
0	1	0	0	Hold	Q
1	0	0	1	Reset	0
1	1	1	0	Set	1

It is behaving exactly like a D clocked latch, where $A = \text{clk}$ and $B = D$.

3. (8 pts.) Complete the timing diagram for the circuit shown in Figure 5.10. Which basic memory element does this circuit act like?

 


Figure 5.10: A 2-stage sequential circuit.

4. (15 pts.) Complete the timing diagram for the basic memory elements in Figure 5.11. The clock cycle is 20 ns. When necessary, assume that Q is initialized to 0 and the output settles to 0 after a period of rapid toggling.

Solution

5. (15 pts.) Complete the timing diagram for the basic memory elements in Figure 5.12. The clock cycle is 20 ns. When necessary, assume that Q is initialized to 0 and the output settles to 0 after a period of rapid toggling.

Solution

6. (4 pts.) Consider the furnace controller discussed at the beginning of this chapter. Determine which state the controller should transition into when in a particular state and given a particular combination of inputs. Fill in the eight entries in the following table with the next state the system should move into. The next state should be either ON if the system should transition (or remain in) the ON state, OFF if the system should transition (or remain in) the OFF state, or X if the input combination is meaningless.


 


Figure 5.11: A variety of basic memory elements and the signals applied to them.

 

7. **(8 pts.)** Derive the next state equations for each type (D, T, SR, and JK) of basic memory element. The next state equation is a symbolic equation describing the next state (Q^+) as a function of the inputs (D,T,SR, or JK) and state (Q). In order to determine the next state equations for a JK memory element, build a 3-variable Kmap with Q , J , and K as the inputs. The entries in the Kmap should be Q^+ . Solving this Kmap will yield the next state equation. Show all work for full credit.
8. **(16 pts.)** Derive the transition list for each type (D, T, JK, and SR) of basic memory element. A transition list describes the input(s) necessary to elicit a particular change in state. For example, imagine that a D flip flop output is currently in the 0 state and it needs to transition to the 1 state after the clock edge. In other words, $Q = 0$ and $Q^+ = 1$. What input would have to be provided on the D input to make this happen?


 
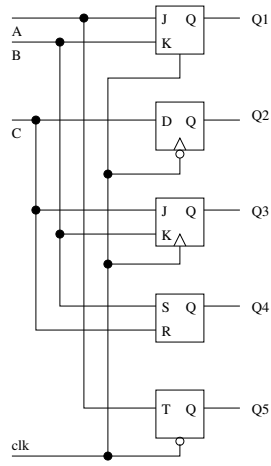
 


Figure 5.12

 

Clearly, $D = 1$. This entry is filled in Table 5.2.

Hint, the Kmaps used to determine the next state equations will help in visualizing all the conditions which elicit a particular change of input. Complete the transition list for all four memory types. For full credit, show how the entries in the transition list are determined.

$Q \rightarrow Q^+$	D	$Q \rightarrow Q^+$	T	$Q \rightarrow Q^+$	J	K	$Q \rightarrow Q^+$	S	R
$0 \rightarrow 0$		$0 \rightarrow 0$		$0 \rightarrow 0$			$0 \rightarrow 0$		
$0 \rightarrow 1$	1	$0 \rightarrow 1$		$0 \rightarrow 1$			$0 \rightarrow 1$		
$1 \rightarrow 0$		$1 \rightarrow 0$		$1 \rightarrow 0$			$1 \rightarrow 0$		
$1 \rightarrow 1$		$1 \rightarrow 1$		$1 \rightarrow 1$			$1 \rightarrow 1$		

Table 5.2: The transition lists for the four types of basic memory elements.


S2	S1	S0	Operation
0	0	0	Hold
0	0	1	Load
0	1	0	ASR
0	1	1	ASL
1	0	0	LSR
1	0	1	LSL
1	1	0	CSR
1	1	1	CSL

Table 6.3: The truth table for a universal shift register.

6.0 Exercises

1. **(8 points)** Build a 4-bit universal shift register in Table 6.3 using D flip-flops and 8:1 multiplexers.

Solution

 


2. **(8 pts.)** Use a counter and a comparator to implement the following circuits.

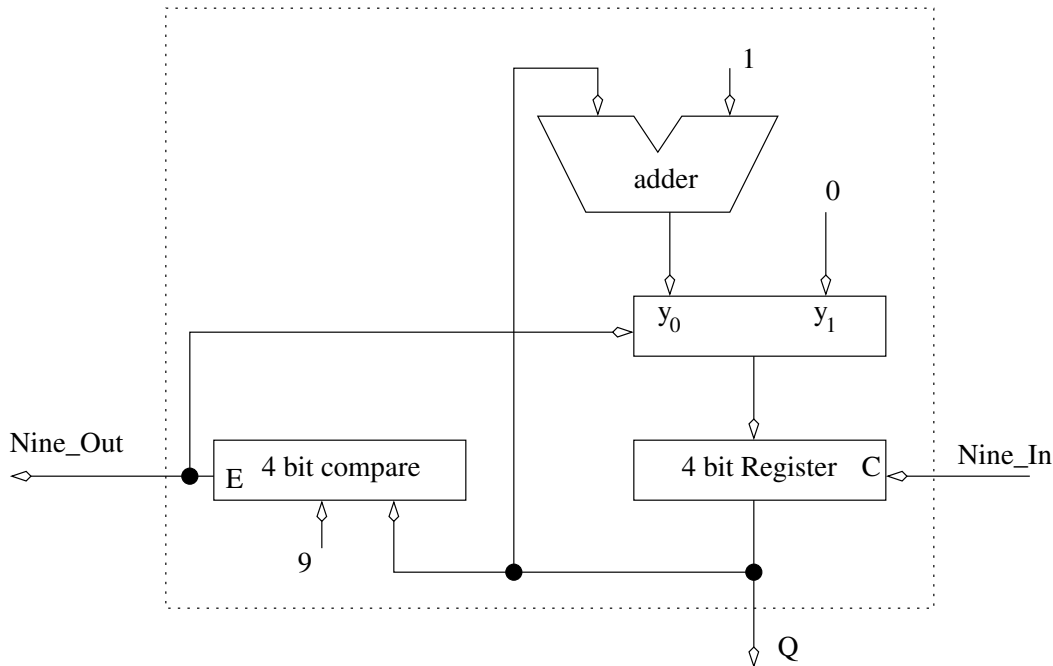- a) Show how to modify the counter (by adding some external logic) to implement a mod-10 counter. A mod-10 counter counts from 0 to 9 and then goes back to 0. It spends one full clock cycle on each of these count values.

Solution Our mod 10 counter will have 1 data input, representing the state of the least significant counter. Call this input *Nine In*. *Nine In* equals 1 when the less significant counters output equals 9, otherwise *Nine In* equals 0. Our mod 10 counter will have four bits of output representing the current count value. The mod 10 counter will also have a *Nine Out* output which will equal 1 when our current

count value equals 9, otherwise Nine Out equals 0. Let the constant value 9 be sent to the Y input of the comparator and the 4-bit register (Q) sent to the X input. When $Q \geq 9$ the comparator outputs $G=0$, $L=1$, $E=0$. When $Q=0$ then the comparator outputs $G=0$, $L=0$, $E=1$. Hence by running the E output of the comparator to the select input of the mux, the $Q+1$ will be sent to the register input when $Q \geq 9$. Notice that the register will only latch a new value ($Q+1$ or 0) when the less significant counter has rolled over.



- b) Use four mod-10 counters to build a 4-digit decimal counter which counts up from 0 to 9999. Draw a schematic for the 4-digit decimal counter.

Solution Just ripple four of the above counter head to tail via Nine In and Nine Out. Set the Nine In input of the least significant counter to 1.


3. (8 pts.) Design a circuit which contains three 8-bit registers X,Y,Z. The behavior of the circuit is determined by the statement:

`if (X > Y) then Z = X+X else Z = Y+Y`

The registers are preloaded with values in them. Submit a circuit diagram showing the building blocks uses, their interconnections and any miscellaneous logic required to make them operate together. **Solution**

 
4. (8 pts.) Design a circuit which contains three registers X,Y,Z. The behavior of the circuit is determined by the statements:

```
1. while (X > 0) {
2.     Z = Z+Y;
3.     X = X-1;
4. }
```



The registers are preloaded with values in them. Submit a circuit diagram showing the building blocks used, their interconnections and any miscellaneous logic required to make them operate together. The design should use an adder and an adder subtractor plus some other building blocks. Hint, use the enable inputs of the registers to control when they latch information.

Solution

 


5. **(8 pts.)** Given three 32-bit registers A,B,PC, design a circuit which adds PC and A (putting the result back into PC) when A is equal to B. Otherwise, add 1 to PC. The contents of A and B are to remain unchanged.

Solution

 
6. **(8 pts.)** Build a circuit that performs the following:

```
for(i=0; i<100; i++)
    total = total + i;
```



Use the counter described in this chapter for the i variable; assume that the counter is initialized to 0. **total** is stored in a register and its initialized to 0. Use a comparator to shut down the counter and put the register in hold when the count value reaches a critical value. Until this critical value is reached the comparator should allow the counter to count and the register to load.

Solution Note that the counter really needs only one of two control settings 00 for holding and 10 for counting up. Thus, the LSB of the counters control input can be hardwired to 0. It's the MSB of the counters control that needs controlled by the comparator. Since the counter is in the range of 0-100, the counter has a 7-bit output. It is an interesting exercise to determine the number of bits required for the adder's output so that it does not overflow during the computation. The figure below shows that 13 bits are required (the upper six bits of the counter's output are padded with 0's so that the counters output can be feed into the adder).

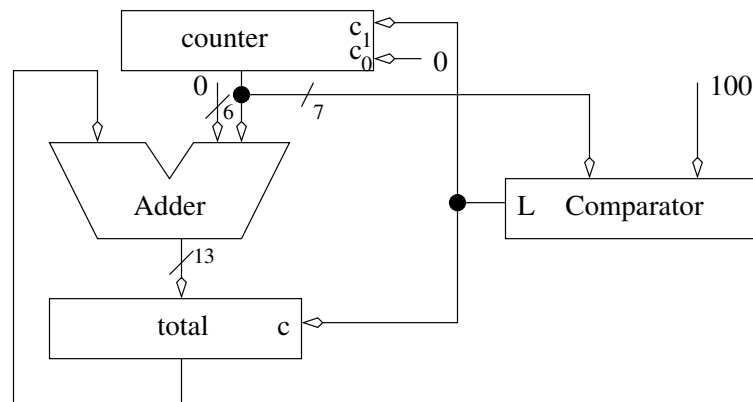


7. (8 pts.) Build a circuit that performs the following:


```

for(i=0; i<100; i++)
    total = total + 1;

```

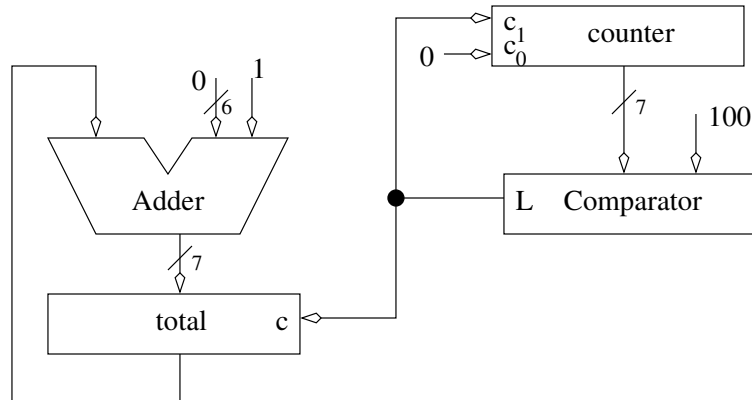Solution

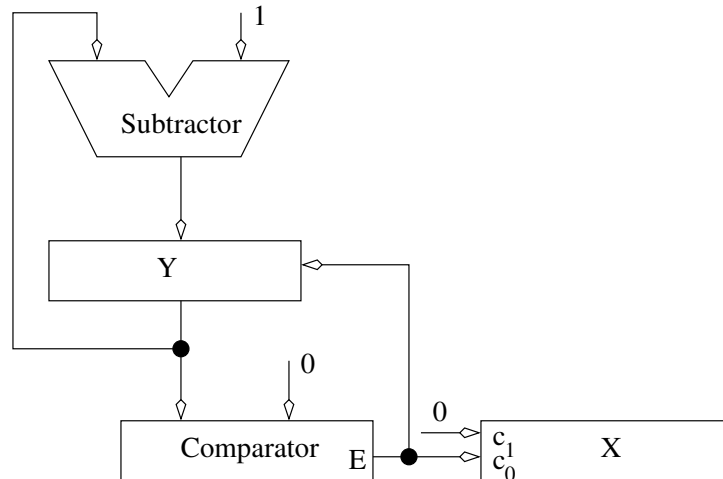8. **(8 pts.)** Design a circuit that can shift (circular to the right) the contents of register X by an amount given in register Y. X is stored in the circular shift register described in this chapter. The solution will require a comparator and a counter. **Solution**



9. **(8 pts.)** Assume a 32kx8 RAM is full of data. Show the hardware required to realize the following algorithm.


```

for(i=0; i<32767; i++)
    total = total + M[i];

```

Where $M[i]$ is the 8-bit word stored at address i . Assume the total register is initialized to 0. The i variable should be the output of a counter. Use a comparator to shut down the counter and to put the register in hold when the count value reaches a critical value.

Solution

 


10. (8 pts.) Show how to initialize a 32kx8 RAM in the following manner.

```
for(i=0; i<32767; i++)
    M[i] = i mod 256;
```

Where the “ $i \bmod 256$ ” statement means store the least significant eight bits of the i variable into the RAM.

Solution

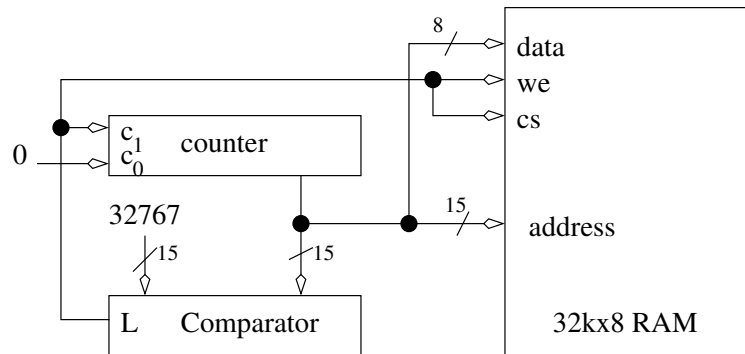

11. (5 pts.) Complete the timing diagram in Figure 6.13 for a 4-bit arithmetic shift register. Use the control setting from the truth table on page ??.

Solution

12. (5 pts.) Complete the timing diagram in Figure 6.14 for a 4-bit counter. Use the control setting from the truth table on page ??.

Solution

13. (5 pts.) Complete the timing waveforms for A_1 , A_0 , Q_1 , Q_0 based on the circuit diagram shown in Figure 6.15. Use the truth table on page ?? for the register. Put the decimal representation of the signals in the timing diagram (like the timing diagram in Figure ??).

Solution


 


Figure 6.13: The timing diagram for a 4-bit arithmetic shift register in Problem 11.

 

14. (4 pts.) The circuit shown in Figure 6.16 generates a Fibonacci sequence, a sequence starting with 1,1,2,3... The next number in the sequence is the sum of the preceding two numbers. Complete the timing diagram, assuming the circuit starts with the values shown. Identify the signal which generates a complete Fibonacci sequence.

 


Figure 6.14: The timing diagram for a 4-bit counter in Problem 12.

 
 


Figure 6.15: The circuit diagram and incomplete timing diagram for Problem 13.

 
 


Figure 6.16: A circuit which generates a Fibonacci sequence.

7.0 Exercises

1. A finite state machine has been implemented with four flip-flops, two inputs and three outputs.
 - a) What are the minimum and maximum number of states in the diagram? **Solution** *Since there are three flip flops we can have a maximum of 8 states. The minimum number of states is a bit tricky. A practical answer is 5, because if you had fewer states you would use fewer flip flops. However, the question asks for a minimum, in which case you could have 1 state. Note, that a 1 state FSM would only generate a single output and hence would not be a very interesting circuit.*
 - b) What are the minimum and maximum number of transition arrows starting at a particular state? **Solution** *These values are the same. Since there are two bits of input there are four different inputs that can be applied at each state. Thus, four arrows must leave each state.*
 - c) What are the minimum and maximum number of transition arrows ending in a particular state? **Solution** *In a typical design your systems will have a reset state, it normal for such states to have NO input arcs. You only visit them when the power is turned on. This is the minimum number of arcs that can terminate at a state. On the other hand, I could image a machine where transition arc points to a particular state (not a very interesting FSM). Hence all 32 arcs could point to a single state.*
 - d) What are the minimum and maximum number of different binary patterns that are displayed on the outputs? **Solution** *this is a tricky question, you need to determine which of the inputs and outputs constrains the number of distinct patterns on the output. You should consult figure 7.1 for some guidance. There are three bits of output which have the possibility of generating 8 different outputs. There are a total of six bits of input to the combinational logic box, more than enough to cope with the 8 different output. On the other end of the scale, I can imagine a FSM which only produces a single output, it would however, not be very interesting.*
2. **(20 points)** The state assignment for a FSM influences the amount of combinational logic required in the realization. In the following problem this phenomena is investigated. Determine the MIEs for the following state table using both the state assignments.

State Table			State Assignment 1				State Assignment 2			
CS x	0	1	State	Q_2	Q_1	Q_0	State	Q_2	Q_1	Q_0
A	A,0	B,0	A	0	0	0	A	0	0	0
B	C,1	F,1	B	0	0	1	B	1	1	1
C	D,0	C,0	C	0	1	1	C	0	0	1
D	A,1	H,1	D	0	1	0	D	1	1	0
E	F,1	E,1	E	1	0	0	E	1	0	1
F	G,0	F,0	F	1	0	1	F	0	1	1
G	G,1	C,1	G	1	1	1	G	1	0	0
H	D,1	E,1	H	1	1	0	H	0	1	0

After obtaining the MIEs for both realizations, determine the cost of each solution according to the following formula: $C(FSM) = A + O + 6 * F$. Where $C(FSM)$ denotes the cost of the FSM, A is the cost of the AND gates, O is the cost of the OR gates, and F is the number of flip flops. The cost of an AND gate is equal to the number of inputs to the AND gate. Likewise the cost of an OR gate is equal to the number of inputs. NOT gates are free. For example, the circuit $A'B + ABC'$ costs $2 + 3 + 2 = 7$.

Submit:

- a) Shared steps of the design process.
b) Derive the MIEs for each of the two realizations. **Solution**

State Assignment 1

$Q_2Q_1 \ Q_0x$	00	01	11	10
00	$000,0$	$001,0$	$101,1$	$011,1$
01	$000,1$	$110,1$	$011,0$	$010,0$
11	$010,1$	$100,1$	$011,0$	$111,1$
10	$101,1$	$100,1$	$101,0$	$111,0$

$$D_2 = Q_1Q'_0X + Q'_1Q_0X + Q_2Q_0X' + Q_2Q'_1$$

$$D_1 = Q_2Q_1X' + Q'_2Q_1X + Q_1Q_0 + Q_0X'$$

$$D_0 = Q_2Q'_1X' + Q'_2Q'_1X + Q'_1Q_0 + Q_2Q_0 + Q_0X$$

$$Z = Q'_2Q'_1Q_0 + Q_1Q'_0 + Q_2Q'_0 + Q_2Q_1$$

State Assignment 2

$Q_2Q_1 \ Q_0x$	00	01	11	10
00	$000,0$	$111,0$	$001,0$	$110,0$
01	$110,1$	$101,1$	$011,0$	$100,0$
11	$000,1$	$010,1$	$011,1$	$001,1$
10	$100,1$	$001,1$	$101,1$	$011,1$

$$D_2 = Q_2Q'_1Q'_0X' + Q_2Q'_1Q_0X + Q'_2Q_1Q'_0 + Q'_2Q'_0X + Q'_2Q_0X'$$

$$D_1 = Q'_2Q_1Q'_0X' + Q'_2Q'_1Q'_0X + Q_2Q_1X + Q_1Q_0X + Q'_1Q_0X'$$

$$D_0 = Q'_1X + Q'_2X + Q_2Q_0$$

$$Z = Q_1Q'_0 + Q_2$$

- c) Determine the cost of each of the two realizations.

	<i>State Assignment 1</i>	<i>State Assignment 2</i>
D_2	15	22
D_1	14	22
D_0	17	9
Z	13	4
<i>Total</i>	$6*3 + 59 = 77$	$6*3 + 57 = 75$

- d) Determine the cost of each of the two realizations using Espresso. **Solution** *Espresso cost 77 for state assignment 1*
Espresso cost 75 for state assignment 2

3. **(8 pts.)** Realize the FSM in the previous problem using a one-hot encoding. Determine the MIEs and the cost of the circuit using the same metric. It is helpful to convert the state table into a state diagram. **Solution**

$$D_A = Q_AX' + Q_DX'$$

$$D_B = Q_AX$$

$$D_C = Q_BX' + Q_CX + Q_GX$$

$$D_D = Q_CX' + Q_HX'$$

$$D_E = Q_EX + Q_HX$$

$$D_F = Q_B X + Q_E X' + Q_F X$$

$$D_G = Q_F X' + Q_G X'$$

$$D_H = Q_D X$$

$$Z = Q_B + Q_D + Q_E + Q_G + Q_H$$

The cost of this solution is $6 \cdot 8 + 6 + 2 + 9 + 6 + 6 + 9 + 6 + 2 + 5 = 48 + 51 = 99$

4. **(8 points)** Enhance the vending machine discussed in this chapter as follows. Add two buttons for a beverage selection; *regular* soda and *diet* soda, see Figure 7.17. This machine will have a change dispenser. If the user deposits more than 35¢, the circuit should send a signal to either the *nickel change* dispenser or the *dime change* dispenser, a single bit sent for one clock cycle to a dispenser will yield a single coin. When the user deposits 35¢(or more) the machine gives any change and then waits for one of the two buttons to be depressed. Depending on the selection, the circuit should send a signal to either the *regular dispenser* or the *diet dispenser* mechanism. The dispenser need only get a signal for one clock cycle. After the dispensing, go back to the reset state.


 


Figure 7.17: A basic vending machine.

Solution

 Note, that in the figure if a input does not appear on any arc emanating from a state then it is implied that this input will have no effect on the next state. Below are the outputs for each of the states above.



<i>outputs from the vending FSM</i>			
<i>state</i>	<i>nickel change</i>	<i>diet dispense</i>	<i>regular dispense</i>
	<i>0 give none</i>	<i>0 give none</i>	<i>0 given none</i>
	<i>1 give nickel</i>	<i>1 dispense diet</i>	<i>1 dispense regular</i>
<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>5</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>10</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>15</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>20</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>25</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>30</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>35</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>40</i>	<i>1</i>	<i>0</i>	<i>0</i>
<i>d</i>	<i>0</i>	<i>1</i>	<i>0</i>
<i>r</i>	<i>0</i>	<i>0</i>	<i>1</i>

5. **(6 pts.)** Build a FSM for a car alarm. The input to the FSM comes from a tilt sensor. The tilt-sensor outputs 1 when the car has been physically displaced by a preset amount, otherwise the tilt sensor outputs 0. The output of the circuit drives an alarm, when the alarm output equals 1 the alarm sounds, otherwise the alarm does not sound. Once the alarm has been set off, it will continue sounding until a reset input equals 1, at which point the alarm will stop sounding.

Draw the state diagram and from this determine the MIEs and OEs.

6. **(12 pts.)** Build a FSM which displays the revolutions per second (RPS) of a motor. The output shaft of the motor is attached to a sensor whose output pulses to logic 1 every time the motor's shaft completes a single revolution. This sensor signal is attached to a counter. The behavior of the counter to the pulse input is determined by a 1-bit control input (coming from the FSM) given by the following truth table.

control	behavior
0	reset to 0
1	count up

The counter's output is eight bits wide, representing two BCD digits. Thus, the counter's output will go from 19 to 20 when the control input is 1 and there is a pulse on the sensor line. This 8-bit output from the counter is sent to the data input of an 8-bit register. The register's control input comes from the FSM. The output of the register is split into two nybbles (a 4-bit value is called a nybble) each sent its own BCD to 7-segment converter. In order to determine when a second is up, the FSM is fed a reference signal denoted by the variable R with a period of exactly 1Hz and a 50% duty cycle; the duty cycle of a square wave is the proportion of time the signal spends at logic 1. That is R is at logic 1 for half a second and then at logic 0 for half a second. The FSM is being supplied with a clock signal, clk , with a frequency much greater than 1Hz (perhaps in the MHz range). The architecture of the FSM is given in the figure below.

Submit:

- a) Label the arcs of the FSM with R or R' so that the circuit operates correctly.
- b) Determine the output for each state. Instead of writing the output in each state, list the outputs in the following control word table.

state	counter	register
	0 reset	0 hold
	1 count up	1 reset
RefLo		
RefHi		
Load		
Reset		

- c) Determine the output equations.
 - d) Determine the memory input equations assuming a one-hot encoding of the states.
7. (12 pts.) Build a digital circuit which controls an automatic garage door opener. The garage door circuit has three bits of input. The first input, called *button*, comes from a the main control button used to open or close the garage door. When pressed $button = 1$ otherwise $button = 0$. The garage door rides in a track, at the top and bottom of of which are two limit switches. The top limit switch equals 1 when the garage door is all the way up, otherwise its output equals 0. The bottom limit switch equals 1 when the garage door is all the way down, otherwise its output equals 0. The garage door circuit has two bits of output called *motor*. When $motor = 01$, the motor moves the door in a downward motion, closing the door. When $motor = 10$, the motor moves the door upward, opening the garage door. When $motor = 00$, the motor is turned off.

Figure 7.18: The garage door and the circuit controlling it.

Construct the FSM assuming a one-hot encoding of the states. Determine the memory input equations and output equations.

Solution

Control unit *The control unit includes so called wait states. Wait states are a result of the fact that the clock running the FSM is usually much faster than the physical phenomena being monitored by the FSM. Unless told otherwise, you can assume that any FSM that you are building has a clock which operates on the order of megahertz.*

This means that the resulting FSM can make around 1 million state transitions per second. Clearly, a garage door needs more than one millionth of a second to open or close. Consequently, the FSM in this problem needs to wait for the door to be opened. This is done by having the FSM repetitively check the status of the door via the up or down limit switches. In addition to waiting for the garage door to open and close the FSM must wait for a button press.

Figure 7.19: The FSM for the garage door controller.

The state diagram for the garage door controller has four states. In the open and close state, the FSM is waiting for a button push, while the button is not pressed the door stays open or closed. As soon as the button is pressed the door starts to open or close. It stays in this state until the limit switches tell the FSM that the door has reached the limit of its travel.

Memory Input Equations Since we are building the garage door controller assuming a one hot encoding of the states, each state will get its own flip flop. Each flip flop will output a 1 when the FSM is in that state. The memory input equations for a particular state are determined by answering, “how do you get into that state?” The four answers to this questions are provided below.

$$\begin{aligned} D_{open} &= Q_{open}button' + Q_{opening}up \\ D_{close} &= Q_{close}button' + Q_{closing}down \\ D_{opening} &= Q_{close}button + Q_{opening}up' \\ D_{closing} &= Q_{open}button + Q_{closing}down' \end{aligned}$$

Output Equations The outputs for complex FSMs are usually not written inside the states, rather a separate table is constructed which contains the output for each state. Even though this is a simple example we will construct an output table.

State	motor
	00 stop
	01 down
	10 up
open	00
close	00
opening	10
closing	01

Call the outputs Z_{m1} and Z_{m0} , for the most and least significant bits of the output respectively. Then the outputs are determined by asking for which states does the output equal 1? The answers to this question are shown below.

$$\begin{aligned} Z_{m1} &= Q_{opening} \\ Z_{m0} &= Q_{closing} \end{aligned}$$

8. **(8 pts.)** Build a digital circuit to control a single traffic light. The circuit has three outputs, *Rlight*, *Ylight* and *Glight*. When *Rlight* = 1 the red light illuminates otherwise the light is off. The same behavior holds true for *Ylight* and *Glight*. In order to sequence the lights, the circuit has three timers, *Rtimer*, *Gtimer* and *Ytimer*. Each timer controls the length of time that its light should be illuminated. Each timer has one bit of input

and one bit of output. When a timer's input is 0, the timer is reset. When a timer's one bit input is 1, the timer counts down its preset timer interval. When a timer counts all the way down, its output goes to 1 and stays there until the timer is reset (by applying an input of 0). The state diagram of the circuit is shown in the figure below. As shown in this figure the FSM receives input from the three timers, while the output of the FSM controls the counters. Complete the following three tasks.

- Label the arcs of the FSM with the input values (Rt, Yt or Gt) needed to make the circuit operate correctly.
- Next, determine what the output should be in each of the states. Instead of writing the output in each state, the outputs are organized in a separate table. In this table, each row will contain the output associated with a particular state. Each column in the table will be associated with one bit of the output.

state	Rlight	Ylight	Glight	Rtimer	Ytimer	Gtimer
	0 off	0 off	0 off	0 rst	0 rst	0 rst
	1 on	1 on	1 on	1 run	1 run	1 run
R						
Y						
G						

- Finally, write the memory input equations and output equations for the traffic light controller. In order to write the memory input equations use the labels on the state transitions from the state diagram. In order to write the output equations use the output table.

$$\begin{array}{ll}
 Q_{red} = & Z_{Rlight} = \\
 Q_{yellow} = & Z_{Ylight} = \\
 Q_{green} = & Z_{Glight} = \\
 & Z_{Rtimer} = \\
 & Z_{Ytimer} = \\
 & Z_{Gtimer} =
 \end{array}$$

- (16 pts.)** Build a FSM which make the hexapod robot shown in Figure 7.20 walk forward.

Each leg of the hexapod robot is moved by two nitinol (Flexinol) wires. At rest, nitinol wire is straight. When 5 volts (logic 1) is applied to the wire, it bends in a particular direction. The two wires making up a particular leg are positioned so that they move in perpendicular directions. One wire moves a leg up or down and the other will move the wire forward or backwards. The table below elaborates.

wire	logic 0	logic 1
w_0	down	up
w_1	forward	backward

The hexapod robot walks by moving three legs in unison; see *A* and *B* in Figure 7.20. The movements of *A* and *B* are coordinated so that, at times, the hexapod is balanced on three legs. A portion of the walking gait is shown in Figure 7.21; note that in this figure the viewer is looking down at the top of the robot which is moving to the right. The dotted legs are assumed to be in the air, solid legs are in contact with the ground.

Assume that the legs can move to their correct position in one clock cycle. Define each state as a position of the legs in Figure 7.21. Draw the state diagram, and determine the memory input and output equations.

 


Figure 7.20: A hexapod walking robot.

 


Figure 7.21: The walking gait of the hexapod robot.

Solution

Note that the states have been given numbers to simplify the description of the states. Here is a listing of the outputs associated with each state:

State	Aw_1	Aw_0	Bw_1	Bw_0
1	0	0	1	1
2	1	0	0	1
3	1	1	0	0
4	0	1	1	0

MIEs and OEs

$$\begin{array}{ll}
 \text{MIEs} & \text{OEs} \\
 D_1 = D_4 & Z_{Aw_1} = Q_2 + Q_3 \\
 D_2 = D_1 & Z_{Aw_0} = Q_3 + Q_4 \\
 D_3 = D_2 & Z_{Bw_1} = Q_1 + Q_4 \\
 D_4 = D_3 & Z_{Bw_0} = Q_1 + Q_2
 \end{array}$$

10. (12 pts.) Build a FSM which makes the simple robot shown in Figure 7.22 move along (track) the black line crossing two intersections.

The FSM has two inputs, a left sensor, denoted ls , and a right sensor, denoted rs . These two sensors look down at the ground. When a sensor sees white, it outputs 0; when it see black, it outputs 1. The sensors are spaced far enough apart that they can straddle the black line and see white on either side. The FSM has two outputs, a left motor, denoted


 


Figure 7.22: A simple line-tracking robot that must cross two intersections.

lm and a right motor, denoted rm . A motor rotates when it is sent a 1 and does not rotate when it is sent a 0. The FSM should constantly check that the robot is straddling the line. If it is not the FSM should take corrective action by stopping one of the wheels.

Submit the state diagram for the FSM, MIEs and OEs using a one-hot encoding of the states.

Solution

 

State	lm	rm
	0 stop left wheel	0 stop right wheel
	1 turn left wheel	1 turn right wheel
Reset	1	1
Straight	1	1
Left	0	1
Right	1	0
OnLine	1	1
Up	1	1
Stop	0	0

11. **(16 pts.)** Make the robot from Problem 10 cross 63 intersections. The problem is that the number of states will grow to large to handle with a FSM by itself. Additional hardware, in the form of a counter and comparator, are added to the FSM to address this problem.

 


Figure 7.23: The innards of a intersection counting, line tracking robot.

Assume that the counter is reset to 0 when the circuit is first turned on. The robot must still track the line, but must also count up once every time it crosses an intersection.


Remember the digital circuit shown in Figure 7.23 is operating much faster than the robot is crossing intersections. The state diagram needs to have wait states while it crosses the intersection, similar to those in the DAISY example. Assume the counter counts up when the control input is 1 and the clock rises. When the control input is 0, then the counter holds its current count value.

Submit the state diagram for the FSM, OEs and MIEs for a one-hot encoding of the states.

Solution *If you encoded 64 line crossing using only a FSM you would have on the order*

of 256 states, 4 for each line crossing. The solution is to use a counter to keep track of how many lines have been crossed. The states below explain.

DP & CU

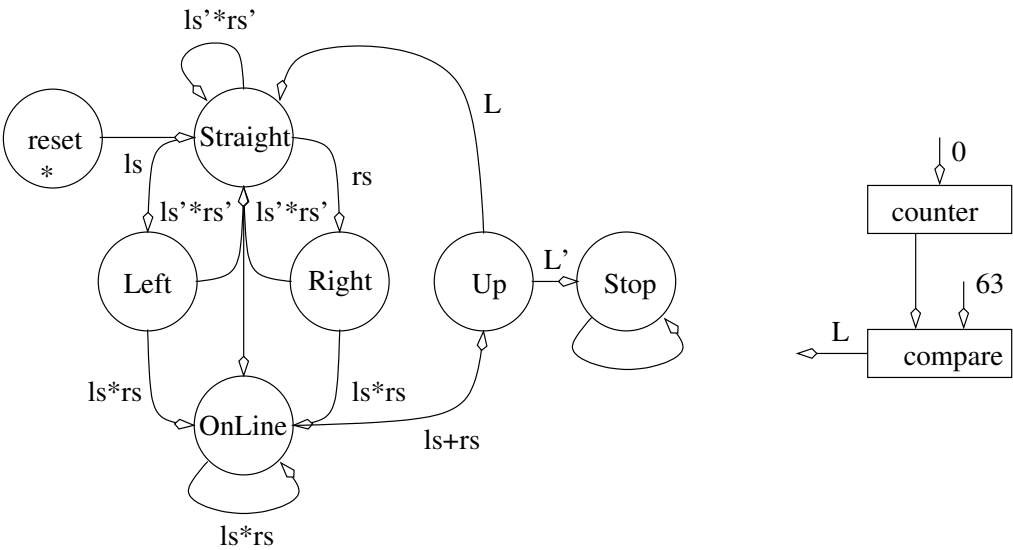

Control Word

State	lm	rm	counter
	0 stop left wheel	0 stop right wheel	00 hold
	1 turn left wheel	1 turn right wheel	01 load
			10 count
Reset	1	1	01
Straight	1	1	00
Left	0	1	00
Right	1	0	00
OnLine	1	1	00
Up	1	1	10
Stop	0	0	00

One could easily derive the MIEs and OEs for the FSM.

12. (24 pts.) Construct a digital circuit to control the operation of a simple washing machine, see Figure 7.24. To use the simple washing machine set the temperature switch to either hot, tepid or cold and then press the start button. To build a digital circuit to control the washing of clothes its necessary to understand the washing cycle. When the start button is pressed water of the selected temperature pours into the washing drum. The simple washing machine has two electronically controlled water valves, the hot valve admits hot water into the washing drum and the cold valve admits cold water. Water continues to pour into the drum until it fills. There are two water level sensors; the full switch signals when the drum is full of water and the empty switch signals when the drum is empty. After the drum is full of water the simple washing machine starts to agitate the clothes. The simple washing machine has a motor controlled by two bits, which agitates (a rapid back and forth motion), spins (a rapid rotation in one direction) or does

 


Figure 7.24: A humble washing machine with a close-up of the start button and temperature switch.

nothing. After agitating for 15 minutes, the agitation cycle stops and the machine drains its water. Water leaves the drum through a drain valve. When the drum is emptied of water the washing machine enters the rinse cycle. The rinse cycle fills the drum with cold water and agitates for 5 minutes. The rinse cycle concludes by draining the water from the drum. When the drum is emptied of water the washing machine enters the spin cycle. This lasts for 5 minutes. The simple washing machine keeps track of time using a 5 minute timer. To use the timer it must first be reset for one clock cycle. After being reset the timer will count down as long as the timer input is set to run. After 5 minutes have elapsed the timer output will go to logic 1 and stay there until the timer is reset. In order to get longer time intervals, the timer should be reset for another 5 minutes and count down again. When the spin cycle is done, the washing is complete. The inputs from the washing machine to the digital circuit have the following meaning.

inputs to the digital circuit				
start	temperature	empty	full	timer out
0 off	00 hot	0 not empty	0 not full	0 nothing
1 on	01 cold	1 empty	1 full	1 5 minutes elapsed
	10 tepid			

The outputs from the digital to the washing machine have the following meaning. The left most column is explained below.

outputs from the digital circuit					
state	hot	cold	motor	timer in	drain
	0 close	0 close	00 off	00 hold	0 close
	1 open	1 open	01 agitate	01 reset	1 open
			10 spin	10 run	
S1					

Draw the state diagram for the FSM to control the washing machine. Label the arcs of the state diagram with the input (or its negation) that causes the transition. Use simple Boolean expressions on these arcs, for example (start and hot). For each state define the output using a table similar to the one above. For example, if **S1** is a state fill in the bit values for the o outputs depending on what state **S1** is supposed to do. Determine the memory input equations and output equations assuming a one-hot encoding.

Solution

- a) No control table (-6)
- b) Disposable washing machine (-1)
- c) No OEs (-5)
- d) start * cold (-2)
- e) no complements on arcs (-2)

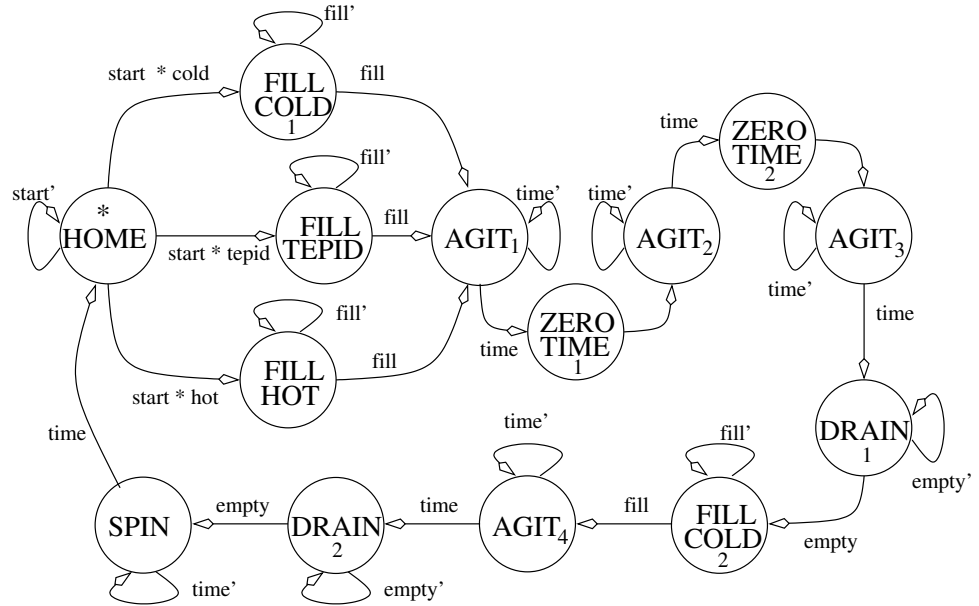


Figure 7.25: The FSM for a washing machine.

outputs from the digital circuit					
state	hot	cold	motor	timer in	drain
	0 close	0 close	00 off	00 nothing	0 close
	1 open	1 open	01 agitate	01 reset	1 open
			10 spin	10 start	
				11 stop	
HOME	0	0	00	00	0
COLD	0	1	00	01	0
TEPI	1	1	00	01	0
HOT	1	0	00	01	0
AGIT	0	0	01	10	0
ZERO	0	0	00	01	0
DRAI	0	0	00	01	1
SPIN	0	0	10	10	0

The memory input equations are a snap.

$$D_{home} = Q_{home}start' + Q_{spin}time$$

$$D_{cold1} = Q_{home} * start * cold$$

$$D_{tepi} = Q_{home} * start * tepid$$

$$\begin{aligned}
D_{hot} &= Q_{home} * start * hot \\
D_{agit1} &= Q_{cold1} * fill + Q_{tepid} * fill + Q_{hit} * fill + Q_{agit1} * time' \\
D_{zero1} &= Q_{agit1} * time \\
D_{agit2} &= Q_{zero1} * time + Q_{agit2} * time' \\
D_{zero2} &= Q_{agit2} * time \\
D_{agit3} &= Q_{zero2} * time + Q_{agit2} * time' \\
D_{drain1} &= Q_{agit3} * time + Q_{drain1} * empty' \\
D_{cold2} &= Q_{drain1} * empty + Q_{cold2} * fill' \\
D_{agit4} &= Q_{cold2} * fill + Q_{agit4} * time' \\
D_{drain2} &= Q_{agit4} * time + Q_{drain2} * empty' \\
D_{spin} &= Q_{drain2} * empty + Q_{spin} * time'
\end{aligned}$$

13. **(36 pts.)** Construct a digital circuit to control the movement of an elevator in a four-story building. The elevator will always wait on its current floor until a call button is pressed; see Figure 7.26. The elevator then moves to the floor that was called. The elevator then opens its doors and waits for an elevator control button to be pressed. If no elevator control button is pressed and a call to another floor is received, then the elevator closes the doors and goes to the new floor. When a floor is selected on the elevator control panel, then the door close and the elevator moves to the desired floor.

 


Figure 7.26: The layout of an elevator in a four story tall building.

The inputs to the digital circuit clearly include all the buttons. When a button is pressed on the elevators control panel two things happen. A 2-bit binary value representing the button pressed becomes valid and a 1-bit panel request becomes valid. The panel request line will remain valid until acknowledged.

When a call button is pressed two things happen. A 2-bit binary value representing which call button was pressed becomes valid and a 1-bit call request becomes valid. The call request line will remain valid until acknowledged.

Another input tells the circuit when the elevator is or is not aligned with a floor. For example, consider an elevator moving from the first to the third floor. Initially, the align

variable is 1. When the elevator starts to move away from the first floor towards the second, the align variable goes to 0. When the elevator reaches the second floor, the align variable will go to logic 1 and remain there for a short while (at least several milliseconds) because there is some slack allowed in what is considered “aligned”. After the elevator passes the second floor, the align variable goes back to 0 and stays there until the elevator reaches the third floor.

Here is the table of inputs to the FSM, their abbreviations, to be used in the FSM, and their meaning.

Control panel floor	Pfloor	2-bit floor number	
Panel request	Preq	The panel has a valid floor	
Call floor	Cfloor	2-bit floor number	
Call request	Creq	The call buttons have a valid floor	
Align	Align	0 not aligned	1 Aligned

The outputs from the digital circuit to control the door and the movement of the elevator.

Panel acknowledge	Pack	Acknowledge the panel request	
Call acknowledge	Cack	Acknowledge the call request	
Door	0 close	1 open	
Motor	00 stop	01 up	10 down

Submit; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations.

14. **(36 pts.)** Construct a digital circuit to control the movement of traffic at the four way intersection shown in Figure 7.27.

 


Figure 7.27: The layout of a four way intersection.

The circuit comes equipped with timers. The timer has 2 inputs which set the timer to some preset amount of time or allows the timer to count down. When the timer reaches 0 then the output of the timer goes to 1. When the timer is not at 0 then the output equals 1. The specific inputs and behavior are described in the following truth table.

timer input	behavior
00	count down
01	set to timer to 5 seconds
10	set to timer to 15 seconds
11	set to timer to 30 seconds

In addition to the timer there are a variety of real world inputs sent to the circuit described in the following table.

Name	Abbreviation	Function
E or W Pressure Sensor	EW-PS	1 if 250 lb. or more on E or W sensor
Ped button	ped	1 if any pedestrian crosswalk button

The outputs from the digital circuit to control the lights are:

light	0x red	10 yellow	11 green
-------	--------	-----------	----------

The main sequence of events is outlined below;

```
while(1) {
    Nlight = Slight = green;
    Elight = Wlight = red;
    wait 30 seconds;
    while ((EW-PS == 0) && (ped == 0));
    Nlight = Slight = yellow;
    wait 5 seconds;
    if (ped == 1) {
        Nlight = Slight = red;
        Elight = Wlight = red;
        wait 15 seconds;
    }
    Nlight = Slight = red;
    Elight = Wlight = green;
    wait 15 seconds;
    Elight = Wlight = yellow;
    wait 5 seconds;
    if (ped == 1) {
        Nlight = Slight = red;
        Elight = Wlight = red;
        wait 15 seconds;
    }
}
```

Submit; the control unit, the control word table, the memory input equations, and output equations.

Solution

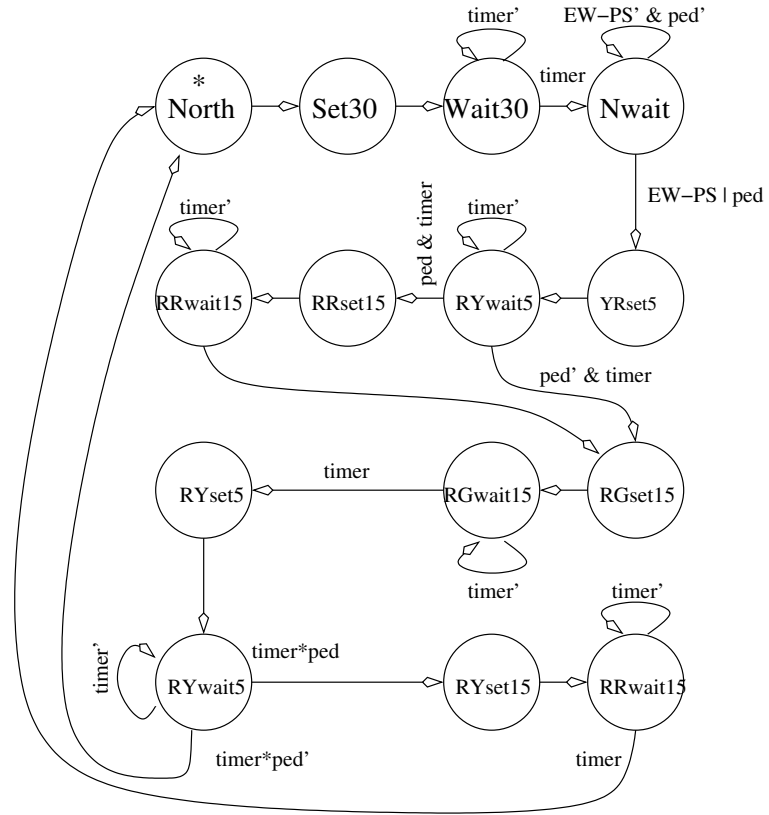


Figure 7.28: The FSM for a traffic light controller.

<i>outputs from the digital circuit</i>			
<i>state</i>	<i>Timer</i>	<i>NS light</i>	<i>EWlight</i>
	00 down	00 red	00 red
	01 5 sec	01 red	01 red
	10 15 sec	10 yellow	10 yellow
	11 30 sec	11 green	11 green
<i>North</i>	00	11	00
<i>set30</i>	11	11	00
<i>wait30</i>	00	11	00
<i>Nwait</i>	00	11	00
<i>YRset5</i>	01	10	00
<i>YRwait5</i>	00	10	00
<i>RRset15</i>	10	00	00
<i>RRwait15</i>	00	00	00
<i>RGset15</i>	10	00	11
<i>RGwait15</i>	00	00	11

The memory input equations are a snap.

$$D_{North} = Q_{RYwait5} * ped * timer + Q_{RRwait15} * timer$$

$$D_{Set30} = Q_{North}$$

$$\begin{aligned}
D_{Wait30} &= Q_{Set30} + Q_{Wait30} * timer' \\
D_{Nwait} &= Q_{Wait30} * timer + Nwait * EW_P S' * ped' \\
D_{YRset5} &= Q_{Nwait} * (EW_P S + ped) \\
D_{YRwait5} &= Q_{YRset5} + Q_{YRwait5} * timer' \\
D_{RRset15} &= Q_{YRwait5} * ped * timer \\
D_{RRwait15} &= Q_{RRset15} + Q_{RRwait15} * timer' \\
D_{RGset15} &= Q_{YRwait5} * ped' * timer + Q_{RRwait15} * timer \\
D_{RGwait15} &= Q_{RGset15} \\
D_{RYset5} &= Q_{RGwait15} * timer' \\
D_{RYwait5} &= Q_{RYset5} + Q_{RYwait5} * timer' \\
D_{RRset15} &= Q_{RYwait5} * ped \\
D_{RRwait15} &= Q_{RRset15} + Q_{RRwait15} * timer'
\end{aligned}$$

The output equations

$$\begin{aligned}
Z_{t1} &= Q_{set30} + Q_{RRset15} \\
Z_{t0} &= Q_{set30} + Q_{YRset5} \\
Z_{ns1} &= Q_{North} + Q_{set30} + Q_{wait30} + Q_{Nwait} + Q_{YRset5} + Q_{YRwait5} \\
Z_{ns0} &= Q_{North} + Q_{set30} + Q_{wait30} + Q_{Nwait} \\
Z_{ew1} &= Q_{RGset15} + Q_{RGwait15} \\
Z_{ew0} &= Q_{RGset15} + Q_{RGwait15}
\end{aligned}$$

8.0 Exercises

1. **(4 pts.)** Show how to eliminate the 4-bit 2:1 mux in the bit counter by assuming that the Y register had an asynchronous active low reset input. Consider the fact that the external world still needs the ability to hit a single button to reset the state of the entire circuit.
2. **(6 pts.)** A control unit has been built with the following control word:

Reg A	Reg B	Reg P	P mux
00 hold	00 hold	1 hold	1 Load 0
11 lsr	11 lsr		
10 lsl	10 lsl	0 load	0 Load Add
01 load	01 load		

Regrettably, these settings were completely wrong. In reality here is what the control word should have been:

Reg A	Reg B	Reg P	P mux
00 hold	00 hold	0 hold	0 Load 0
01 lsr	01 lsr		
10 lsl	10 lsl	1 load	1 Load Add
11 load	11 load		

The design team is in a total panic. The design team thinks that it will take weeks to straighten out the error, they claim that the control unit needs to be redesigned. However, there is a cheap and easy solution. Design some combinational logic to insert between the faulty control unit and the datapath in order to straighten out the bum control signals. There is one error can be fixed by changing something in the datapath, no extra hardware is required. Identify this error and its solution.

3. **(8 pts.)** Modify the algorithm for the bit counting circuit so that it uses a two-line handshake to transmit the Y register. The circuit should take the role of an active producer in the transmission of Y. The circuit has four handshaking lines and two data lines. Hint, a common error of students is to insert a three-state buffer on the output of the Y register to the outside world to prevent its transmission to the outside world until the value of Y is finalized. Don't do this! If the outside world reads the value of Y before the circuit's signals are valid (via the send_REQ signal) then it's their own dumb fault. Just send the Y signal outside the datapath as is.
4. **(16 pts.)** A 8kx32 RAM is full of integer data. Design a circuit to scan the RAM and find its smallest value.

Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

5. **(16 pts.)** A 8kx32 RAM is full of integer data. Design a circuit that determines the sum of the integers *between* addresses A and B. The values of A and B are to be read in using a two-line handshake where the circuit is to act as a passive consumer. The sum is to be placed in a 32-bit register S. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

Solution

Algorithm

```

while(REQ==0);
A = datain;
ACK=1;
while(REQ==1);
ACK=0;
while(REQ==0);
B = datain;
ACK=1;
while(REQ==1);
ACK=0;
S=0;
for(i=A; i<B; i++)
  MBR=RAM[i];
  S=S+MBR;
// end for

```

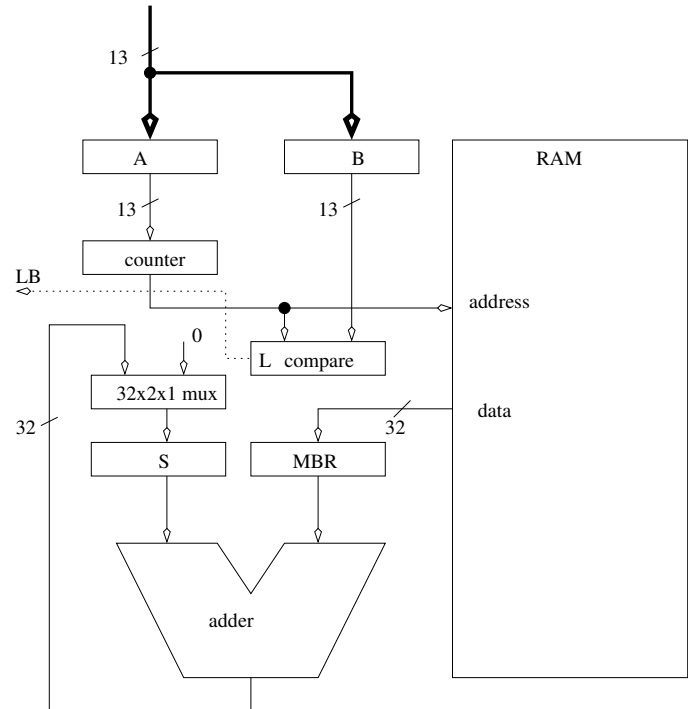
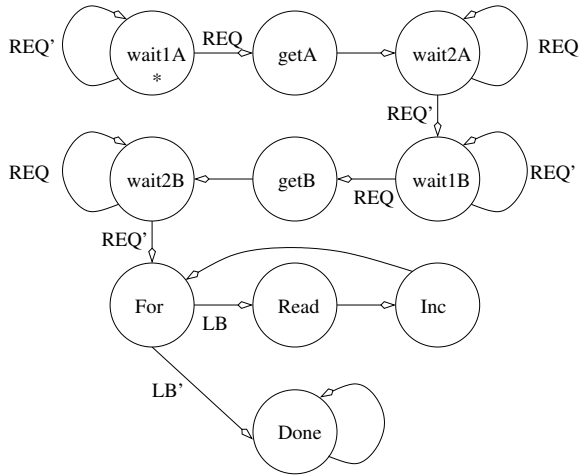
DP & CU

Figure 8.29: The datapath and control to determine the sum between addresses A and B.

Control Word

<i>STATE</i>	<i>A</i>	<i>B</i>	<i>MUX</i>	<i>S</i>	<i>MBR</i>	<i>counter</i>
	0 hold	0 hold	0 pass 0	0 hold	0 hold	00 hold
	1 load	1 load	1 pass $S+MBR$	1 load	1 load	01 UP
						10 load
<i>Wait1A</i>	0	0	0	0	0	00
<i>GetA</i>	1	0	0	0	0	00
<i>Wait2A</i>	0	0	0	0	0	00
<i>Wait1B</i>	0	0	0	0	0	00
<i>GetB</i>	0	1	1	1	0	10
<i>Wait2B</i>	0	0	0	0	0	00
<i>For</i>	0	0	0	0	0	00
<i>Read</i>	0	0	0	0	1	01
<i>Inc</i>	0	0	1	1	0	00
<i>Done</i>	0	0	0	0	0	00

MIEs and OEs

MIE

$$D_{Wait1a} = Q_{wait1a}req'$$

$$D_{GetA} = Q_{wait1a}req$$

$$D_{wait2a} = Q_{getA} + Q_{wait2a}req$$

$$D_{wait1b} = Q_{wait2a}req' + Q_{wait1b}req'$$

$$D_{GetB} = Q_{wait1b}req$$

$$D_{wait2B} = Q_{GetB} + Q_{wait2b}req$$

$$D_{For} = Q_{wait2B}req'$$

$$D_{Read} = Q_{For}LB$$

$$D_{Inc} = Q_{Read}$$

$$D_{Done} = Q_{For}LB'$$

OE

$$Z_A = Q_{getA}$$

$$Z_B = Q_{getB}$$

$$Z_{MUX} = Q_{getB} + Q_{Inc}$$

$$Z_S = Q_{getB} + Q_{Inc}$$

$$Z_{MBR} = Q_{Read}$$

$$Z_{c1} = Q_{GetB}$$

$$Z_{c0} = Q_{Read}$$

6. **(16 pts.)** Design a circuit that repetitively looks at a 1-bit input X. Anytime X changes logic values increment an 8-bit register Y. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.
7. **(16 pts.)** A 256x8 RAM is full of data. Design a circuit that jumps around in memory. It does this by fetching a word and using the retrieved word as the next address to jump to. The circuit is to start at address 0. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

To desired behavior of the circuit is illustrates in Figure 8.30. If the address=0 then the circuit will jump to address 3F then 28, 53, 3F and continue cycling for ever amount these three addresses.

8. **(16 pts.)** A 256x8 RAM is full of data. Design a circuit that jumps around in memory. The current address should be stored in a register called PC. If the MSB of the fetched word is 1, then the remaining seven bits represent a 7-bit 2's complement number; add these seven bits to the PC. If the MSB of the fetched word is 0 then just increment the PC. Repeat this process forever. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

 


Figure 8.30: A 256x8 RAM loaded with some data.

The desired behavior of the circuit is illustrated in Figure 8.31. In this figure if PC=0 then the word at that address (3F) has a MSB of 0 so the PC is incrementde to 1. The word at address 1 is fetched (BC) and has an MSB of 1 so the least significant seven bits of BC are added to the PC, making its new value 3D. repeating this process sees the PC goto address 21, 22, 21, 22 into a never ending cycle. Make sure the solution identifies how to add the least significant seven bits to an 8-bit PC.

 


Figure 8.31: A 256x8 RAM loaded with some data.

Solution

Control Word

<i>STATE</i>	<i>RE</i>	<i>CS</i>	<i>MUX</i>	<i>MBR</i>	<i>PC</i>
	0 nada	0 nada	0 pass 1	0 hold	0 hold
	1 read	1 RAM	1 pass MBR	1 load	1 load
<i>READ</i>	1	1	<i>x</i>	1	0
<i>MSB?</i>	0	0	<i>x</i>	0	0
<i>INC</i>	0	0	0	0	1
<i>MBR</i>	0	0	1	0	1

MIEs and OEs

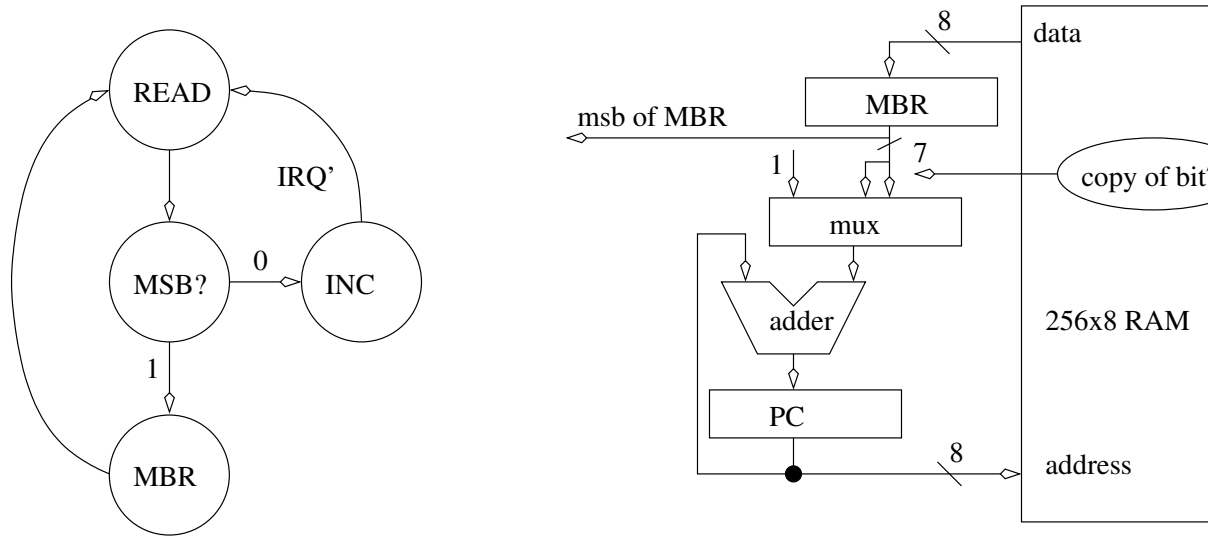


Figure 8.32: The datapath and control to conditionally hop around in RAM.

MIE	OE
$D_{read} = Q_{mbr} + Q_{inc}$	$Z_{re} = Q_{read}$
$D_{msb} = Q_{read}$	$Z_{cs} = Q_{read}$
$D_{inc} = Q_{msb}m'$	$Z_{MUX} = Q_{mbr}$
$D_{mbr} = Q_{msb}m$	$Z_{mbr} = Q_{read}$

9. **(16 pts.)** Modify the circuit in the previous problem as follows. Anytime an external input, called IRQ , is asserted the circuit is to stop jumping around and assert and ACK . The outside world will then read the PC (which must be routed outside the datapath) and then drop the IRQ . The circuit should then drop the ACK and resume jumping. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.
10. **(16 pts.)** Design a circuit that reads successive words from a $1k \times 12$ RAM and updates a 12-bit register called **ACC** based on the upper two bits of the memory word. The address of the current memory word should be contained in a register called PC (Program Counter). Since the words read from the RAM will tell us what operation to perform on the ACC , the memory word will be stored in a register called IR (Instruction Register). If the upper two bits of IR are:
 - a) 00 then add the lower 10 bits of the IR to ACC . Pad the upper two bits of the IR with 0's before adding to the ACC .
 - b) 01 then store the ACC to the address specified by the lower 10 bits of the IR .
 - c) 10 then load the ACC from from the address specified by the lower 10 bits of the IR .
 - d) 11 then clear the value of ACC to 0.


The PC is to be initialized to 0. After the each memory word is read and the appropriate operation performed on ACC , the PC should be incremented. Turn in; an algorithm

the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

Solution

Algorithm

Datapath and Control

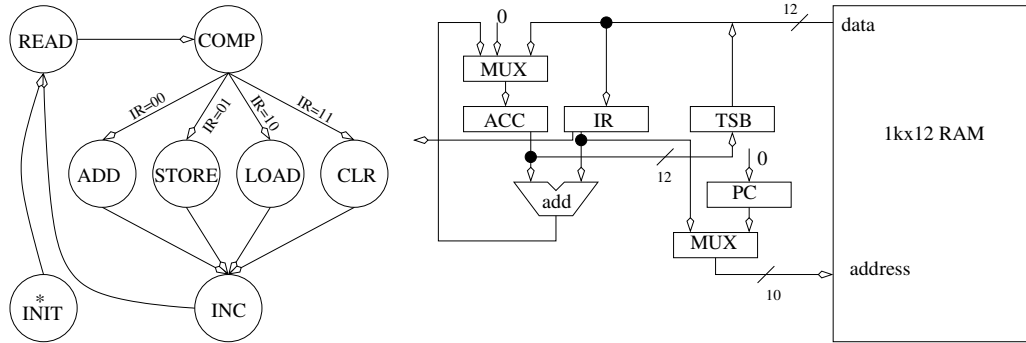

Control Word

State	ACC mux	Acc	IR	TSB	PC	Addr Mux	CS	R/W'
	00 add	0 hold	0 hold	0 Z	00 hold	0 PC	0 no	0 write
	01 0	0 load	0 load	1 pass	01 load	1 IR	0 on	1 read
	10 RAM				10 up			
Init	01	1	0	0	01	x	0	x
Read	xx	0	1	0	00	0	1	1
Comp	xx	0	0	0	00	x	0	x
Add	00	1	0	0	00	x	0	x
Stor	xx	0	0	1	00	1	1	0
Load	10	0	0	0	00	1	1	1
Clr	01	1	0	0	00	x	0	x
Inc	xx	0	0	0	10	x	0	x

MIEs and OEs

$$\begin{aligned}
 \text{MIE} \quad & D_{Init} = Q_{wait1a}req' \\
 & D_{Read} = Q_{wait1a}req \\
 & D_{Comp} = Q_{getA} + Q_{wait2A}req \\
 & D_{Add} = Q_{wait2a}req' + Q_{wait1B}req' \\
 & D_{Stor} = Q_{wait1b}req \\
 & D_{Load} = Q_{getB} + Q_{wait2b}req \\
 & D_{Clr} = Q_{wait2B}req' \\
 & D_{Inc} = Q_{ForLB} \\
 \text{OE} \quad & Z_{m1} = Q_{load} \\
 & Z_{Init} = Q_{Clr} \\
 & Z_{Acc} = Q_{Init} + Q_{Add} + Q_{Clr} \\
 & Z_{IR} = Q_{Read} \\
 & Z_{TSB} = Q_{Stor} \\
 & Z_{PC1} = Q_{Inc} \\
 & Z_{PC0} = Q_{Init} \\
 & Z_{CS} = Q_{Read} + Q_{Stor} + Q_{Load} \\
 & Z_{Amux} = Q_{Read} + Q_{Stor} + Q_{Load} \\
 & Z_{RW} = Q_{Read} + Q_{Load}
 \end{aligned}$$

11. (16 pts.) Design a circuit that moves M consecutive words from address S (source) to address D (destination). For example, if $M = 4$, $S = 3EA$ and $D = 1FE$ then the circuit would move words $3EA$, $3EB$, $3EC$ and $3ED$ to address $1FE$, $1FF$, 200 and 201 . Each of M, S, D is preloaded into a register. While this problem appears simple, its really rather treacherous. The circuit will have to handle cases where $S + M > D$. In such a case the order of the data movement must be carefully planned. In order to simplify the design, assume that $S < D$. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding. Do not worry about the sizes of the registers or RAM.
12. (16 pts.) Design a circuit that determines how many times a user specified 8-bit value, called **key**, occurs in an $1K \times 8$ RAM. **key** is to be read using a two-line handshake; the

circuit is the passive consumer. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

13. **(16 pts.)** Design a circuit that records the number of times that it has seen an 8-bit, user specified value, **key**. The key will be shown to the circuit, at most, 16 times. The collection of keys is stored in a 1kx12 RAM. The RAM is larger than it needs to be because it is thought that in the future the number of keys will be increased. Each word of the RAM is organized as follows; The upper eight bits hold the key and the lower four bits hold the “hit count”, the number of times that this key has been seen. The circuit should read in the key using a two-line handshake; the circuit is the passive consumer. The circuit should then scan the RAM looking for a matching key; a match, if it exists, will only occur once in the RAM. If a match is found then increment the lower four bit and store the key and the incremented hit count back to RAM. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.
14. **(36 pts.)** Design a digital circuit to control access to an automated parking garage containing 828 parking spaces. Drivers pull up to the garages gate and insert their pass card into a card reader. The card reader sends the pass card ID number to the digital circuit. If their pass card has a valid code then the gate opens. There is a pressure sensor just inside the entry way which sends a signal to the circuit whenever a significant load is present (over 150 lbs). The exit procedure is similar, the users have to insert their pass card into a card reader. The digital circuit then raises the exit gate bar, a pressure sensor at the exit tells the circuit when it is OK to close the exit gate. See Figure 8.33.

 


Figure 8.33: The layout of an automated garage.

The signal names are defined in the following table:

Entrance gate	InGate	0 Close gate	1 Open gate
Entrance sensor	InSen	0 No weight	1 Weight present
Entrance REQ	InREQ	0 No card read data	1 Card reader has data
Entrance ACK	InACK	Circuit control	
Entrance ID	InID	Card ID	
Exit gate	OutGate	0 Close gate	1 Open gate
Exit sensor	OutSen	0 No weight	1 Weight present
Exit REQ	OutREQ	0 No card read data	1 Card reader has data
Exit ACK	OutACK	Circuit control	
Exit ID	OutID	Card ID	

The gate requires a logic 1 to start and to stay open. The sensor will generate a logic 1 while there is more than 150 lbs. on the sensor. Only close the gate when the rear wheels of the car activate the sensor (hope no unicycle use the garage). The entrance card reader will provide InID or OutID using a two-line handshake, where the circuit is the passive consumer. Assume that at any point in time only one car is entering or leaving the garage. That is, deal with only one direction at a time.

In addition to controlling access to the garage, the clients would also like to keep track of how many times a pass ID has been used to gain access in-to and out-of the garage. The count will be checked and reset once a month. Cars pass into and out of the garage at most 4 times a day.

To implement this circuit use a *single* RAM. Each word of the RAM must be divided into three fields; ID, Ins and Outs corresponding to the pass ID number, number of times into the garage and number of times out of the garage respectively. The digital circuit will scan successive IDs in the RAM looking for a match. If a match is found then either increment the Ins or Outs field then store this item back into the RAM. A major issue in this design is determining the sizes of the data items. Use the information in the word statement to make the design as space efficient as possible. Turn in; an algorithm

 


Figure 8.34: The format of the RAM in the garage circuit problem.

the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

15. **(16 pts.)** Design a circuit that converts a 6-bit binary number into a 2 digit BCD representation. The circuit acquires a 6-bit number through a two-line handshake where the circuit is a passive consumer. The circuit is then to convert this 6-bit number into two BCD digits and signals its completion via a DONE signal.

A number X can be converted from binary into BCD digits by iteratively checking that X is greater than 10, then subtracting 10 from X . Each subtraction should increment a tens digit counter.

Make sure to identify the size of all the signals in the datapath and the size of any register, counters, etc... Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

16. **(8 pts.)** Design a circuit that converts a 2 digit BCD number into a binary number. The circuit acquires the BCD digits through 2 read operations most significant digit first. Each read operation takes the form of a two-line handshake where the circuit is a passive consumer.

A 2 digit BCD number can be converted into binary by multiplying the most significant digit by 10 then adding it to the least significant BCD digit. A number can be multiplied by 10 using the shift-and-add technique presented on page ?? . Note, this task can be accomplished without using a single shift register. For example, the adder in Figure 8.35 generates the value of $9 \cdot X$ from a 4-bit register by adding X , shifted left by three bits, to X .

 


Figure 8.35: A simple circuit to compute $9 \cdot X$.

Make sure to identify the size of all the signals in the datapath and the size of any register, counters, etc... Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

17. **(36 pts.)** Design a digital circuit that plays a game of roulette, allows betting and keeps track of total earnings. The roulette wheel has 8 slots, labeled $1 \dots 8$. The player can play one of the numbers straight or play even or odd. The player starts with \$10. The layout of the machine is shown in Figure 8.36.

The sequence of events is as follows:

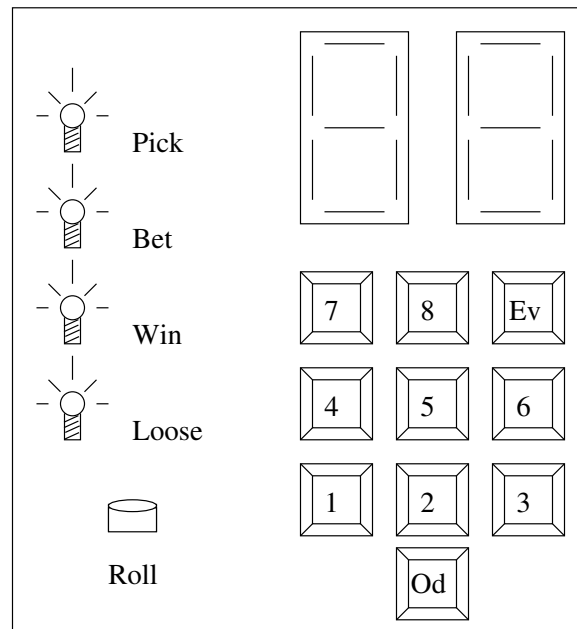


Figure 8.36: The layout of the roulette playing machine. The two 7-segment displays at the top are used for a variety of purposes.

- The circuit lights up the PICK LED. The player enters their guess; a number between 1-8, even or odd. While holding down their guess they press the roll button.
- The circuit displays the picked number in the left most 7-segment display. The circuit lights up the BET LED. The player enters a one digit bet between 1 to 8. While holding down their bet they press the roll button.
- The circuit displays the bet on the rightmost 7-segment display. The player pushes and holds down the roll button. The circuit increments a mod 8 counter while the roll button is depressed. It would be nice to display the current count value on right 7-segment display. Since the clock cycle is on the order of milliseconds, then the user would not be able to anticipate the roll.
- The player releases the roll button. The final roll is displayed on the rightmost 7-segment display. The circuit stops incrementing the counter and checks to see if the final value matches the players guess. If the match is correct then light the WIN LED and increment the players earnings. If the match is incorrect then light the LOOSE LED and decrement the players earnings.
- The player hits the roll button to clear the roll information from the 7-segment displays.
- The circuit displays the players earnings on the 7-segment display.
- When the user pushes the roll button then go to step 1.


Set reasonable bounds on the maximum winnings. Values may be displayed in hexadecimal (assume there is a hex to 7-segment display converter available). See page 25 for more information. Turn in; an algorithm the datapath and control unit, the control word

table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.

Solution

Algorithm

Datapath and Control

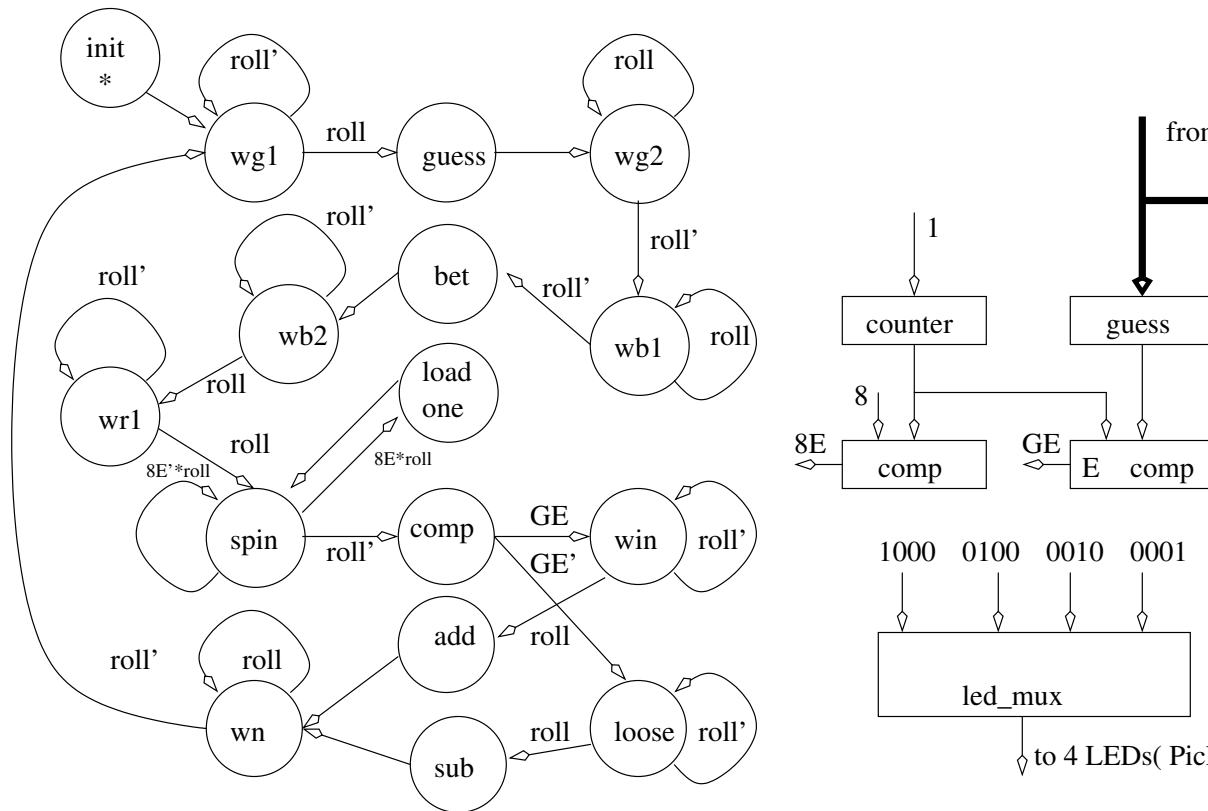

Note from the figure that, the user may acquire up to $0xFF$ cash. Each hex digit of the users total cash will be displayed on its own 7-segment display.

Control Word

State	counter	guess	bet	cmux	bmux	cash	add/sub	ledmux	rmux	lmux
	00 hold	0 hold	0 hold	0 \$10	0 bet	0 hold	0 add	00 (pick)	00 cash	00 cash
	01 load	0 load	1 load	1 add/sub	1 betj2	1 load	1 sub	01 (bet)	01 bet	01 guess
	10 up							10 (win)	10 count	10 blank
								11 (loose)	11 blank	
init	00	0	1	0	x	1	x	00	11	11
wg1	00	0	0	x	x	0	x	00	00	00
guess	00	1	0	x	x	0	x	00	11	01
wg2	00	0	0	x	x	0	x	00	11	01
wb1	00	0	0	x	x	0	x	01	11	01
bet	01	0	1	x	x	0	x	01	11	01
wb2	00	0	0	x	x	0	x	00	01	01
wr1				x	x		x			
spin	10	0	0	x	x	0	x	00	10	01
load 1	01	0	0	x	x	0	x	00	10	01
comp	00	0	0	x	x	0	x	00	10	01
win	00	0	0	1	1	1	0	10	10	01
add										
loose	00	0	0	1	0	1	1	11	10	01
sub										
wn	00	0	0	x	x	0	x	00	00	00

MIEs and OEs**MIE**

$$\begin{aligned}
D_{init} &= 0 \\
D_{wg1} &= Q_{wg1} * roll' + Q_{wn} * roll' \\
D_{guess} &= Q_{wg1} * roll \\
D_{wg2} &= Q_{guess} + Q_{wg2} * roll \\
D_{wb1} &= Q_{wg2} * roll' + Q_{wb1} * roll \\
D_{bet} &= Q_{wb1} * roll' \\
D_{wb2} &= Q_{bet} + Q_{wb2} * roll' \\
D_{spin} &= Q_{wb2} * roll + Q_{spin} * 8E' * roll + Q_{load1} \\
D_{load1} &= Q_{spin} * 8E * roll \\
D_{comp} &= Q_{spin} * roll' \\
D_{win} &= Q_{comp} * GE \\
D_{loose} &= Q_{comp} * GE' \\
D_{wn2} &= Q_{wn} * roll + Q_{win} * roll + Q_{loose} * roll
\end{aligned}$$

OE

$$\begin{aligned}
Q_{c1} &= Q_{spin} \\
Z_{c0} &= Q_{bet} + Q_{load1} \\
Z_{guess} &= Q_{guess} \\
Z_{bet} &= Q_{init} + Q_{bet} \\
Z_{cmux} &= Q_{win} + Q_{loose} \\
Z_{bmux} &= Q_{win} \\
Z_{cash} &= Q_{init} + Q_{win} + Q_{loose} \\
Z_{addsub} &= Q_{loose} \\
Z_{led1} &= Q_{win} + Q_{loose} \\
Z_{led0} &= Q_{wb1} + Q_{bet} + Q_{loose} \\
Z_{rseg1} &= not(Q_{wg1} + Q_{wb2} + Q_{wn}) \\
Z_{rseg0} &= Q_{init, guess, wg2, wb1, bet, wb2} \\
Z_{lseg1} &= Q_{init}
\end{aligned}$$

18. **(20 pts.)** Design a tone generator. The tone generator is a box with two buttons on it labeled “Up” and “Down” and a 1-bit output. At start-up the tone generator outputs a 440Hz square wave (clock-like signal). Every time that the Up button is pressed the tone generator should increase the frequency of the square wave by $\sqrt[12]{2} - 1.0 = 0.059463094 \approx 7/128$ of its current frequency. To determine the fraction $7/128$ of X , shift X left by 7-bits (dividing by 128) then multiplying it by $4+2+1$. Every time that the down button is pressed the circuit should decrease the frequency by $7/128$ of its current value. Assume that the master clock frequency of the circuit is 4Mhz. Turn in any relevant calculations, algorithm, datapath and control, control word, MIEs, OEs and the maximum tone frequency of the circuit. Turn in; an algorithm the datapath and control unit, the control word table, the memory input equations, and output equations. The control unit is to be implemented using a ones hot encoding.