

CMPEN 271 – Fall 2008

Return this exam! No calculators!

Exam 1

Name:

1. **(1 pt.)** Design is ...
 - a) A box whose input and outputs are binary numbers.
 - b) The transformation of a working system into a word statement.
 - c) A boolean variable can equal either 0 or 1.
 - d) One of the representations of a logical function.
 - e) None of the above.
2. **(2 pts.)** Convert 101011_2 to decimal.
 - a) 16
 - b) 24
 - c) 42
 - d) 84
 - e) none of the above
3. **(2 pts.)** Convert 35_{10} to binary.
 - a) 110101_2
 - b) 010111_2
 - c) 111111_2
 - d) 100011_2
 - e) none of the above
4. **(2 pts.)** Convert 35_{16} to decimal.
 - a) 24
 - b) 35
 - c) 48
 - d) 53
 - e) none of the above
5. **(2 pts.)** What is the largest number that you can make with N -bits?
 - a) $\log_2(N)$
 - b) N
 - c) N^2
 - d) $2^N - 1$
 - e) none of the above
6. **(1 pt.)** Which of the following describes a normal design process?
 - a) $WS \rightarrow TT \rightarrow CD \rightarrow Sym$
 - b) $WS \rightarrow Sym \rightarrow TT \rightarrow CD$
 - c) $WS \rightarrow CD \rightarrow Sym \rightarrow TT$
 - d) $WS \rightarrow TT \rightarrow Sym \rightarrow CD$
 - e) $WS \rightarrow Kmap \rightarrow CD$

For questions 7-11 assume $F(A,B,C) = ((A'B)'C + (BC')')'$


7. **(2 pts.)** What does $F(0,1,0)$ equal?
- a) 0
 - b) 1
 - c) C
 - d) C'
 - e) Not enough information.
8. **(2 pts.)** What does $F(1,1,C)$ equal?
- a) 0
 - b) 1
 - c) C
 - d) C'
 - e) Not enough information.
9. **(1 pt.)** How many NOT gates does it take to realize F as is (do not simplify)?
- a) 1
 - b) 2
 - c) 3
 - d) 4
 - e) None of the above.
10. **(1 pt.)** How many OR gates does it take to realize F as is (do not simplify)?
- a) 1
 - b) 2
 - c) 3
 - d) 4
 - e) None of the above.
11. **(2 pts.)** How many AND gates does it take to realize F as is (do not simplify)?
- a) 1
 - b) 2
 - c) 3
 - d) 4
 - e) None of the above.

Utilize the following truth table for problems 12-15.

A	B	C	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

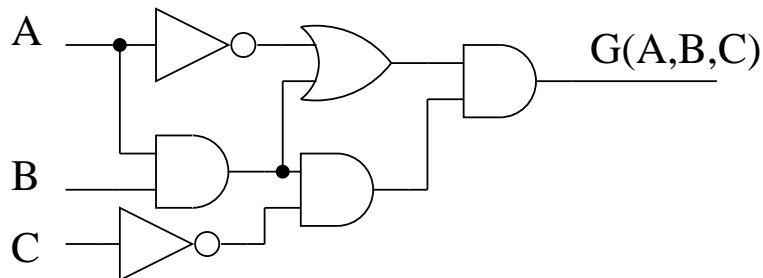12. **(1 pt.)** What function is described by $\sum m(0, 3, 4, 6, 7)$?
 a) F b) F' c) G d) G' e) none of the above
13. **(1 pt.)** What function is described by $\prod M(0, 4, 5)$?
 a) F b) F' c) G d) G' e) none of the above
14. **(1 pt.)** How many product terms does the canonical SOP expression for F' have?
 a) 1 b) 2 c) 3 d) 4 e) 5
15. **(1 pt.)** How many sum terms does the canonical POS expression for G have?
 a) 1 b) 2 c) 3 d) 4 e) 5
16. **(2 pts.)** $A' + AB' = A + B'$
 a) True
 b) False
17. **(3 pts.)** What is the SOP_{\min} expression for $F = AB'(A'C + B') + A'(C + C'B')$?
 a) B'
 b) B' + A'
 c) B' + A'C
 d) AB' + A'C + A'B'
 e) None of the above.

Utilize the following circuit diagram for problems 18,19.



18. (4 pts.) What is the symbolic representation of $G(A,B,C)$ as shown?
- $ABC'(A'+AB)$
 - $(AB+A')C'$
 - $(A'+AB)BC'$
 - ABC'
 - None of the above.
19. (2 pts.) What does $G(0,1,0)$ equal?
- 0
 - 1
20. (1 pt.) A cell in a 8 variable kmap is adjacent to how many other cells?
- 3
 - 8
 - 16
 - 64
 - 256
21. (2 pts.) How many different SOP_{\min} solutions exist for $F(A,B,C)=\Sigma m(0,2,5,6,7)$?
- 1
 - 2
 - 3
 - 4
 - 5

$A \backslash BC$	00	01	11	10
0				
1				

22. (4 pts.) Determine the SOP_{\min} expression for $F(A,B,C,D)=\sum m(0,1,5,6,7,8,9,14)$

- a) $A'B'C' + A'BD + BCD' + AB'C'$
 b) $B'C' + A'BD + BCD'$
 c) $A'C'D + BCD' + B'C'$
 d) $B'C'D' + B'C'D + A'BD + BCD'$
 e) None of the above.

$AB \backslash CD$	00	01	11	10
00				
01				
11				
10				

23. (4 pts.) Determine the SOP_{\min} realization for F.

A	B	C	F
0	0	X	1
1	0	0	0
1	1	X	X
0	X	0	1
1	0	1	0
X	1	1	X

$A \backslash BC$	00	01	11	10
0				
1				

- a) $A' + B$
 b) $A + BC'$
 c) $A + C'$
 d) $A'BC' + A'B'$
 e) None of the above.
24. (6 pts.) Determine the POS_{\min} expression for $F(A,B,C,D) = (A' + D)(A' + B' + C')(A + B + D')(B' + C' + D')(A + B' + C + D')$, show your work.