

CSE 271 – Fall 2004

Exam 2

Name:

SSN:

D	Q+	T	Q+	S	R	Q+	J	K	Q+
0	0	0	Q	0	0	Q	0	0	Q
0	1	0	Q	0	1	0	0	1	0
1	1	1	Q'	1	0	1	1	0	1
				1	1	x	1	1	Q'

All counter in this exam are 4-bits wide and have the following behavior.

clk	C_1C_0	D	Q^+
0,1,↓	xx	x	Q
↑	00	x	Q
↑	01	x	$Q+1$
↑	10	x	$Q-1$
↑	11	D	D


All shift registers in this exam are 4-bits wide and have the following behavior.

clk	C_1C_0	D	Q^+	comment
0,1,↓	xx	x	Q	hold
↑	00	x	Q	hold
↑	01	x	$Q \gg 1$	shift right
↑	10	x	$Q \ll 1$	shift left
↑	11	D	D	parallel load

- (1 pt.) Assuming a word size of 5 bits, interpret 10101 as a 2's complement number.
a) -21 b) -11 c) -10 d) -5 e) None of the above
- (1 pt.) Assuming a word size of 5 bits, determine the 2's complement representation of -12.
a) 10100 b) 11100 c) 10011 d) 10010 e) None of the above
- (1 pt.) How many OR gates are there inside a 3:8 decoder?
a) 1 b) 3 c) 8 d) 16 e) None of the above
- (1 pt.) How many inputs do the AND gates inside a 3:8 decoder have?
a) 1 b) 3 c) 4 d) 8 e) None of the above
- (1 pt.) How many AND gates are there in an 8:1 mux?
a) 1 b) 2 c) 3 d) 8 e) None of the above

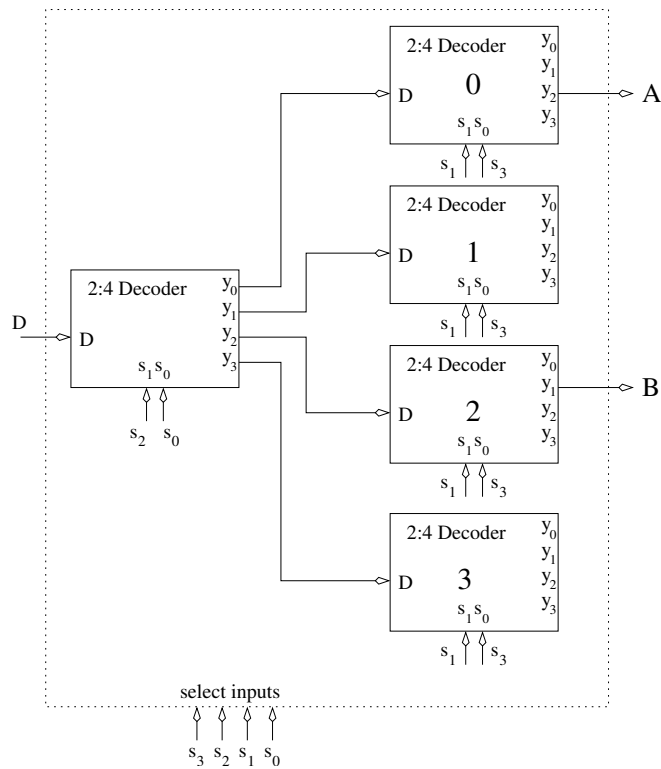
6. (1 pt.) How many 2:1 muxes are needed to construct a 64x1 mux?
 a) 31 b) 32 c) 63 d) 64 e) None of the above

You are given the following 4:16 decoder built from 2:4 decoders. Unfortunately, the student who built it wired the select lines in a most unusual fashion. Its your job to label each output with the index which selects it. Most of the outputs have been omitted for clarity.




7. (1 pt.) What is the value of the output labeled A?
 a) y_1 b) y_2 c) y_4 d) y_8 e) None of the above
8. (1 pt.) What is the value of the output labeled B?
 a) y_1 b) y_6 c) y_9 d) y_{12} e) None of the above

 9. (2 pt.) Which line of pseudo-code best characterizes the following piece of hardware.



 - a) if ($X < Y$) then $Z = X+3$ else $Z = Y+3$;
- b) if ($X < Y$) then $Z = Y+3$ else $Z = X+3$;
- c) if ($X > Y$) then $Z = X+3$ else $Z = Y+3$;
- d) if ($X > Y$) then $Z = Y+3$ else $Z = X+3$;
- e) None of the above


For questions 10-11 you are to complete the state table for the following circuit.



- 10. (1 pt.) What does G^+ equal for $(A,B)=(0,0)$?
 - a) 0 b) 1 c) F d) F' e) illegal
- 11. (1 pt.) What does F^+ equal for $(A,B)=(1,1)$?
 - a) 0 b) 1 c) F d) F' e) illegal
- 12. (2 pt.) What is the logic inside **box** in order to make the count sequence on Q go from 3 to 10 (inclusive of both) over and over.

 
- a) $c_1 = L'$ $c_0 = 0$
- b) $c_1 = L'$ $c_0 = 1$
- c) $c_1 = L$ $c_0 = 0$
- d) $c_1 = L$ $c_0 = 1$
- e) None of the above

For questions 13-16 use the circuit and timing diagram show below. If necessary, you can assume that Q settles to 0 after a period of rapid toggling.



 
13. (1 pt.) What is the value of Q_1 at time=25nS?
 a) 0 b) 1 c) Toggling rapidly d) Unknown
14. (1 pt.) What is the value of Q_1 at time=75nS?
 a) 0 b) 1 c) Toggling rapidly d) Unknown
15. (1 pt.) What is the value of Q_2 at time=15nS?
 a) 0 b) 1 c) Toggling rapidly d) Unknown
16. (1 pt.) What is the value of Q_2 at time=45nS?
 a) 0 b) 1 c) Toggling rapidly d) Unknown

For problems 17-19 use the timing diagram below as the input to a counter.
Determine the output sequence Q to answer the questions below.



 
17. (1 pt.) What is the value of Q at time 15?
 a) 0000 b) 0001 c) 1110 d) 1111 e) None of the above
18. (1 pt.) What is the value of Q at time 65?
 a) 0000 b) 0001 c) 1110 d) 1111 e) None of the above
19. (1 pt.) What is the value of Q at time 85?
 a) 0000 b) 0001 c) 1110 d) 1111 e) None of the above

For problems 20-22 use the timing diagram below as the input to an arithmetic shift register. Determine the output sequence Q to answer the questions below.



 20. (1 pt.) What is the value of Q at time 25?
 a) 0000 b) 0111 c) 1110 d) 1111 e) None of the above
21. (1 pt.) What is the value of Q at time 65?
 a) 0000 b) 0111 c) 0110 d) 1110 e) None of the above
22. (1 pt.) What is the value of Q at time 85?
 a) 0000 b) 0111 c) 0110 d) 1110 e) None of the above

For problems 23-27 use the following figure and timing diagram. You should assume that all the devices process 5-bits data values.



23. **(2 pt.)**What is the value of P at time 15?
a) 0 b) 2 c) 3 d) 5 e) 8
24. **(2 pt.)**What is the value of A_0 at time 25?
a) 7 b) 8 c) 11 d) 13 e) 16
25. **(2 pt.)**What is the value of Q at time 35?
a) 7 b) 8 c) 11 d) 13 e) 16
26. **(2 pt.)**What is the value of A_1 at time 45?
a) 8 b) 10 c) 13 d) 16 e) 19
27. **(2 pt.)**What is the value of M at time 55?
a) 2 b) 8 c) 10 d) 11 e) 12