

Counter counts up/down from 0 to $2^N - 1$

N-bit counter w/ parallel load

Data in : N-bit \bar{D}


Data out : N-bit \bar{Q}

Control : 2-bit \bar{C}


Status : None (for now)

Behavior

reset	clk	Q	D	Q^+	comment
0	x	x	x	$\bar{0}$	
1	0, 1, ↓	x	x	Q	
1	↑	00	x	Q	hold
1	↑	01	D	D	load
1	↑	10	x	$Q+1$	up
1	↑	11	x	$Q-1$	down

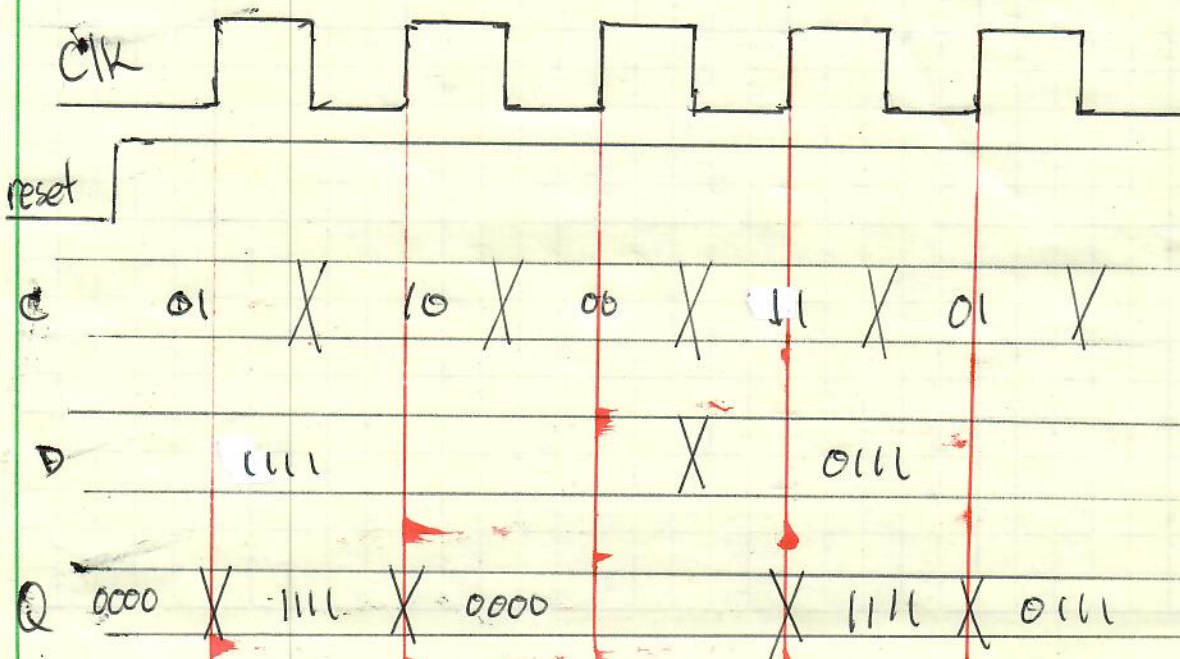

Internal organization of 4-bit

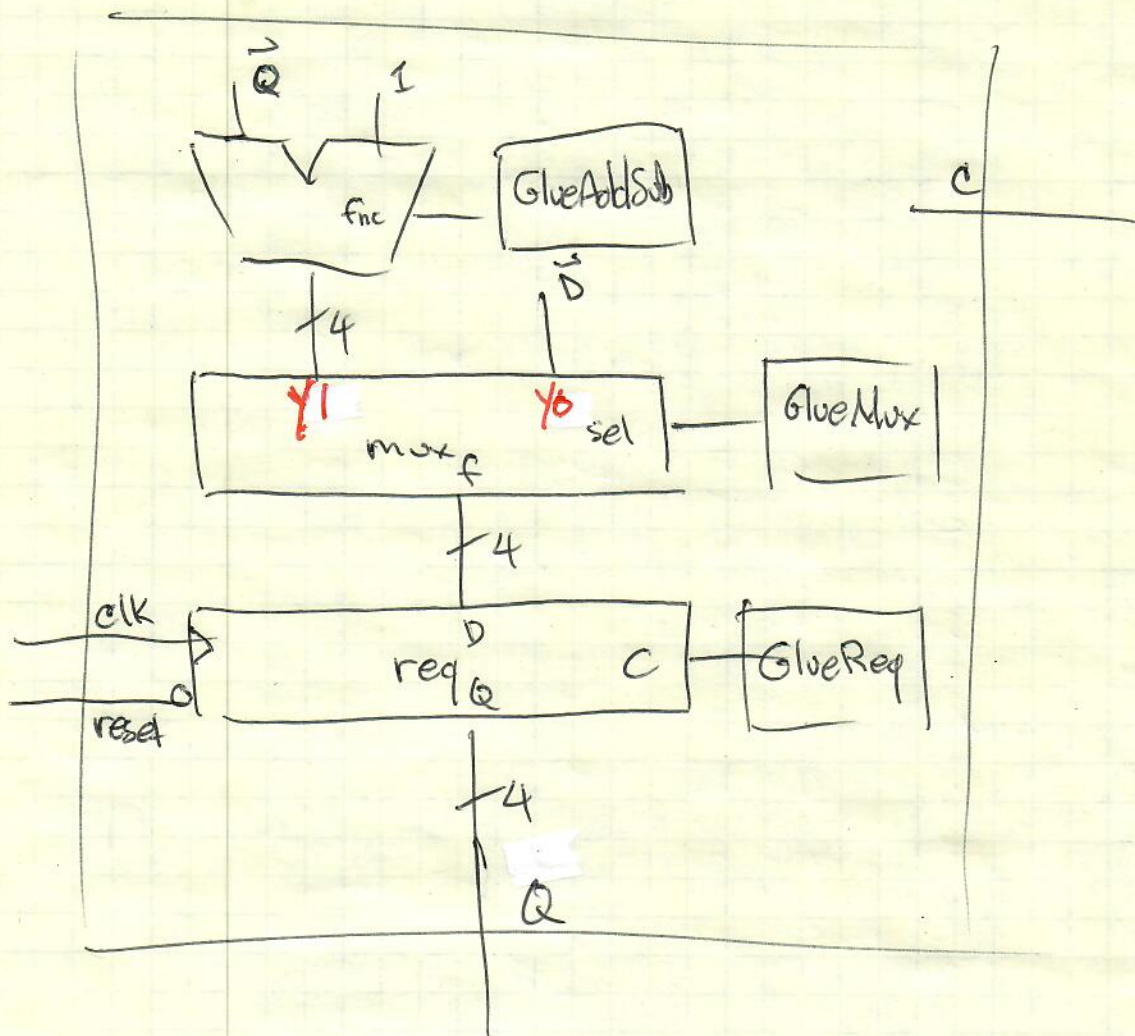

c	GlueAddSub	GlueMux	GlueReg
0 0	X	X	0
0 1	X	0	1
1 0	0	1	1
1 1	1	1	1

Add logic for rollover

rollover = 1 when ($\bar{Q} = 1111$ and $C = 10$) or
($\bar{Q} = 0000$ and $C = 11$)

