

CMPEN 270 – Fall 2015

Exam 2

Name:

PSU ID:


1. **(3 pts.)** Assuming a word size of 5 bits, interpret 10110 as a 2's complement number.
 a) -9 b) -10 c) -5 d) 22 e) None of the above.
2. **(3 pts.)** Assuming a word size of 5 bits, determine the 2's complement representation of -9.
 a) 11011 b) 10111 c) 10110 d) 11001 e) None of the above.
3. **(4 pts.)** How many inputs do the AND gates in a 32:1 mux have?
 a) 5 b) 6 c) 31 d) 32 e) None of the above.
4. **(3 pts.)** How many 2:1 muxes does it take to build a 32:1 mux?
 a) 3 b) 7 c) 15 d) 31 e) None of the above.

Questions 5-7 concern the construction of a bit-slice of a comparator. The questions will ask you to complete the entries in the truth table below denoted by a , b , and c .


G_{in}	L_{in}	E_{in}	x	y	G_{out}	L_{out}	E_{out}
0	0	1	1	1	a		
1	0	0	0	1		b	
1	0	1	1	0			c

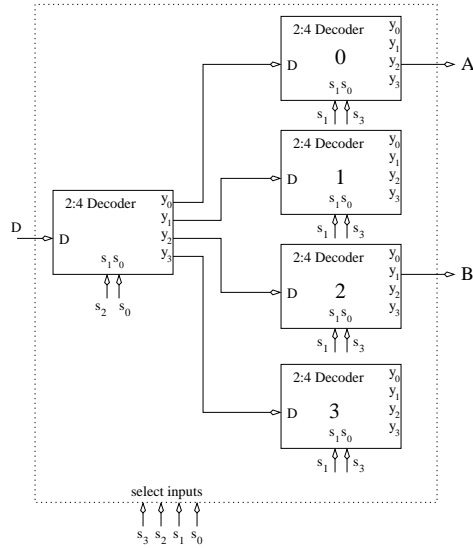5. **(2 pts.)** What is the value of a ?
 a) 0 b) 1 c) x
6. **(2 pts.)** What is the value of b ?
 a) 0 b) 1 c) x
7. **(2 pts.)** What is the value of c ?
 a) 0 b) 1 c) x

You are given the following 4:16 decoder built from 2:4 decoders. Unfortunately, the student who built it wired the select lines in a most unusual fashion. Its your job to label each output with the index which selects it. Most of the outputs have been omitted for clarity.



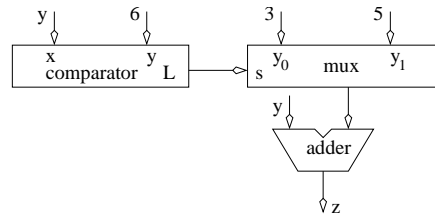8. **(3 pts.)** What is the value of the output labeled A?
 a) y_1 b) y_2 c) y_4 d) y_8 e) None of the above
9. **(3 pts.)** What is the value of the output labeled B?
 a) y_1 b) y_6 c) y_9 d) y_{12} e) None of the above
10. **(5 pts.)** Which line of pseudo-code is equivalent to the following piece of hardware. Y is a 4-bit binary number.




- a) if (5 < Y) then Z = X+3 else Z = Y+5;
- b) if (6 < Y) then Z = Y+3 else Z = Y+5;
- c) if (6 > Y) then Z = X+3 else Z = Y+5;
- d) if (5 > Y) then Z = Y+3 else Z = Y+5;

You have a digital design which calls for a circuit which performs the following task (written as a C if/then statement). You have decided on the architecture. Its your job to design to complete the truth table for the glue-logic box (only an arbitrary portion of the complete truth table is shown).

```

if      (sum > 18) z = sum-18
else if (sum > 12) z = sum-12
else if (sum > 6)  z = sum-6
else          z = sum

```

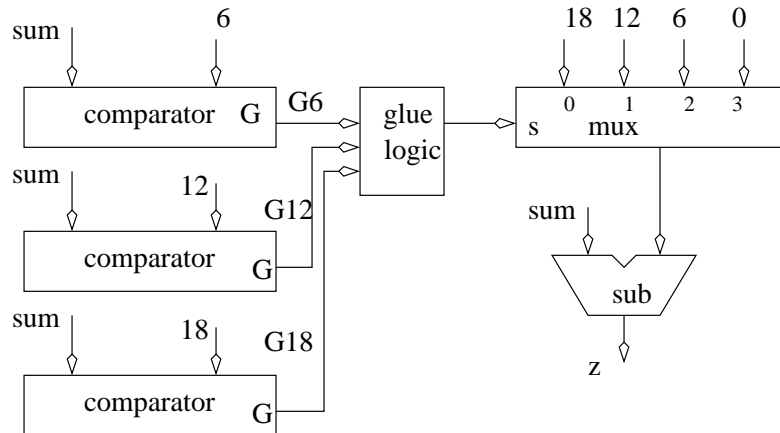


G6	G12	G18	select
0	0	0	a
1	1	0	b
1	0	1	c

11. **(3 pts.)**What is the (decimal) value of a in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x
12. **(3 pts.)**What is the (decimal) value of b in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x
13. **(3 pts.)**What is the (decimal) value of c in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x


D	Q+	T	Q+	S	R	Q+	J	K	Q+
0	0	0	Q	0	0	Q	0	0	Q
1	1	1	Q'	0	1	0	0	1	0
				1	0	1	1	0	1
				1	1	x	1	1	Q'

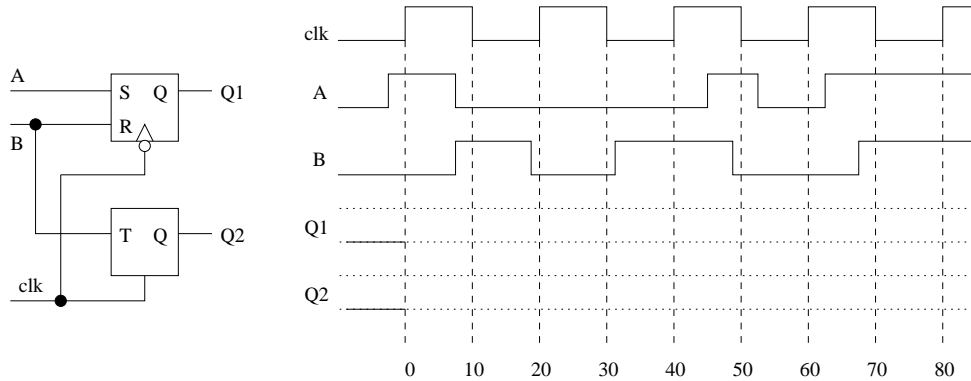For questions 14-19 use the following figure. Assume that initial value of Q is 0 (as shown in the figure), and that the outputs, after a period of rapid toggling, end-up at 0.



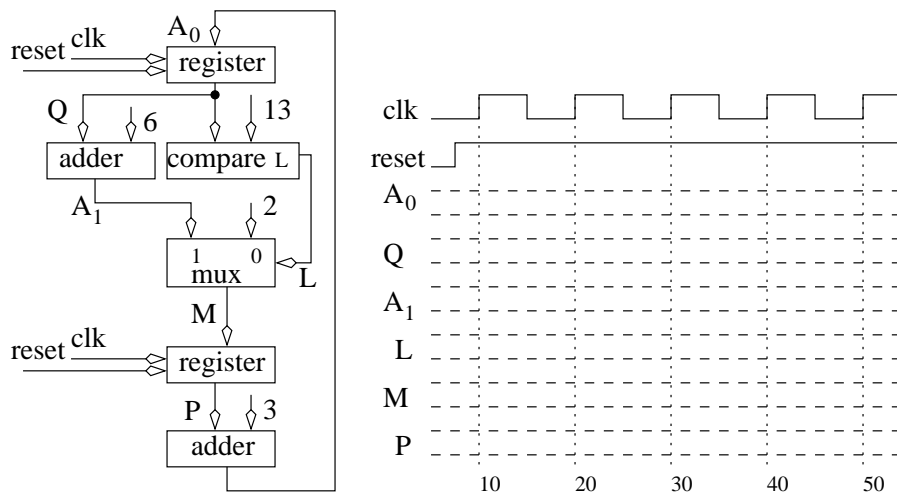14. (3 pts.) What is the value of Q1 at time 25
a) 0 b) 1 c) toggling d) unknown
15. (2 pts.) What is the value of Q1 at time 35
a) 0 b) 1 c) toggling d) unknown
16. (1 pt.) What is the value of Q1 at time 65
a) 0 b) 1 c) toggling d) unknown
17. (2 pts.) What is the value of Q2 at time 25
a) 0 b) 1 c) toggling d) unknown
18. (1 pts.) What is the value of Q2 at time 45
a) 0 b) 1 c) toggling d) unknown

For problems 19-23 use the following figure and timing diagram. You should assume that all the devices process 5-bits data values.



19. (5 pts.) What is the value of Q at time 15?
 - a) 0
 - b) 3
 - c) 6
 - d) 9
 - e) none of the above
20. (4 pts.) What is the value of P at time 25?
 - a) 2
 - b) 9
 - c) 12
 - d) 15
 - e) none of the above
21. (3 pts.) What is the value of A_1 at time 35?
 - a) 5
 - b) 9
 - c) 12
 - d) 18
 - e) none of the above
22. (2 pts.) What is the value of M at time 45?
 - a) 2
 - b) 5
 - c) 11
 - d) 12
 - e) none of the above
23. (1 pts.) What is the value of Q at time 55?
 - a) 5
 - b) 11
 - c) 12
 - d) 14
 - e) none of the above