

EENG 284 – Spring 2024
Exam 1

Name:

CWID:

Clearly circle your answer to each question.

1. **(2 pts.)** Convert 101000_2 to decimal.
a) 20 b) 24 c) 40 d) 42 e) none of the above
2. **(2 pts.)** Convert 42_{10} to binary.
a) 010010_2 b) 100010_2 c) 100110_2 d) 100100_2 e) none of the above
3. **(2 pts.)** Convert 42_{16} to binary.
a) b) c) 1000110_2 d) e) none of the above
 1000010_2 1000100_2 1001000_2
4. **(2 pts.)** How many bits do you need to represent the number 48?
a) 4 b) 5 c) 6 d) 7 e) none of the above
5. **(1 pts.)** When represented as 4-bit binary numbers does $12 + 4$ generate overflow?
a) yes b) no c) Trick question, 12 cannot be represented in 4-bit
6. **(2 pt.)** Which expression is equivalent to $(A' + B)'(B + AC)$?
a) 0
b) 1
c) $AB'C$
d) $AB' + AB'C$
e) None of the above

For questions 7-10 let $F(A,B,C) = A'B + A(B' + BC')$

7. **(2 pts.)** What does $F(0,1,0)$ equal?
 a) 0 b) 1 c) C d) C' e) none of these
8. **(1 pts.)** What does $F(1,1,C)$ equal?
 a) 0 b) 1 c) C d) C' e) none of these
9. **(2 pts.)** How many AND gates does it take to realize F as is (do not simplify)?
 a) 1 b) 2 c) 3 d) 4 e) none of these
10. **(2 pts.)** How many OR gates does it take to realize F as is (do not simplify)?
 a) 1 b) 2 c) 4 d) 5 e) none of these

Utilize the following truth table for problems 11 and 12.

| A | B | C | F | G |
|---|---|---|---|---|
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 |

11. **(2 pts.)** What function is described by $\prod M(0,3,4,6,7)$?
 a) F b) F' c) G d) G' e) none of the above
12. **(2 pts.)** How many sum terms does the canonical POS expression for F have?
 a) 1 b) 2 c) 3 d) 4 e) 5
13. **(3 pts.)** How many different SOP_{\min} solutions exist for $F(A,B,C) = \sum m(1,3,4,5,6)$?
 a) 1 b) 2 c) 3 d) 4 e) 5

| A\BC | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

Utilize the following word statement for problems 14 and 15.


Design a 4-input $a_1a_0b_1b_0$, two output o_1o_0 digital circuit. $A = a_1a_0$ and $B = b_1b_0$ represent 2-bit binary numbers. The output is the smaller (or either if a same) of A and B . For example, if $A = 10$ and $B = 01$, then $O = 01$.

14. (2 pt.) How many rows of the truth table have $O_1 = 1$?
 a) 1 b) 4 c) 9 d) 12 e) None of the above.
15. (2 pt.) How many rows of the truth table have $O_0 = 0$?
 a) 1 b) 4 c) 9 d) 12 e) None of the above.
16. (1 pt.) A grouping of 4 cells generates a product term with 4 variables. How many variables does the kmap have?
 a) 3 b) 4 c) 5 d) 6 e) None of the above.

| a_1 | a_0 | b_1 | b_0 | o_1 | o_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | | |
| 0 | 0 | 0 | 1 | | |
| 0 | 0 | 1 | 0 | | |
| 0 | 0 | 1 | 1 | | |
| 0 | 1 | 0 | 0 | | |
| 0 | 1 | 0 | 1 | | |
| 0 | 1 | 1 | 1 | | |
| 1 | 0 | 0 | 0 | | |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | | |
| 1 | 0 | 1 | 1 | | |
| 1 | 1 | 0 | 0 | | |
| 1 | 1 | 0 | 1 | | |
| 1 | 1 | 1 | 0 | | |
| 1 | 1 | 1 | 1 | | |

Truth Table for O

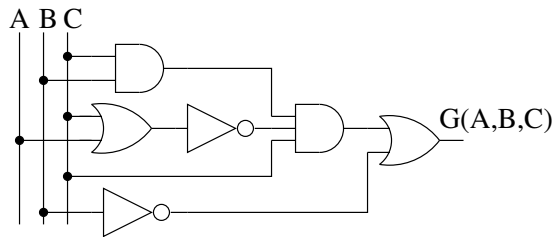For questions 17,18 use the figure below.



17. (2 pt.) What is the symbolic representation of $G(A, B, C)$ (do not simplify).
 a) $BC + (A + C)' + B'$
 b) $BC(A+C)' + B'$
 c) $BC(A+C)'C + B'$
 d) B'
 e) None of the above.
18. (2 pt.) What is $G(1,1,0)=$?
 a) 1
 b) 0

19. **(3 pts.)** Determine the SOP_{min} expression for
 $F(A,B,C,D) = \sum m(1, 5, 7, 8, 9, 14) \sum d(0, 6, 12, 13)$

| $AB \backslash CD$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

- a) $AC' + C'D + A'BC + BCD'$
- b) $B'C' + A'BD + BCD'$
- c) $A'C'D + BCD' + B'C'$
- d) $B'C'D' + B'C'D + A'BD + BCD'$
- e) None of the above.

20. **(3 pt.)** Determine the SOP_{min} expression for
 $F(A,B,C,D) = AB'C' + A'B'D + CD + A'B'CD'$

| $AB \backslash CD$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

- a) $A'B'D + A'B'C + ACD + AB'C'D' + AB'CD'$
- b) $A'B'C + AB'C' + B'D + CD$
- c) $A'B'C + A'BD + AB'C' + AB'D + CD$
- d) $A'B' + AB' + CD$
- e) None of the above.

21. **(3 pt.)** Determine the POS_{min} expression for
 $F(A,B,C,D) = (A+B'+D)(B+C')(B'+C'+D)$

| $AB \backslash CD$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

- a) $(B+C')(A+B'+D')(C'+D)$
- b) $(B+C'+D')(C'+D)(A+B'+D)$
- c) $(A+B'+D)(B+C')(B'+C'+D)$
- d) $(B+C)(A'+C)(B+D)$
- e) None of the above.

| $AB \backslash CD$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |