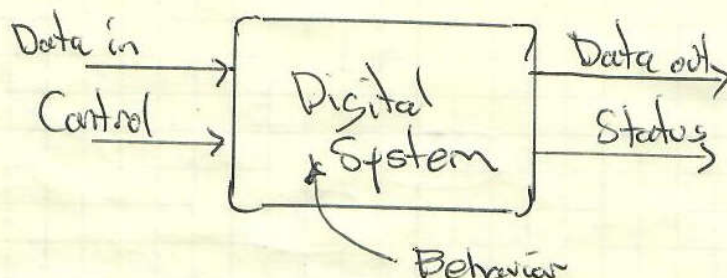


Combinational logic building blocks

Refine our view of the input & output: The transformation of **input to output data** is determined by **control inputs**. Exceptional processing events are reported by **status outputs**.



N:M Decoder

Data input : 1-bit D

Data output : M bits $Y = y_{M-1} \dots y_1 y_0$

Control : N-bit $S = s_{N-1} \dots s_1 s_0$

Status : None

Behavior : $y_s = D$, all other $y_i = 0$

Truth Table for 2:4 decoder

s_1	s_0	D	y_3	y_2	y_1	y_0
0	0	0				
0	0	1				1
0	1	0				
0	1	1			1	
1	0	0				
1	0	1		1		
1	1	0				
1	1	1	1			

$$y_0 = s_1' s_0' D$$


$$y_1 = s_1' s_0 D$$

$$y_2 = s_1 s_0' D$$

$$y_3 = s_1 s_0 D$$

Build larger decoder from a collection of smaller decoders.

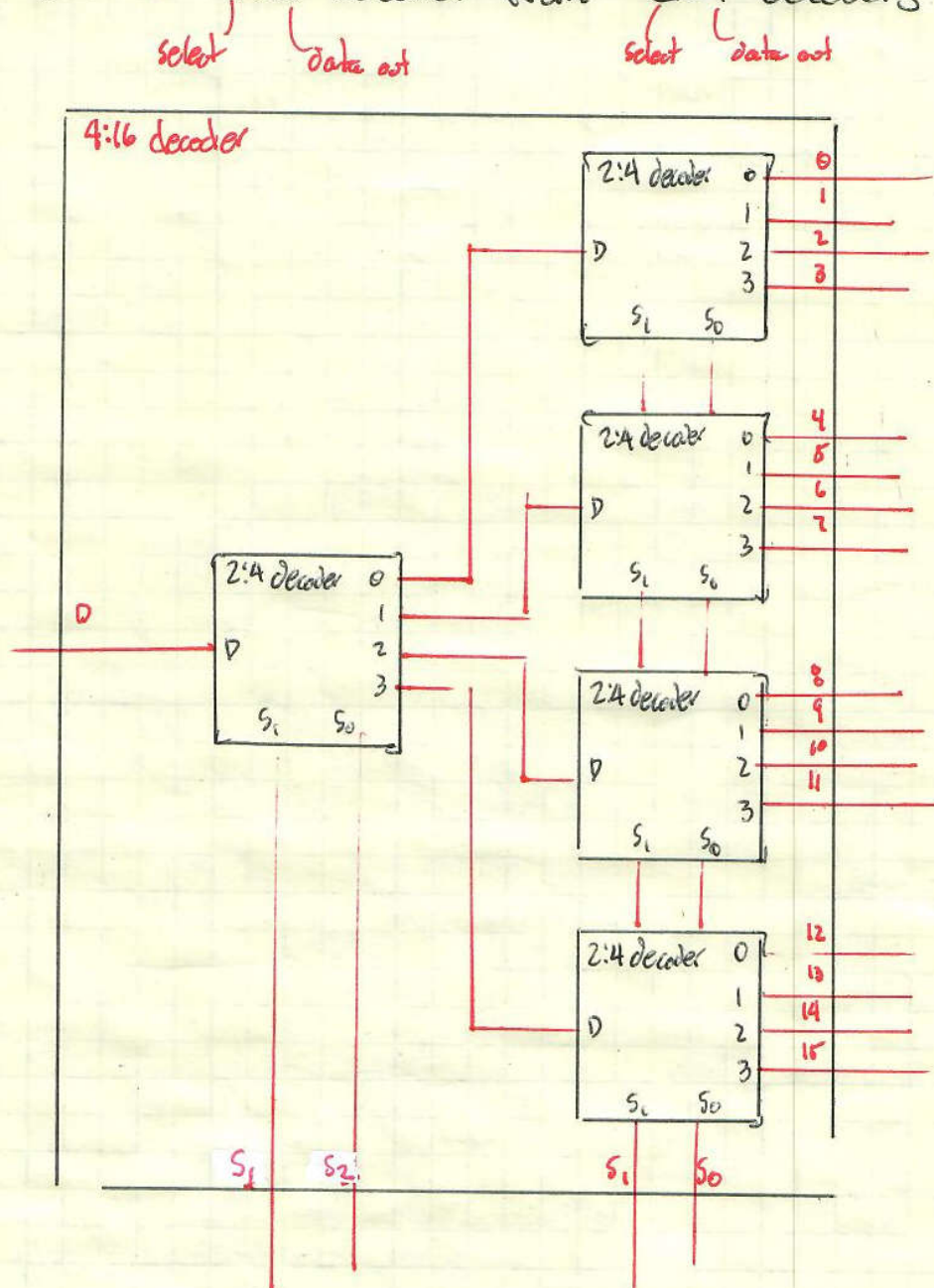Ex: Build a 4:16 decoder from 2:4 decoders




Exam Grand Rules

- Exam is online on Canvas
- Do not have to show up to class room
- I will be on Zoom to answer any questions
- Held during normal class hours
- Exam opens @ 8:55 w/ 60 minutes due @ 10:15
- Once you start you cannot pause exam
- Mostly multiple choice
- 1 3x5 card

Topics

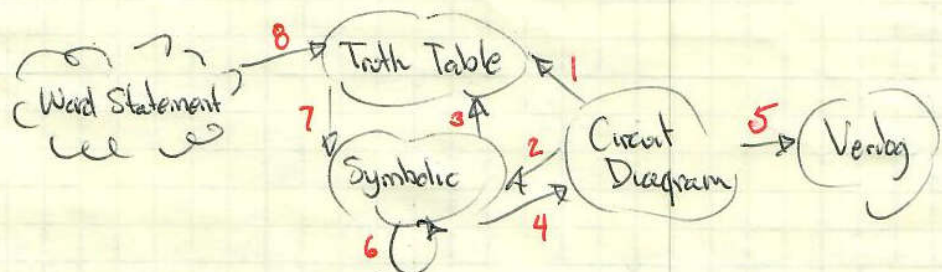- Numbers Binary \leftrightarrow Hex \leftrightarrow Decimal
N-bits has 2^N representations
Word size & overflow
- Addition
- 5 representations of logic functions



1, 2
3, 4
5
6
7
8

Push bits/symbols through circuit
Operator precedence
CSA, testbench, waveforms
Boolean Algebra Bulldozer = convert problems to fully populated
Minterms Maxterms
Multiple input and output

- Kmap

3, 4, 5 var
Don't cares

SOP
POS
SOPmin
POSmin
SOPmax
POSmax
ITM

- Determine the truth table for a function with 4 bits of input a, a_0, b, b_0 and 4 bits of output. Let $A = a, a_0$ and $B = b, b_0$ each represent 2-bit binary numbers. Let $X = x_3, x_2, x_1, x_0$ represent a 4-bit binary number. The behavior of the circuit is given by the equation

$$X = A * B;$$

a, a_0, b, b_0	x_3, x_2, x_1, x_0
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 0
0 0 1 0	0 0 0 0
0 0 1 1	0 0 0 0
0 1 0 0	0 0 0 0
0 1 0 1	0 0 0 1
0 1 1 0	0 0 1 0
0 1 1 1	0 0 1 1

- Determine the POS min expression for $F(A, B, C) = \Pi M(0, 1, 4, 6)$

Step	1	2	3	4	5	6
Function	ΠM	Σm	Kmap	Kmap	SOP min	POS min
Form	F	F	F	F'	F'	F

$$\textcircled{1} F(A, B, C) = \Pi M(0, 1, 4, 6)$$

$$\textcircled{2} F(A, B, C) = \Sigma m(2, 3, 5, 7)$$

$$\textcircled{3}$$

	BC	00	01	11	10
A	0			1	1
1		1	1		

F

$$\textcircled{4}$$

	BC	00	01	11	10
A	0			1	1
1		1	1		

F'

$$\textcircled{5} F' = A'B' + AC'$$

$$\textcircled{6} F = (A+B)(A'+C)$$