

# CMPEN 271 – Spring 2012

Return this exam! No calculators!

Exam 1

Name:

1. **(2 pts.)** Convert  $100100_2$  to decimal.  
a) 20            b) 24            c) 40            d) 42            e) none of the above
2. **(2 pts.)** Convert  $36_{10}$  to binary.  
a)  $010010_2$     b)  $100010_2$     c)  $100110_2$     d)  $100100_2$     e) none of the above
3. **(2 pts.)** Convert  $36_{16}$  to binary.  
a)  $110010_2$     b)  $110100_2$     c)  $110110_2$     d)  $111000_2$     e) none of the above
4. **(2 pts.)** How many bits are required to represent the numbers between 0 and  $78_{10}$ ?  
a) 6            b) 7            c) 78            d)  $2^{78}$             e) none of the above
5. **(1 pts.)** When represented as 4-bit binary numbers does  $12 + 4$  generate overflow?  
a) yes            b) no c) Trick question, 12 cannot be represented in 4-bit
6. **(1 pt.)** How many 1's does the output column in a truth table for a 5-input NAND gate have?  
a) 0            b) 1            c) 5            d)  $2^5 - 1$             e)  $2^5$
7. **(1 pt.)** Which expression is equivalent to  $(A' + B)'(B' + AC)$ ?  
a) 0  
b) 1  
c)  $AB'$   
d)  $A'B + A'BC'$   
e)  $AB' + A'BC'$

For questions 8-11 assume  $F(A,B,C) = (A+B')C' + AB'C$

8. **(2 pts.)** What does  $F(1,1,0)$  equal?  
 a) 0                      b) 1                      c) C                      d) C'                      e) none of these
9. **(2 pts.)** What does  $F(1,0,C)$  equal?  
 a) 0                      b) 1                      c) C                      d) C'                      e) none of these
10. **(1 pt.)** How many AND gates does it take to realize F as is (do not simplify)?  
 a) 1                      b) 2                      c) 3                      d) 4                      e) none of these
11. **(1 pt.)** How many OR gates does it take to realize F as is (do not simplify)?  
 a) 1                      b) 2                      c) 4                      d) 5                      e) none of these

Utilize the following truth table for problems 12,13.

A	B	C	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0


12. **(1 pt.)** What function is described by  $\prod M(0,4,5)$ ?  
 a) F                      b) F'                      c) G                      d) G'                      e) none of the above
13. **(1 pt.)** How many product terms does the canonical SOP expression for F have?  
 a) 1                      b) 2                      c) 3                      d) 4                      e) 5

Utilize the following word statement for problems 14-15.

Design a 4-input  $a_1a_0b_1b_0$ , 4-output  $O_3O_2O_1O_0$  digital system.  $A = a_1a_0$  and  $B = b_1b_0$  represent 2-bit binary numbers. The output should be the product (multiplication) of the inputs plus 5, that is  $O = A * B + 5$ .

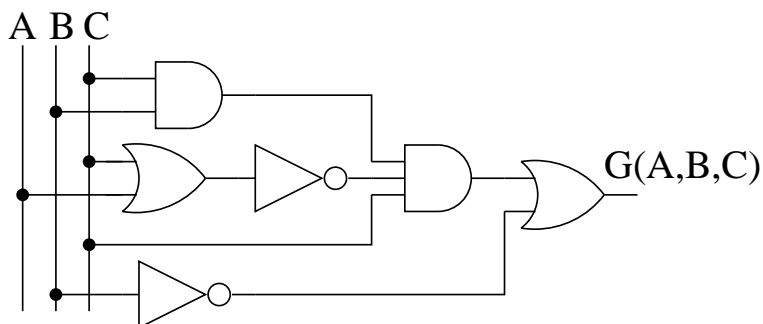14. **(1 pt.)**How many rows will have the output 1011<sub>2</sub>?  
 a) 0                      b) 1                      c) 2                      d) 3                      e) None of the above.
15. **(1 pt.)**How many rows of the truth table will have  $O_0 = 1$ ?  
 a) 1                      b) 3                      c) 9                      d) 12                      e) None of the above.

Utilize the following circuit diagram for problems 16,17.



16. (4 pts.) What is the symbolic representation of  $G(A,B,C)$  as shown?

- a)  $B'$
- b)  $BC + (B+C)C + B'$
- c)  $(BC)(A'C')C + B'$
- d)  $(BC)(A+C)'C + B'$
- e) None of the above.

17. (2 pts.) What does  $G(0,1,0)$  equal?

- a) 0
- b) 1
- c) None of the above

18. (4 pt.) Determine the  $SOP_{min}$  expression for  $F(A,B,C,D)=\Sigma m(0,6,8,10,13,14,15)$

- a)  $BCD' + ACD' + ABC' + A'B'C'D' + AB'C'D'$
- b)  $BCD' + ACD' + ABC' + B'C'D'$
- c)  $B'C'D' + AB'D' + BC''D' + ABD$
- d)  $CD' + AB + B'C'D'$
- e) None of the above.

$AB \backslash CD$	00	01	11	10
00				
01				
11				
10				

19. (4 pt.) Determine the  $SOP_{min}$  expression for  $F(A,B,C,D)=\Sigma m(3,6,9,12) + \Sigma d(0,4,7,8,14)$

- a)  $C'D' + AB' A'CD + BCD'$
- b)  $A'C' + A'B'D' + BC'D + AB'C$
- c)  $BD' + A'CD + AB'C'$
- d)  $BC'D' + AB'C' + A'CD + BCD'$
- e) None of the above.

$AB \backslash CD$	00	01	11	10
00				
01				
11				
10				

20. (4 pt.) Determine the  $\text{POS}_{\min}$  expression for  
 $F(A,B,C,D) = (A+B'+D)(B+C')(B'+C'+D)$

- a)  $(B+C')(A+B'+D')(C'+D)$
- b)  $(B+C'+D')(C'+D)(A+B'+D)$
- c)  $(A+B'+D)(B+C')(B'+C'+D)$
- d)  $(B+C)(A'+C)(B'+D)$
- e) None of the above.

$AB \backslash CD$	00	01	11	10
00				
01				
11				
10				

$AB \backslash CD$	00	01	11	10
00				
01				
11				
10				