

# CMPEN 271 – Fall 2010

## Exam 2

Name:

PSU ID:


1. **(3 pts.)** Assuming a word size of 5 bits, interpret 10110 as a 2's complement number.  
 a) -9            b) -10            c) -5            d) 22            e) None of the above.
2. **(3 pts.)** Assuming a word size of 5 bits, determine the 2's complement representation of -9.  
 a) 11011    b) 10111    c) 10110    d) 11001    e) None of the above.
3. **(4 pts.)** How many inputs do the AND gates in a 32:1 mux have?  
 a) 5            b) 6            c) 31            d) 32            e) None of the above.
4. **(3 pts.)** How many 2:1 muxes does it take to build a 32:1 mux?  
 a) 3            b) 7            c) 15            d) 31            e) None of the above.

Questions 5-7 concern the construction of a bit-slice of a comparator. The questions will ask you to complete the entries in the truth table below denoted by  $a$ ,  $b$ , and  $c$ .


$G_{in}$	$L_{in}$	$E_{in}$	$x$	$y$	$G_{out}$	$L_{out}$	$E_{out}$
0	0	1	1	1	$a$		
1	0	0	0	1		$b$	
1	0	1	1	0			$c$

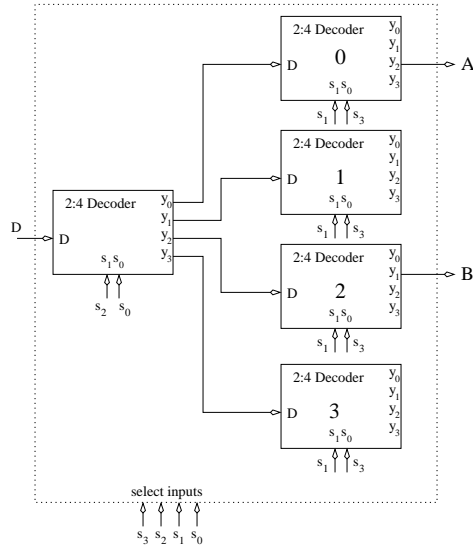5. **(2 pts.)** What is the value of  $a$ ?  
 a) 0            b) 1            c) x
6. **(2 pts.)** What is the value of  $b$ ?  
 a) 0            b) 1            c) x
7. **(2 pts.)** What is the value of  $c$ ?  
 a) 0            b) 1            c) x

You are given the following 4:16 decoder built from 2:4 decoders. Unfortunately, the student who built it wired the select lines in a most unusual fashion. Its your job to label each output with the index which selects it. Most of the outputs have been omitted for clarity.



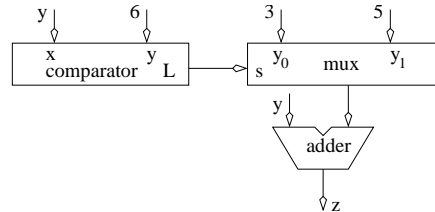8. **(3 pts.)** What is the value of the output labeled A?  
 a)  $y_1$       b)  $y_2$       c)  $y_4$       d)  $y_8$       e) None of the above
9. **(3 pts.)** What is the value of the output labeled B?  
 a)  $y_1$       b)  $y_6$       c)  $y_9$       d)  $y_{12}$       e) None of the above
10. **(5 pts.)** Which line of pseudo-code is equivalent to the following piece of hardware. Y is a 4-bit binary number.




- a) if (5 < Y) then Z = X+3 else Z = Y+5;
- b) if (6 < Y) then Z = Y+3 else Z = Y+5;
- c) if (6 > Y) then Z = X+3 else Z = Y+5;
- d) if (5 > Y) then Z = Y+3 else Z = Y+5;

You have a digital design which calls for a circuit which performs the following task (written as a C if/then statement). You have decided on the architecture. Its your job to design to complete the truth table for the glue-logic box (only an arbitrary portion of the complete truth table is shown).

```

if      (sum > 18) z = sum-18
else if (sum > 12) z = sum-12
else if (sum > 6)  z = sum-6
else          z = sum

```

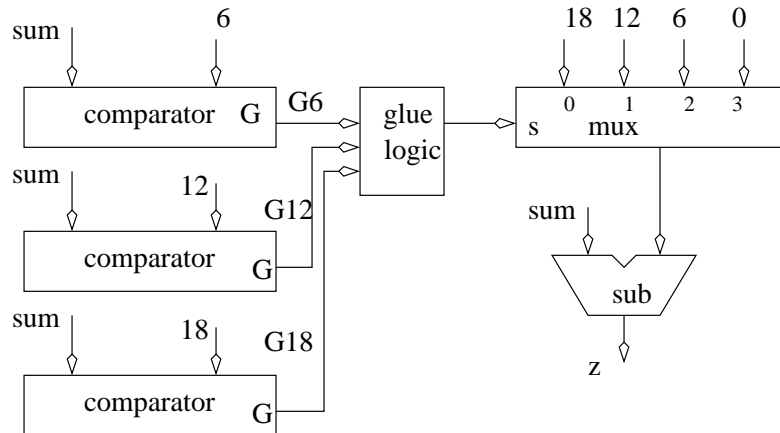


G6	G12	G18	select
0	0	0	a
1	1	0	b
1	0	1	c

11. **(3 pts.)**What is the (decimal) value of a in the truth table?  
 a) 0            b) 1            c) 2            d) 3            e) x
12. **(3 pts.)**What is the (decimal) value of b in the truth table?  
 a) 0            b) 1            c) 2            d) 3            e) x
13. **(3 pts.)**What is the (decimal) value of c in the truth table?  
 a) 0            b) 1            c) 2            d) 3            e) x


D	Q+	T	Q+	S	R	Q+	J	K	Q+
0	0	0	Q	0	0	Q	0	0	Q
1	1	1	Q'	0	1	0	0	1	0
				1	0	1	1	0	1
				1	1	x	1	1	Q'

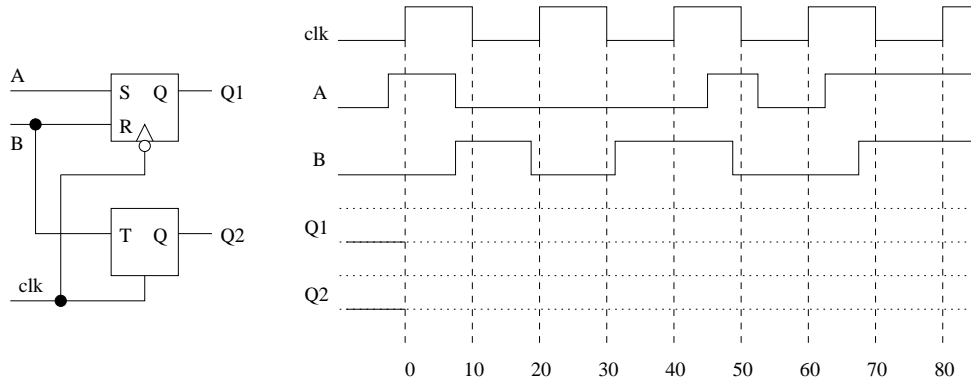For questions 14-19 use the following figure. Assume that initial value of Q is 0 (as shown in the figure), and that the outputs, after a period of rapid toggling, end-up at 0.



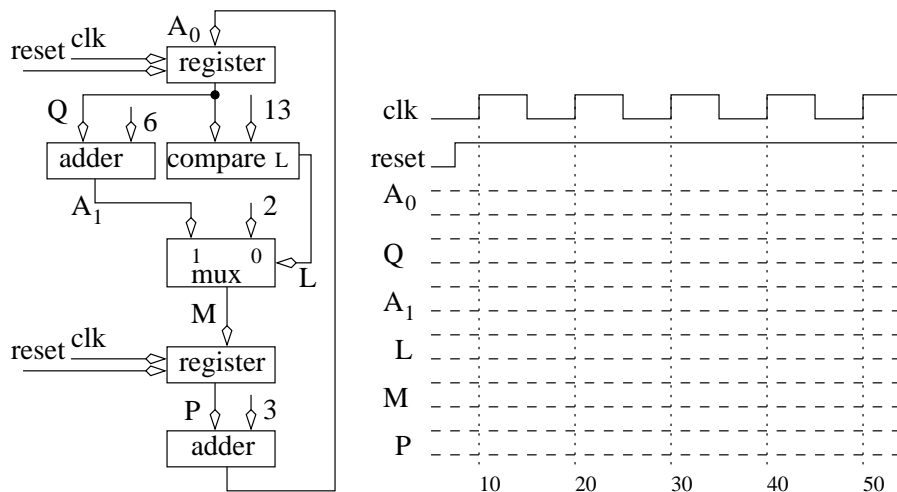14. (3 pts.) What is the value of Q1 at time 25
  - a) 0
  - b) 1
  - c) toggling
  - d) unknown
15. (2 pts.) What is the value of Q1 at time 35
  - a) 0
  - b) 1
  - c) toggling
  - d) unknown
16. (1 pt.) What is the value of Q1 at time 65
  - a) 0
  - b) 1
  - c) toggling
  - d) unknown
17. (2 pts.) What is the value of Q2 at time 25
  - a) 0
  - b) 1
  - c) toggling
  - d) unknown
18. (1 pts.) What is the value of Q2 at time 45
  - a) 0
  - b) 1
  - c) toggling
  - d) unknown

For problems 19-23 use the following figure and timing diagram. You should assume that all the devices process 5-bits data values.



19. (5 pts.) What is the value of  $Q$  at time 15?
  - a) 0
  - b) 3
  - c) 6
  - d) 9
  - e) none of the above
20. (4 pts.) What is the value of  $P$  at time 25?
  - a) 2
  - b) 9
  - c) 12
  - d) 15
  - e) none of the above
21. (3 pts.) What is the value of  $A_1$  at time 35?
  - a) 5
  - b) 9
  - c) 12
  - d) 18
  - e) none of the above
22. (2 pts.) What is the value of  $M$  at time 45?
  - a) 2
  - b) 5
  - c) 11
  - d) 12
  - e) none of the above
23. (1 pts.) What is the value of  $Q$  at time 55?
  - a) 5
  - b) 11
  - c) 12
  - d) 14
  - e) none of the above