

Circuits w/ memory

Sequential Circuits

Up to today $output = f(input)$

combinational

$output = f(input, \underline{state})$

sequential

- memory of past inputs
- current step in a process
- hidden stored binary number

let's look @ an example: Cross coupled NORs

SR latch






S = Set = make a value 1

R = Reset = make a value 0

Truth Table for NOR


a	b	$(a+b)'$
0	0	1
0	1	0
1	0	0
1	1	0

} if either input is 1
output is 0

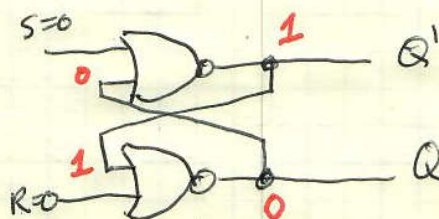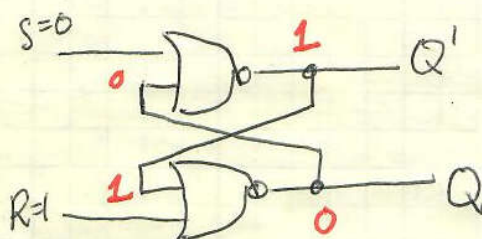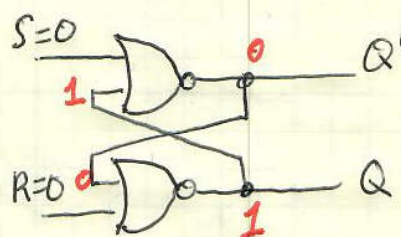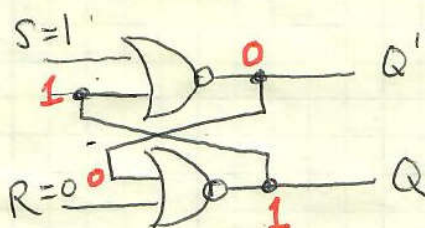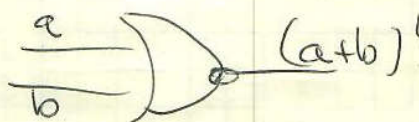

How \ When	Latch	Clock Latch	Flip Flop
D			
T			
SR			
JK			

S	R	Q^+	
0	0	Q	hold
0	1	0	reset
1	0	1	set
1	1	X	forbidden

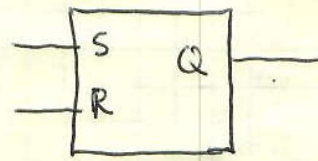

SR latch.

Basic Memory Elements

Store 1 bit of information

Stored bit is output as Q

Characterized by 2 attributes

When they sample data input

How they convert data input into stored bit

When Latch always sampling data input

Clock latch samples data input when clk input = 1

flip flop samples data input when clk input \uparrow

How

D	Q^+
0	0
1	1

J	Q^+
0	Q
1	Q'

S	R	Q^+
0	0	Q
0	1	0
1	0	1
1	1	X

J	K	Q^+
0	0	Q
0	1	0
1	0	1
1	1	Q'

Complete the timing diagram.

