

③ Symbolic to Truth table

Ex: $F(A, B, C) = AB' + A(B' + BC)'$

1. Identify input, outputs output on LHS, by itself, w/ parenthesis
2. Write shell of truth table

A	B	C	$F(A, B, C)$	AB'	$B' + BC'$	$A(B' + BC)'$
0	0	0			1	
0	0	1			1	
0	1	0			1	
0	1	1				
1	0	0	1	1	1	
1	0	1	1	1	1	
1	1	0			1	
1	1	1	1			1

3. Evaluate function for each input

Evaluate = substitute + apply operations (in right order)

$$F(1, 0, 1) = 1 \cdot 0' + 1 \cdot (0' + 0 \cdot 1)'$$

substitute

$$= 1 \cdot 1 + 1 \cdot (1 + 0 \cdot 0)'$$

apply operations
operator precedence

$$= 1 + 1 \cdot (1)$$

High parenthesis
Not
And
Low Or

$$= 1 + 1 \cdot 0$$

$$= 1 + 0$$

$$= 1$$

4. Break expression into

few parts, easy to put together, easy to evaluate

product term - AND of variables
ask, what input will cause product term to equal 1? What rows cause variables to equal 1?

④ Symbolic to Circuit Diagram

$$F(A, B, C) = A(B + C') + B'C$$

- Process
- 1) Identify lowest precedence operator in expression
 - 2) Draw this operator's gate
 - 3) Connect this gate's output to parent gate
 - 4) Remove this operation from the expression creating 0 or more sub expressions
 - 5) Parse each sub expression

expression

circuit diagram

$$A(B + C') + B'C$$

$$A(B + C')$$

$$B'C$$

$$B + C'$$

