


Chapter 6 Sequential Building Blocks

N-bit Register


Data input : N-bit vector $\vec{D} = d_{N-1} \dots d_1 d_0$ Data output : N-bit vector $\vec{Q} = q_{N-1} \dots q_1 q_0$ Control : 1-bit C

Status : None

Other : clk, reset


Behavior 

reset	clk	C	D	Q ⁺	Note
0	X	X	X	0	
1	0, 1, ↓	X	X	Q	
1	↑	0	X	Q	Hold
1	↑	1	D	D	Load

 

Internal organization


Wrong Solution

 

Because you can get a positive edge when
 $clk = 1$ $C \uparrow$

Introduces delay in clk net causing skew

Correct Solution

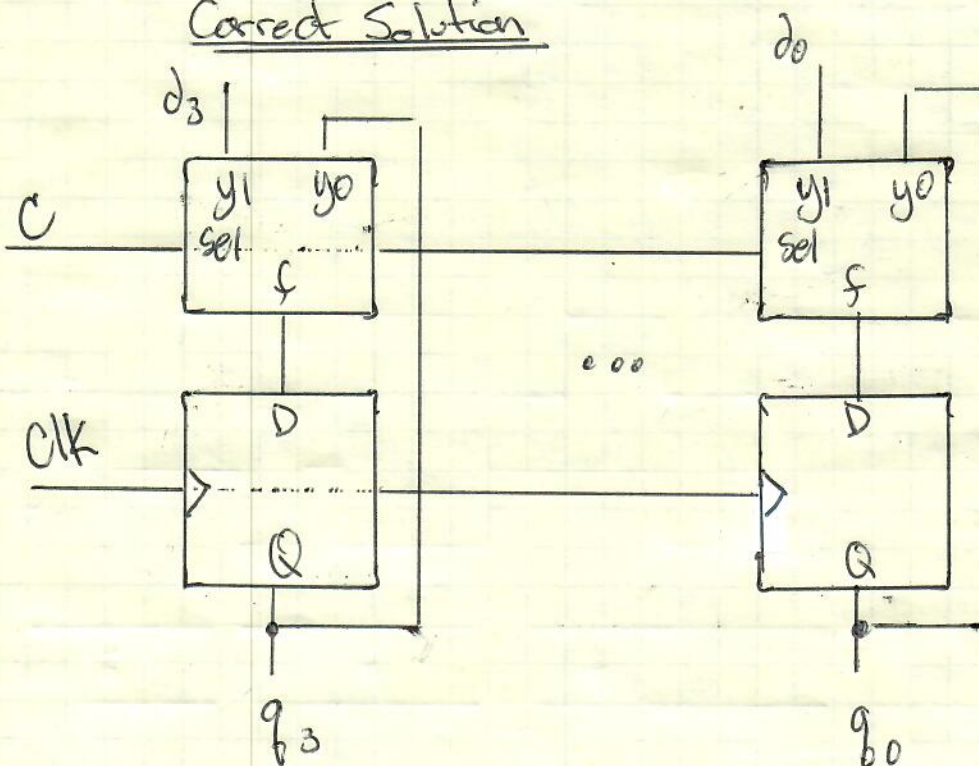

When $C = 1$ d_i passed to D input & loaded on next clk
 $C = 0$ q_i passed to D input & loaded on next clk