

CMPEN 271 – Fall 2010

Return this exam! No calculators!

Exam 1

Name:

1. **(2 pts.)** Convert 101000_2 to decimal.
a) 20 b) 24 c) 40 d) 42 e) none of the above
2. **(2 pts.)** Convert 42_{10} to binary.
a) 010010₂ b) 100010₂ c) 100110₂ d) 100100₂ e) none of the above
3. **(2 pts.)** Convert 42_{16} to binary.
a) b) c) 1000110₂ d) e) none of the above
1000010₂ 1000100₂ 1001000₂
4. **(2 pts.)** How many bits are required to represent the numbers between 0 and 127?
a) 7 b) 8 c) 128 d) 2^{128} e) none of the above
5. **(1 pt.)** Which of the following should be avoided.
a) Having a single output drive multiple inputs.
b) Connecting wires together.
c) Connecting a gate's output to another gate's input.
d) Connecting outputs together.
e) Connecting inputs together.
6. **(4 pt.)** Which expression is equivalent to $AB'(B+A'C)'$?
a) 0
b) $AB' + AB'C$
c) $AB' + AB'C'$
d) $A'B + A'BC'$
e) None of the above.

For questions 7-10 assume $F(A,B,C) = (A'B + A(B' + BC'))$

7. **(2 pts.)** What does $F(0,1,0)$ equal?
 a) 0 b) 1 c) C d) C' e) none of these
8. **(1 pts.)** What does $F(1,1,C)$ equal?
 a) 0 b) 1 c) C d) C' e) none of these
9. **(2 pts.)** How many AND gates does it take to realize F as is (do not simplify)?
 a) 1 b) 2 c) 3 d) 4 e) none of these
10. **(2 pts.)** How many OR gates does it take to realize F as is (do not simplify)?
 a) 1 b) 2 c) 4 d) 5 e) none of these

Utilize the following truth table for problems 11 and 12.

A	B	C	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

11. **(2 pts.)** What function is described by $\prod M(0, 3, 4, 6, 7)$?
 a) F b) F' c) G d) G' e) none of the above
12. **(2 pts.)** How many product terms does the canonical POS expression for F have?
 a) 1 b) 2 c) 3 d) 4 e) 5
13. **(3 pts.)** How many different SOP_{\min} solutions exist for $F(A,B,C) = \sum m(1,3,4,5,6)$?
 a) 1 b) 2 c) 3 d) 4 e) 5


A\BC	00	01	11	10
0				
1				

Utilize the following word statement for problems 14 and 15.

Design a 4-input $a_1a_0b_1b_0$, two output o_1o_0 digital circuit. $A = a_1a_0$ and $B = b_1b_0$ represent 2-bit binary numbers. The output is the smaller of A and B . For example, if $A = 10$ and $B = 01$, then $O = 01$.

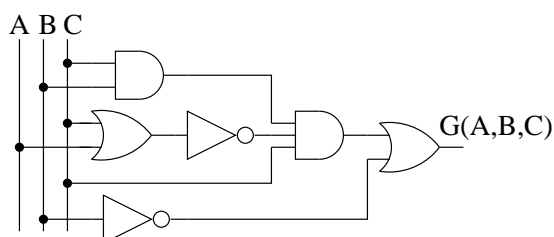14. (2 pt.) How many rows of the truth table will have $O_1 = 1$?
 a) 1 b) 4 c) 9 d) 12 e) None of the above.
15. (2 pt.) How many rows of the truth table will have $O_0 = 0$?
 a) 1 b) 4 c) 9 d) 12 e) None of the above.
16. (1 pt.) A grouping of 4 cells generates a product term with 4 variables. How many variables does the kmap have?
 a) 3 b) 4 c) 5 d) 6 e) None of the above.

For questions 17,18 use the figure below.



a_1	a_0	b_1	b_0	o_1	o_0
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1	0	1
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

Truth Table for O

17. (2 pt.) What is the symbolic representation of $G(A, B, C)$ (do not simplify).
 a) $BC + (A + C)' + B'$
 b) $BC(A+C)' + B'$
 c) $BC(A+C)'C + B'$
 d) B'
 e) None of the above.
18. (2 pt.) What is $G(1,1,0)=$?
 a) 1
 b) 0

19. (4 pt.) Determine the SOP_{min} expression for
 $F(A,B,C,D) = \Sigma m(1,2,3,7,8,9,11,15)$

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

- a) $A'B'D + A'B'C + ACD + AB'C'D' + AB'CD'$
b) $A'B'C + AB'C' + B'D + CD$
c) $A'B'C + A'BD + AB'C' + AB'D + CD$
d) $A'B' + AB' + CD$
e) None of the above.

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

20. (4 pt.) Determine the POS_{min} expression for
 $F(A,B,C,D) = \prod M(0,1,3,4,6,11,13,15) * \prod d(2,7,8,9,14)$

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

- a) $(A'+D)(A+B'+D')$
b) $(A'+C+D)(A+B'+D')(A'+C'+D)$
c) $(A+B'+D')(A'+D')(B+D')(A+B+C)$
d) $(A+B'+C+D)(A'+B+C'+D)(A+B'+C+D')$
e) None of the above.

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

21. (4 pt.) Determine the SOP_{min} expression for
 $F(A,B,C,D) = A'D + BD + AC'D' + AB'D$

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

- a) $A + D$
b) $AC' + D$
c) $AC'D' + D$
d) $AC'D + A'D + AB$
e) None of the above.