

CMPEN 271 – Spring 2012

Exam 2

Name:

PSU ID:

D	Q+	T	Q+	S	R	Q+	J	K	Q+
0	0	0	Q	0	0	Q	0	0	Q
0	0	0	Q	0	1	0	0	1	0
1	1	1	Q'	1	0	1	1	0	1
				1	1	x	1	1	Q'


- (1 * 10⁻⁶ pt.) Assuming a word size of 5 bits, interpret 10100 as a 2's complement number.
 a) -24 b) -12 c) -6 d) -2 e) None of the above.
- (1*10⁻⁶ pt.) Assuming a word size of 4 bits, determine the 2's complement representation of -7.
 a) 1011 b) 1101 c) 1100 d) 1001 e) None of the above.
- (1 * 10⁻⁶ pt.) An If/Then statement represents which piece of hardware?
 a) decoder b) mux c) comparator d) counter e) register
- (1 * 10⁻⁶ pt.) How many 2:1 muxes are needed to construct a 4-bit wide 4:1 mux?
 a) 8 b) 12 c) 18 d) 24 e) None of the above.

Questions 5-7 concern the construction of a bit-slice of a comparator. The questions will ask you to complete the entries in the truth table below denoted by a , b , and c .

G_{in}	L_{in}	E_{in}	x	y	G_{out}	L_{out}	E_{out}
0	0	1	1	0	a		
0	1	0	1	0		b	
1	0	1	1	0			c

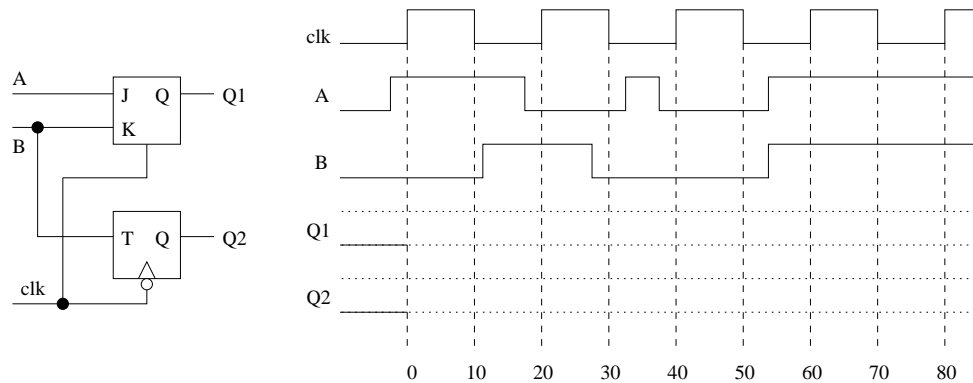5. ($1 * 10^{-6}$ pt.) What is the value of a ?
a) 0 b) 1 c) x
6. ($1 * 10^{-6}$ pt.) What is the value of b ?
a) 0 b) 1 c) x
7. ($1 * 10^{-6}$ pt.) What is the value of c ?
a) 0 b) 1 c) x

For questions 8-11 use the following figure




8. ($1 * 10^{-6}$ pt.) What is the value of Q1 at time 45
a) 0 b) 1 c) toggling
9. ($1 * 10^{-6}$ pt.) What is the value of Q1 at time 65
a) 0 b) 1 c) toggling
10. ($1 * 10^{-6}$ pt.) What is the value of Q2 at time 25
a) 0 b) 1 c) toggling
11. ($1 * 10^{-6}$ pt.) What is the value of Q2 at time 75
a) 0 b) 1 c) toggling

You have a digital design which calls for a circuit to perform the following task.

```

if      (sum > 18) z = sum-18
else if (sum > 12) z = sum-12
else if (sum > 6)  z = sum-6
else              z = sum
  
```

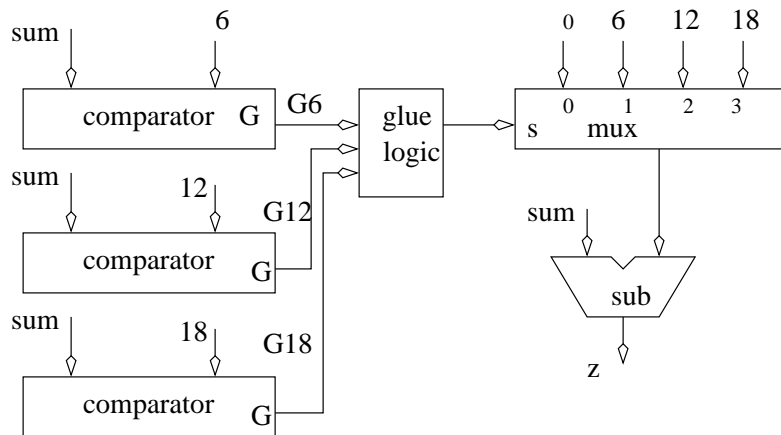You have decided on the architecture shown below. Its your job to design to complete the truth table for the the glue-logic box (only an arbitrary portion of the complete truth table is shown).




G6	G12	G18	select
1	1	0	a
1	0	0	b
1	1	1	c

12. ($1 * 10^{-6}$ pt.)What is the (decimal) value of a in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x
13. ($1 * 10^{-6}$ pt.)What is the (decimal) value of b in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x
14. ($1 * 10^{-6}$ pt.)What is the (decimal) value of c in the truth table?
 a) 0 b) 1 c) 2 d) 3 e) x

For questions 15,17 assume that a 4-bit up/down counter with parallel load has the following truth table. Complete the timing diagram below.

clk	c	D	Q^+	roll
0,1,↓	xx	x	Q	1 if Q=15 and c=01
↑	00	x	Q	0
↑	01	x	$Q + 1$	1 if Q=15 and c=01
↑	10	x	$Q - 1$	0
↑	11	D	D	0

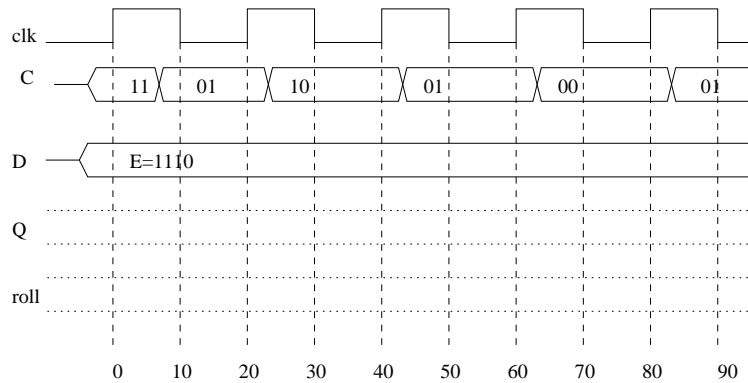


15. ($1 * 10^{-6}$ pt.) What is the value of Q at time 55?
a) 0000 b) 0001 c) 1110 d) 1111 e) none of the above
16. ($1 * 10^{-6}$ pt.) What is the value of Q at time 90?
a) 0000 b) 0001 c) 1110 d) 1111 e) none of the above
17. ($1 * 10^{-6}$ pt.) At which of the following times does roll=1
a) 30 b) 50 c) 70 d) 90 e) none of the above

You have a digital design which calls for a circuit to perform the following task.


```
for (i=0; i<42; i++) total = 2*total + i
```

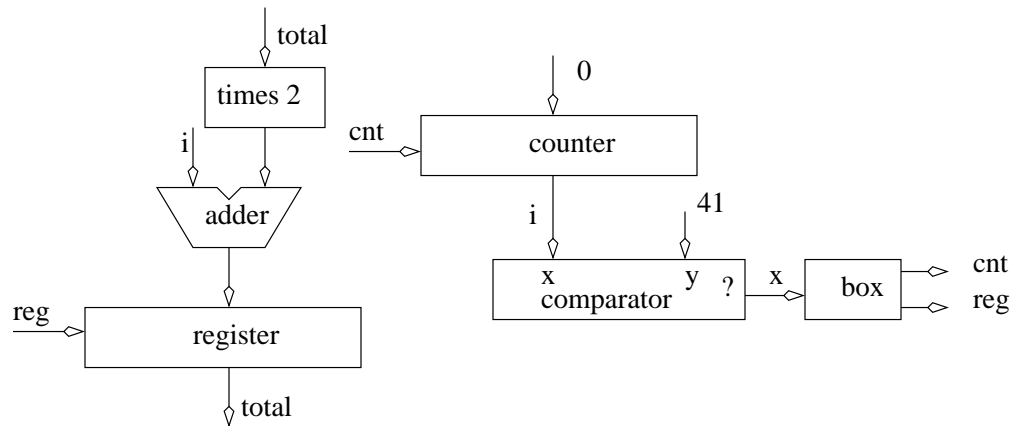You have decided on the architecture shown below. Its your job to finish the design. The box labeled "times 2" multiplies its input by 2 and outputs this value.



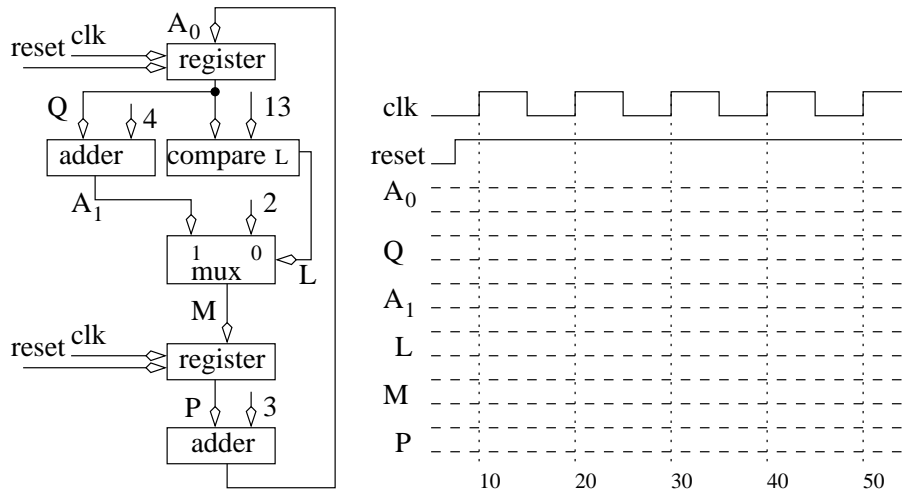18. ($1 * 10^{-6}$ pt.) Which output of the comparator should be connected to the input of "box"?
 a) G b) L c) E d) none of the above.
19. ($1 * 10^{-6}$ pt.) Assume that the counter has the truth table which is the same as question 15-17. What is the logic inside "box" to control the counter? Note, the output of the comparator is called "x."
 a) $cnt_1 = 0$ and $cnt_0 = 0$
 b) $cnt_1 = x'$ and $cnt_0 = 0$
 c) $cnt_1 = 0$ and $cnt_0 = x'$
 d) $cnt_1 = x$ and $cnt_0 = x'$
 e) None of the above.
20. ($1 * 10^{-6}$ pt.) How many logic gates are required in the "times 2" box?
 a) none b) a few c) some d) a lot e) infinite

For problems 21-25 use the following figure and timing diagram.



21. ($2 * 10^{-6}$ pts.) What is the value of P at time 15?
a) 0 b) 3 c) 4 d) 6 e) 11
22. ($2 * 10^{-6}$ pts.) What is the value of A_0 at time 25?
a) 3 b) 5 c) 7 d) 8 e) 10
23. ($2 * 10^{-6}$ pts.) What is the value of A_1 at time 35?
a) 8 b) 11 c) 14 d) 15 e) 18
24. ($2 * 10^{-6}$ pts.) What is the value of Q at time 45?
a) 5 b) 7 c) 11 d) 13 e) 14
25. ($2 * 10^{-6}$ pts.) What is the value of M at time 55?
a) 2 b) 5 c) 7 d) 8 e) 9