

Exam Ground Rules

- Exam is on Canvas
- Don't need to show up to room
- I will be on class Zoom to answer questions
- Held during class
- Exam opens @ 8:55 w/ 60 minutes
due @ 10:15
- 1 3x5 card
- Free response save as PDF - 20% penalty for email

Exam ReviewCh1 Numbers: 2's complement \longleftrightarrow DecimalCh4 Combinational Building Blocks

- Max
- Decoder
- Comparators
- Adder/Subtractor

I/O behavior
 Build big from smaller
 Internal structure
 Combinations
 Behavior
 Glue Logic

} If/then

Ch5 Basic Memory Elements

When How	D	T	SR	JK
L				
CL				
FF				

Timing Diagrams

Ch6 Sequential Building Blocks

- Register
- Shift register
- Counter
- RAM

I/O behavior
 Internal structure
 Combinations
 Behavior
 Glue logic

} Timing

Provide

- Truth tables for sequential control of BBB

State Diagram


State

History of previous inputs


Operating Mode of a system

Step in a process

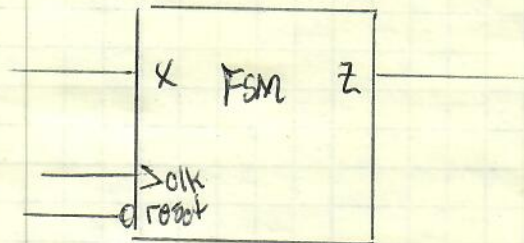
Build a FSM which outputs 1 when the number of 1's seen is a multiple of 3. Note 0 is a multiple of 3




* FSM "looks @ inputs on positive edge"

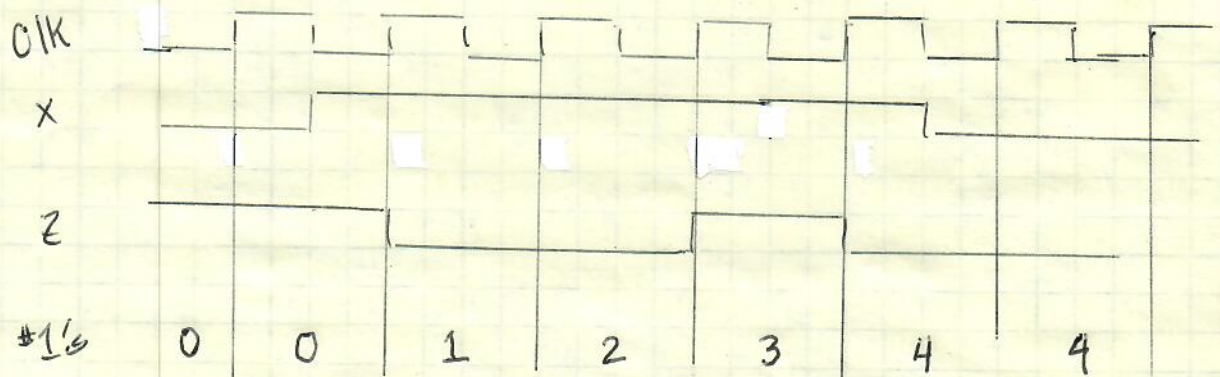

FSM

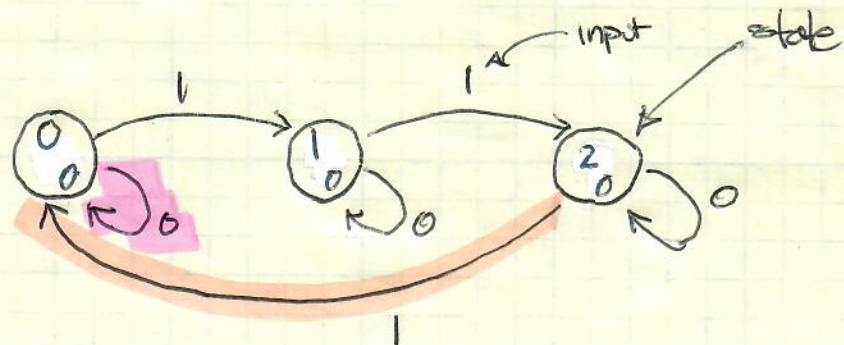

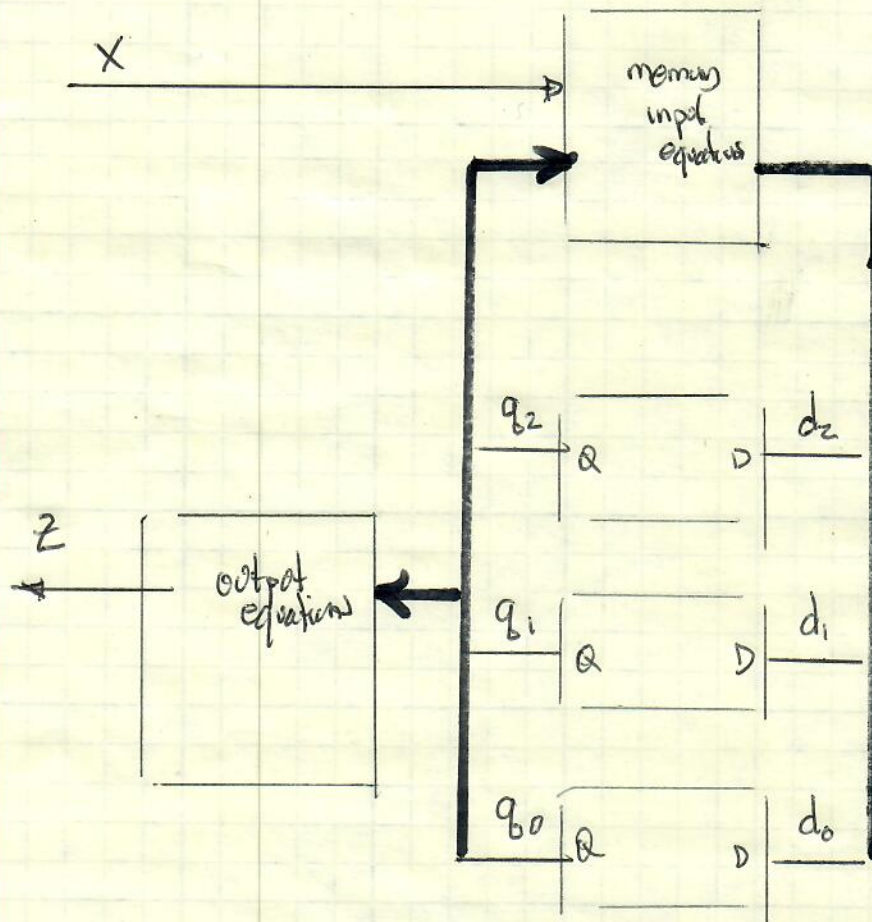

$q_0 = 1$ when in state 0

$q_1 = 1$ when in state 1

$q_2 = 1$ when in state 2

q_2	q_1	q_0	x	d_2	d_1	d_0
1	0	0	0	1	0	0
1	0	0	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	0	1	0

$$d_0 = q_2 x + q_0 x'$$


$$d_1 = q_1 x' + q_0 x$$

$$d_2 = q_2 x' + q_1 x$$

$$Z = q_0$$

Ch7 Finite State Machines

Circuits whose output = $f(\text{input}, \text{state})$

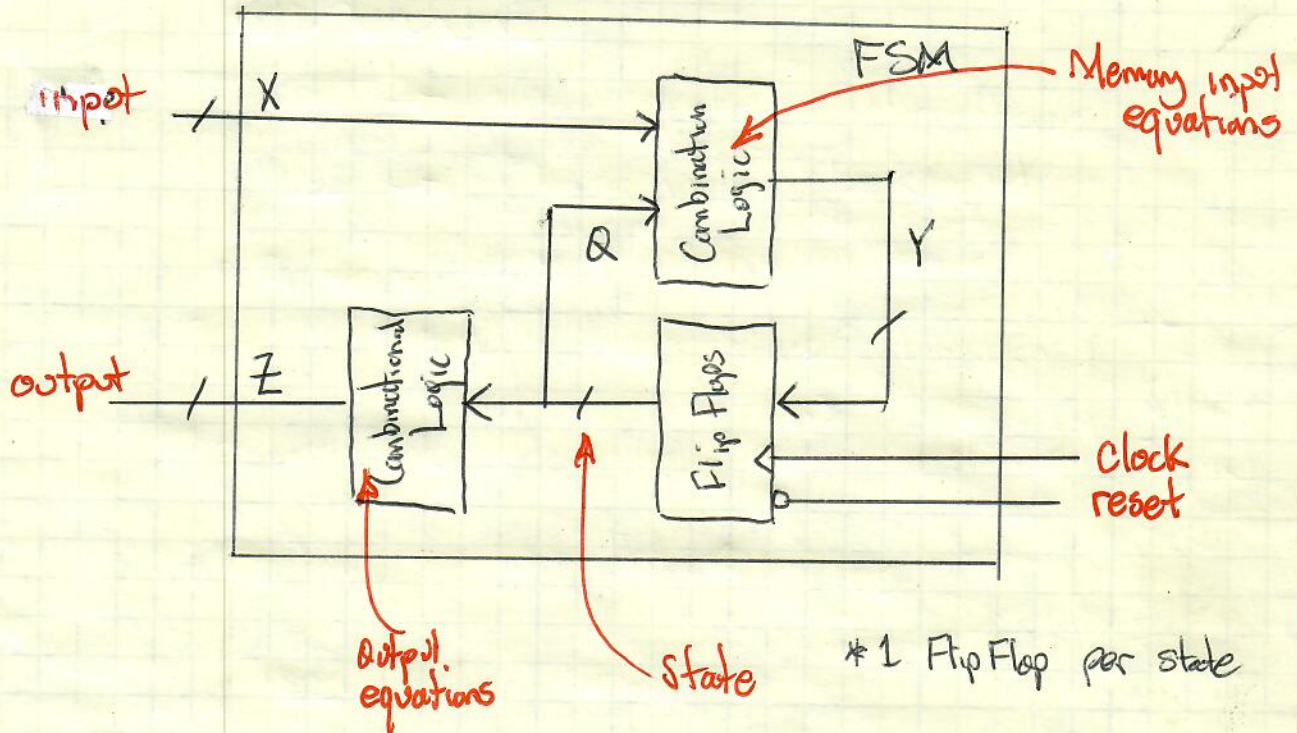Design Process