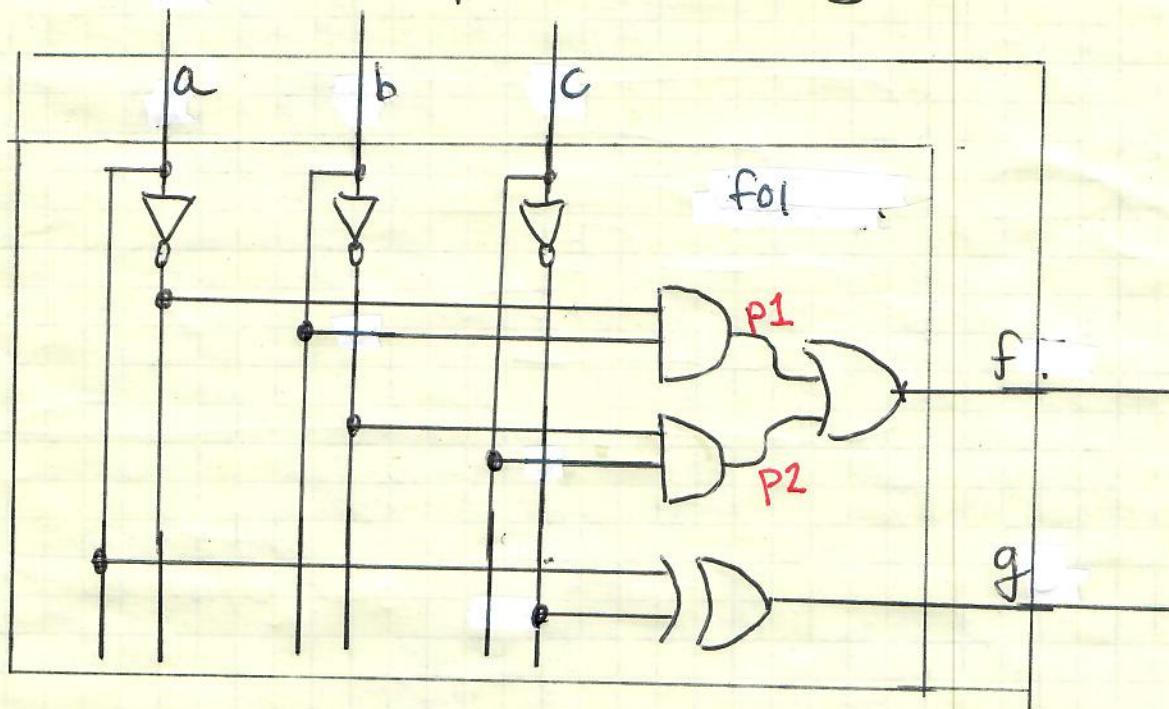


⑤ Circuit Diagram \rightarrow Verilog



```
module f01 (a, b, c, f, g);
```

```
input wire a, b, c;
```

```
output wire f, g;
```

```
wire p1, p2;
```

```
assign p1 = ~a & b;
```

```
assign p2 = ~b & c;
```

```
assign f = p1 | p2;
```

```
assign g = a ^ ~c;
```

```
endmodule
```

every input and output from module

begins and ends inside module

Concurrent

Continuous


Changing order will not change behavior

A wire should be on the LHS of exactly 1 assign

To check your Verilog code you will put it inside a testbench. A testbench is Verilog module constructed to apply inputs to a Verilog module called the unit under test (UUT).


The testbench has 2 main parts

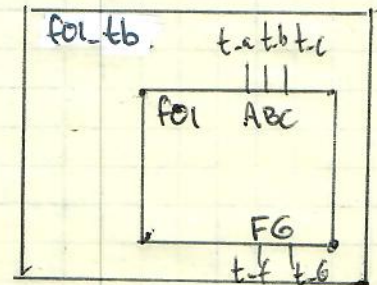- module instantiation
- Stimulus vector definition



You the simulate the testbench to check your Verilog code.

 The simulation will generate a timing diagram
A timing diagram is a plot of logic level vs time



A	B	C	F	G
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	0	0
1	1	1	0	1

$$F = a'b + b'c$$

$$G = a \oplus \sim c$$

