

CMPEN 271 – Fall 2011

Return this exam! No calculators!

Exam 1

Name:

ID:

1. (**2*10⁶ pts.**) Convert 101011_2 to decimal.
a) 16 b) 24 c) 42 d) 84 e) none of the above
2. (**2*10⁶ pts.**) Convert 35_{10} to binary.
a) 110101_2 b) 010111_2 c) 111111_2 d) 100011_2 e) none of the above
3. (**2*10⁶ pts.**) Convert 35_{16} to decimal.
a) 24 b) 35 c) 48 d) 53 e) none of the above
4. (**2*10⁶ pts.**) What is the largest number that you can make with N -bits?
a) $\log_2(N)$ b) N c) N^2 d) $2^N - 1$ e) none of the above

For questions 5-8 assume $F(A,B,C) = ((A'B)'C + (BC')')'$

5. (**2*10⁶ pts.**) What does $F(0,1,0)$ equal?
a) 0
b) 1
c) C
d) C'
e) Not enough information.
6. (**2*10⁶ pts.**) What does $F(1,1,C)$ equal?
a) 0
b) 1
c) C
d) C'
e) Not enough information.


7. (**1*10⁶ pt.**) How many OR gates does it take to realize F as is (do not simplify)?
- 1
 - 2
 - 3
 - 4
 - None of the above.
8. (**2*10⁶ pts.**) How many AND gates does it take to realize F as is (do not simplify)?
- 1
 - 2
 - 3
 - 4
 - None of the above.

Utilize the following truth table for problems 9-12.

A	B	C	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

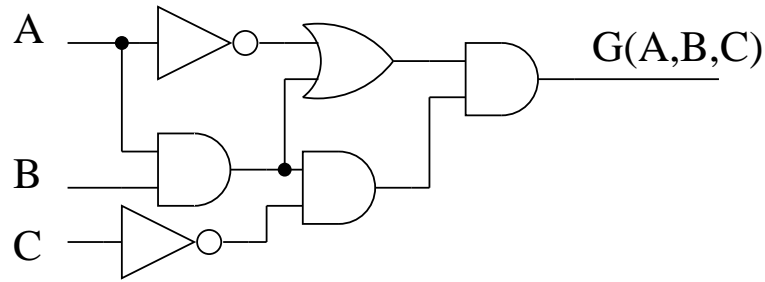9. (**1*10⁶ pt.**) What function is described by $\sum m(0, 3, 4, 6, 7)$?
- F
 - F'
 - G
 - G'
 - none of the above
10. (**1*10⁶ pt.**) What function is described by $\prod M(0, 4, 5)$?
- F
 - F'
 - G
 - G'
 - none of the above
11. (**1*10⁶ pt.**) How many product terms does the canonical SOP expression for F' have?
- 1
 - 2
 - 3
 - 4
 - 5
12. (**1*10⁶ pt.**) How many sum terms does the canonical POS expression for G have?
- 1
 - 2
 - 3
 - 4
 - 5

Utilize the following circuit diagram for problems 13,14.



13. (4×10^6 pts.) What is the symbolic representation of $G(A, B, C)$ as shown?
 - a) $ABC'(A'+AB)$
 - b) $(AB+A')C'$
 - c) $(A'+AB)BC'$
 - d) ABC'
 - e) None of the above.
14. (2×10^6 pts.) What does $G(0,1,0)$ equal?
 - a) 0
 - b) 1
15. (1×10^6 pt.) Which of the following should be avoided.
 - a) Connecting outputs together.
 - b) Connecting inputs together.
 - c) Having a single output drive multiple inputs.
 - d) Connecting wires together.
 - e) Connecting an input to an output.
16. (1×10^6 pt.) Which expression is equivalent to $(AB')'(B'+AC)$? Hint, use De Morgans, distribute, and simplify.
 - a) 0
 - b) $AB' + AB'C$
 - c) $AB' + AC + B' + AB'C$
 - d) $A'B' + ABC$
 - e) None of the above.

Utilize the following word statement for problems 17-19.

Design a 4-input $a_1a_0b_1b_0$. $A = a_1a_0$ and $B = b_1b_0$ represent 2-bit binary numbers. The output should be the product (multiplication) of the inputs, that is $O = A * B$.

17. (1×10^6 pt.) How many bits of output must the circuit have?
 a) 1 b) 2 c) 3 d) 4 e) 5
18. (1×10^6 pt.) How many rows will the truth table have?
 a) 4 b) 8 c) 16 d) 32 e) None of the above.
19. (1×10^6 pt.) How many rows of the truth table will have $o_0 = 1$? Note that o_0 is the least significant bit of the output.
 a) 1 b) 3 c) 9 d) 12 e) None of the above.
20. (1×10^6 pt.) A cell in a 8 variable kmap is adjacent to how many other cells?
 a) 3
 b) 8
 c) 16
 d) 64
 e) 256
21. (2×10^6 pts.) How many different SOP_{\min} solutions exist for $F(A,B,C) = \sum m(0,2,5,6,7)$?

- a) 1
- b) 2
- c) 3
- d) 4
- e) 5

$A \setminus BC$	00	01	11	10
0				
1				

22. (4×10^6 pts.) Determine the SOP_{\min} expression for $F(A,B,C,D) = \sum m(0,1,5,6,7,8,9,14)$

- a) $A'B'C' + A'BD + BCD' + AB'C'$
- b) $B'C' + A'BD + BCD'$
- c) $A'C'D + BCD' + B'C'$
- d) $B'C'D' + B'C'D + A'BD + BCD'$
- e) None of the above.

$AB \setminus CD$	00	01	11	10
00				
01				
11				
10				

23. (4*10⁶ pts.) Determine the SOP_{min} realization for F.

A	B	C	F
0	0	X	1
1	0	0	0
1	1	X	X
0	X	0	1
1	0	1	0
X	1	1	X

A\BC	00	01	11	10
0				
1				

- a) $A' + B$
b) $A + BC'$
c) $A + C'$
d) $A'BC' + A'B'$
e) None of the above.
24. (6*10⁶ pts.) Determine the POS_{min} expression for $F(A, B, C, D) = (A' + D)(A' + B' + C')(A + B + D')(B' + C' + D')$, show your work.