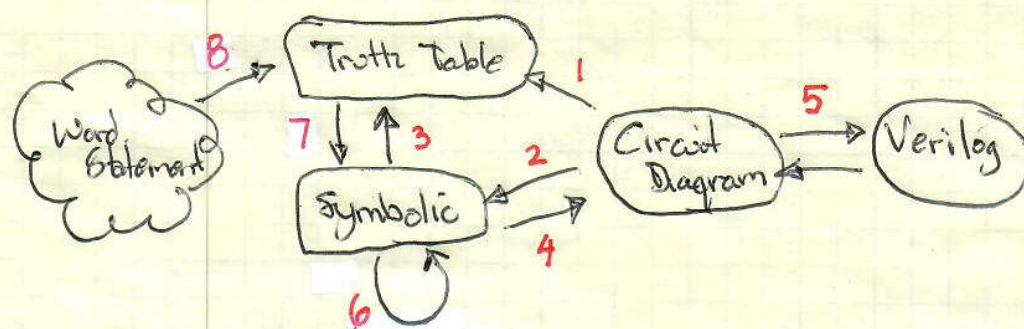


5 representations of logical functions







Word Statement \equiv Describes I/O & behavior using words


Truth Table \equiv Enumeration of every input & associated output

Symbolic \equiv Description of operations and operands to convert input to output

Circuit Diagram \equiv Picture of circuit elements & interconnections to transform input to output

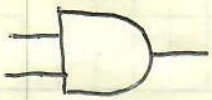Elementary Logic Functions

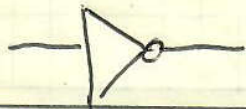Function	AND	OR	XOR	Not																																																			
Word Statement	N-inputs 1 output that equals 1 when <u>All</u> inputs equal 1 else 0	N-inputs 1 output that equals 1 when <u>ANY</u> input equals 1, else 0	2 inputs 1 output that equals 1 when inputs are different, else 0	1 input 1 output that does not equal the input																																																			
Symbolic	$A * B$	$A + B$	$A \oplus B$	A'																																																			
Truth Table	<table><tr><th>A</th><th>B</th><th>$A * B$</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	A	B	$A * B$	0	0		0	1		1	0		1	1		<table><tr><th>A</th><th>B</th><th>$A + B$</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	A	B	$A + B$	0	0		0	1		1	0		1	1		<table><tr><th>A</th><th>B</th><th>$A \oplus B$</th></tr><tr><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td></td></tr></table>	A	B	$A \oplus B$	0	0		0	1		1	0		1	1		<table><tr><th>A</th><th>A'</th></tr><tr><td>0</td><td></td></tr><tr><td>1</td><td></td></tr></table>	A	A'	0		1	
A	B	$A * B$																																																					
0	0																																																						
0	1																																																						
1	0																																																						
1	1																																																						
A	B	$A + B$																																																					
0	0																																																						
0	1																																																						
1	0																																																						
1	1																																																						
A	B	$A \oplus B$																																																					
0	0																																																						
0	1																																																						
1	0																																																						
1	1																																																						
A	A'																																																						
0																																																							
1																																																							
Circuit Diagram																																																							

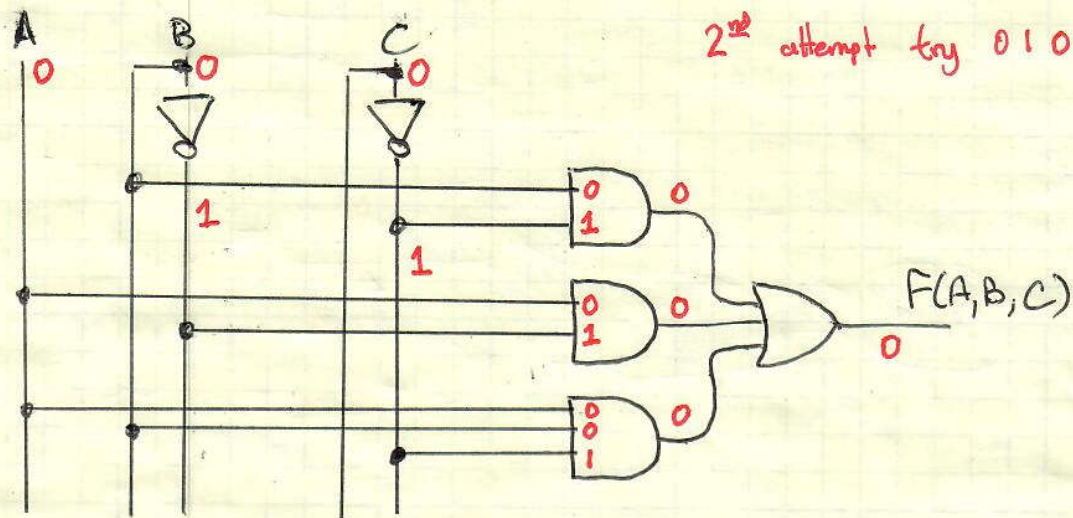① Circuit Diagram \rightarrow Truth TableObservations

1. Gates may have different # of inputs
2. Lines represent wire
3. Logic levels propagate instantly on wire
4. Black dots indicate connection btw wires
5. Crossing wires with no dot are not connected
6. Outputs are not connected together
7. Inputs must be tied to a signal source
8. An output can drive the input of many gates

Step 1

Identify
inputs &
outputs

A, B, C

F


Step 2

Build shell
of truth
table

A	B	C	F(A,B,C)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Step 3

Evaluate
• apply input
• compute output for
each gate until
you reach output

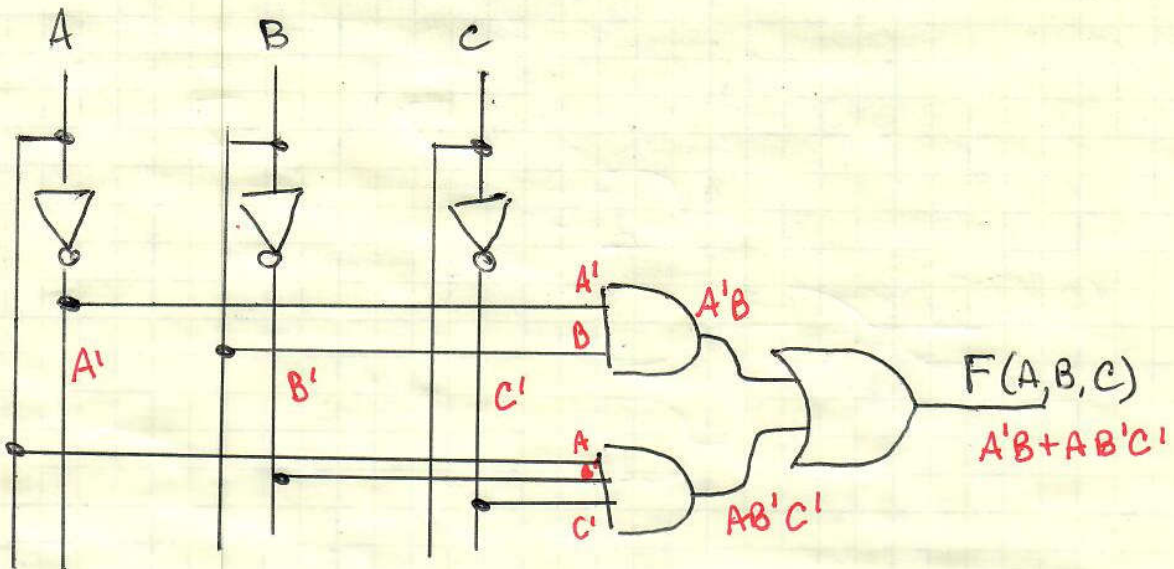② Circuit Diagram to Symbolic

- Flow inputs to output
- Gate output is computed when all inputs have values